

$$U_{is} = V_4 - V_2 \Rightarrow V_4 = U_{is} + V_2$$

$$i_5 = \frac{V_4 - V_1}{R_5} = \frac{V_2 - V_1 + U_{is}}{R_5}$$

$U_{12} = U_{15} = 30V, i_5 = 3A, R_1 = R_5 = 5\Omega, R_3 = R_4 = 10\Omega, i_2 = 0A$

aplic V_0 -referinta $\Rightarrow V_0 = 0V$

$$U_{12} = V_3 - V_0 \Rightarrow V_3 = U_{12} = 30V$$

$$i_1 = \frac{V_3 - V_0}{R_1} \quad i_3 = \frac{V_1 - V_3}{R_3} \quad i_4 = \frac{V_0 - V_2}{R_4} \quad i_5 = \frac{V_2 - V_1 + U_{is}}{R_5}$$

aplic legea I a lui Kirchhoff in nodul 1 si 2

$$1: i_3 = i_5 + i_5 \Rightarrow i_3 = i_4 \Rightarrow \frac{V_1 - 30}{10} = \frac{-V_2}{10} \Rightarrow V_1 = 30 - V_2$$

$$2: i_4 = i_5 + i_5$$

$$i_3 = i_5 + i_5 \Rightarrow \frac{V_1 - 30}{10} = \frac{V_2 - V_1 + 30}{5} + 3 \Leftrightarrow \frac{30 - V_2 - 30}{10} = \frac{V_2 - 30 + V_2 + 30}{5} + 3 \quad | \cdot 10 \Leftrightarrow -V_2 = 4V_2 + 30 \Rightarrow V_2 = -6V$$

$$V_1 = 30 - (-6) = 36V$$

$$i_1 = \frac{30 - 0}{5} = 6A \quad i_3 = \frac{36 - 30}{10} = 0,6A \quad i_4 = \frac{-6}{10} = -0,6A \quad i_5 = \frac{-6 - 36 + 30}{5} = -2,4A$$

aplic legea I a lui Kirchhoff in nodul 3

$$3: i_1 = i_2 + i_3 \Rightarrow i_2 = i_1 - i_3 = 6 - 0,6 = 5,4A$$

$$b) P = \sum R i^2 = R_1 i_1^2 + R_3 i_3^2 + R_4 i_4^2 + R_5 i_5^2 = 5 \cdot 6^2 + 10 \cdot 0,6^2 + 10 \cdot 0,6^2 + 5 \cdot (-2,4)^2 = 216W \quad (1)$$



aplic legea a II-a a lui Kirchhoff in nodul 0

$$0: U_{is} + i_5 R_5 - U_{is} = 0 \Rightarrow U_{is} = U_{is} - i_5 R_5 = 30 - (-2,4) \cdot 5 = 42V$$


$$P_{\text{total}} = i_2 \cdot U_{12} + i_5 \cdot U_{is} + U_{is} \cdot i_5 = 5,4 \cdot 30 + (-2,4) \cdot 30 + 42 \cdot 3 = 216W \quad (2)$$

Dim 1) si 2) \Rightarrow se verifica bilantul puterilor

c)

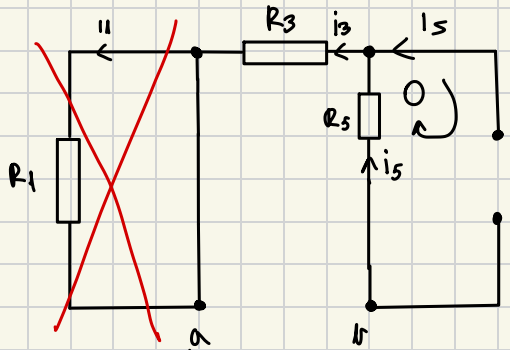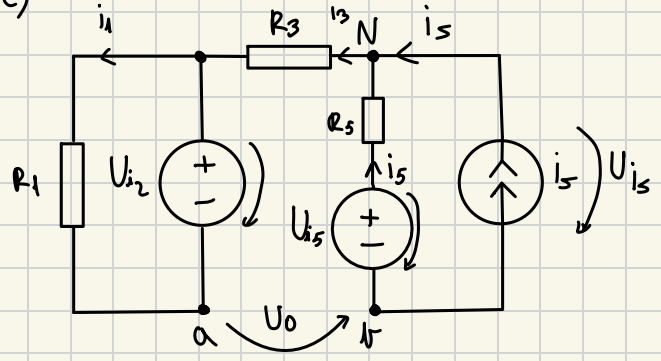
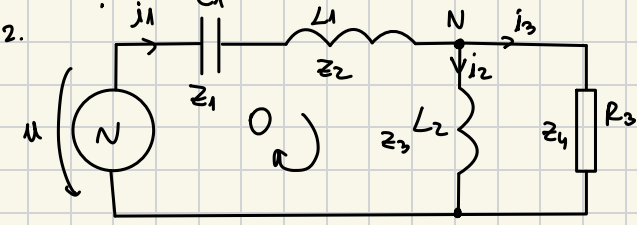
$$R_3, R_5 \text{ - paralel} \Rightarrow R_i = \frac{R_3 \cdot R_5}{R_3 + R_5} = \frac{5 \cdot 10}{5 + 10} = \frac{50}{15} = 3,33\Omega$$



a) $u(t) = \frac{20}{\sqrt{2}} \sin(\omega t + \frac{\pi}{2})$

$U_{R2} = \frac{R_2}{Z_2} = \frac{10}{\sqrt{2}} = 10V$

$f = 200 \text{ Hz} \Rightarrow \omega = 2\pi f = 400\pi \text{ rad/s}$

$Z_1 = \frac{1}{j\omega C_1} = \frac{j1}{j \cdot 400\pi \cdot 25 \cdot 10^{-6}} = -100j \Omega$

$Z_2 = j\omega L_1 = j \cdot 400\pi \cdot \frac{100}{4\pi} = 100j \Omega$

$Z_3 = j\omega L_2 = j \cdot 400\pi \cdot \frac{100}{4\pi} = 100j \Omega$

$Z_4 = R_3 = 20 \Omega$

$Z_{\text{eq}} = Z_1 + Z_2 + \frac{Z_3 \cdot Z_4}{Z_3 + Z_4} = -100j + 100j + \frac{20 \cdot 100j}{20 + 100j} = \frac{2000j}{20 + 100j} = \frac{2000j}{20(1 + 5j)} = \frac{100j}{1 + 5j} = \frac{100j(1 - 5j)}{1 + 25} = \frac{500}{26} + \frac{100j}{26}$

cum $\text{Im}\{Z_{\text{eq}}\} > 0 \Rightarrow$ caracter inductiv

b) $\underline{U} = U(\cos \frac{\pi}{2} + j \sin \frac{\pi}{2}) = jU = 10j \text{ V}$

$\underline{I}_1 = \frac{\underline{U}}{Z_{\text{eq}}} = \frac{10j}{\frac{500 + 100j}{26}} = 0,1 + 0,5j$

$\varphi = \arctan \frac{0,5}{0,1} = \arctan 5$

$|\underline{I}_1| = \sqrt{0,1^2 + 0,5^2} = 0,5$

$i_1(t) = 0,5 \sin(400\pi t + \arctan 5)$

aplic legua a II-a a lui Kirchhoff in nodul O

$0: \underline{I}_1(\underline{Z}_1 + \underline{Z}_2) + \underline{I}_2 \underline{Z}_3 - \underline{U} = 0 \Rightarrow \underline{I}_2 = \frac{\underline{U} - \underline{I}_1(\underline{Z}_1 + \underline{Z}_2)}{\underline{Z}_3} = \frac{10j - (0,1 + 0,5j) \cdot 0}{100j} = 0,1 \text{ A}$

$\varphi = \arctan \frac{0}{0,1} = 0$

$|\underline{I}_2| = \sqrt{0,1^2 + 0} = 0,1$

$i_2(t) = 0,1 \sin(400\pi t)$

aplic legua I a lui Kirchhoff in nodul N

N: $\underline{I}_1 = \underline{I}_2 + \underline{I}_3 \Rightarrow \underline{I}_3 = \underline{I}_1 - \underline{I}_2 = 0,1 + 0,5j - 0,1 = 0,5j$

$\varphi = \arctan \frac{0,5}{0} = \arctan \infty = \frac{\pi}{2}$

$|\underline{I}_3| = \sqrt{0 + 0,5^2} = 0,5$

$i_3(t) = 0,5 \sin(400\pi t + \frac{\pi}{2})$

c) $P = \underline{U} \cdot \underline{I}^* = 10j(0,1 - 0,5j) = 5 + j$

$P_{\text{activ}} = R_3 \cdot |\underline{I}_3|^2 = 20 \cdot 0,5^2 = 5$

$P_{\text{reactiv}} = j \cdot 100 \cdot 0,5^2 + j \cdot 100 \cdot 0,1^2 - j \cdot 100 \cdot 0,1^2 = j$

$\hookrightarrow P = P_{\text{activ}} + P_{\text{reactiv}}$

