

DC Proposed Problems

1.1 An electron has the elementary charge $e = 1.6 \cdot 10^{-19} C$
 $\Rightarrow 6400$ electrons will have $6400 \cdot 1.6 \cdot 10^{-19}$

$$q(5V)C = 6400 \cdot 1.6 \cdot 10^{-19} C = 10240 \cdot 10^{-19} C$$

1.2 $I = 2A$

$$\Delta t = 10\Delta t$$

$$W = 4.6 kJ = 4.6 \cdot 10^3 J$$

$$U = ?$$

$$W = P \cdot \Delta t = (U \cdot I) \cdot \Delta t \Rightarrow U = \frac{W}{I \cdot \Delta t} = \frac{4.6 \cdot 10^3}{2 \cdot 10} = 230 V$$

$$+ 6.1 \cdot 10^3 J \cdot 230 V = 230 \cdot \frac{(230)^2 + 8.0 \cdot 10^3 \cdot 230}{2} = \Rightarrow U = 230 V$$

1.3 $P = 80 W$

$$\Delta t = 3h = 3 \cdot 3600 s$$

$$W = ?$$

$$W = P \Delta t = 80 \cdot 3 \cdot 3600 = 864 kJ$$

1.4 $I = 10 A$

$$U = 230 V$$

$$W = 80 kJ = 80 \cdot 10^3 J$$

$$\Delta t = ?$$

$$W = U \cdot I \cdot \Delta t \Rightarrow \Delta t = \frac{W}{U \cdot I} = \frac{80 \cdot 10^3}{230 \cdot 10} = 34.78 \Delta t$$

$$\Rightarrow \Delta t = 34.78 \Delta t$$

1.5

$$q(t) = 10 \sin 4\pi t \text{ mC}$$

$$u(t) = 2 \cos 4\pi t \text{ V}$$

a) $p(0.3) = ?$

$$i(t) = \frac{dq}{dt} = 40\pi \cos(4\pi t) \mu A = 40 \cdot 10^{-3} \pi \cos(4\pi t) \mu A$$

$$\begin{aligned} p(t) &= u(t) i(t) = 2 \cos(4\pi t) \cdot 40 \cdot 10^{-3} \pi \cos(4\pi t) = \\ &= 80 \cdot 10^{-3} \pi \cos^2(4\pi t) \text{ W} \end{aligned}$$

$$p(0.3) = 0.1645 \text{ W}$$

$$\begin{aligned} \text{i)} \quad W &= \int_0^t p dt = 80 \cdot 10^{-3} \pi \int_0^{0.8} \cos^2(4\pi t) dt \\ &= 80 \cdot 10^{-3} \pi \int_0^{0.8} \frac{1 + \cos(8\pi t)}{2} dt = 80 \cdot 10^{-3} \pi \left[\int_0^{0.8} \frac{1}{2} dt + \right. \\ &\quad \left. + \int_0^{0.8} \frac{\cos 8\pi t}{2} dt \right] = 80 \cdot 10^{-3} \pi \left[\frac{1}{2} t \Big|_0^{0.8} + \frac{80 \cdot 10^{-3} \pi}{2} \cdot \frac{\sin 8\pi t}{8\pi} \Big|_0^{0.8} \right] \\ &= 32 \cdot 10^{-3} \pi + 5 \cdot 10^{-3} \sin 8\pi t \Big|_0^{0.8} = 32 \cdot 10^{-3} \pi + 5 \cdot 10^{-3} \sin(8\pi \cdot 0.8) \\ &= 32 \cdot 10^{-3} \pi + 5 \cdot 10^{-3} \cdot 0.95 = (32\pi + 5 \cdot 0.95) \cdot 10^{-3} \\ &= 105.28 \cdot 10^{-3} \text{ J} \end{aligned}$$

1.6

$$U = 12 \text{ V}$$

$$I = 150 \mu A = 150 \cdot 10^{-3} \text{ A}$$

a) $P = U \cdot I = 12 \cdot 150 \cdot 10^{-3} = 1.8 \text{ W}$

b) $St = 30 \text{ min} = 1800 \text{ s}$ $W = P \cdot St = 3240 \text{ J}$

1.4

$$R_1 = 15 \Omega$$

$$R_2 = 10 \Omega$$

$$R_3 = 7 \Omega$$

$$R_4 = 5 \Omega \quad a) R_S = R_3 + R_4 \Rightarrow R_S = 12 \Omega$$

$$U = 24 V \quad \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow \frac{1}{R_p} = \frac{1}{15} + \frac{1}{10} + \frac{1}{12}$$

$$a) R_e = ?$$

$$\frac{1}{R_e} = \frac{15}{60} \Rightarrow R_e = 4 \Omega$$

$$b) J = ?$$

$$c) J_3 = ? \quad b) J = \frac{U}{R_e} = \frac{24}{4} = 6 A$$

$$d) U_R = ?$$

$$P_{R_2} = ?$$

$$d) U_R = J \cdot R_2 = 6 \cdot 10 = 60 V$$

$$c) 0 = J_1 R_1 - U \Rightarrow J_1 = \frac{U}{R_1} = \frac{24}{15} \Rightarrow J_1 = 1.6 A$$

$$J = J_1 + J' \Rightarrow J' = 4.4 A$$

$$J_2 = J_1 R_1 - U \Rightarrow J_2 = \frac{J_1 R_1}{R_2} = \frac{1.6 \cdot 15}{10} = 2.4 A$$

$$J_3 = J' - J_2 \Rightarrow J_3 = 2 A$$

$$d) U_R = J_3 R_4 \Rightarrow U_R = 10 V$$

$$P_{R_2} = J_2^2 R_2 \Rightarrow P_{R_2} = 57.6 W$$

$$A_{N,L} = L \left(= \mu_0 t + \epsilon_0 t = g \right)$$

$$W_d \cdot \gamma = \mu_0 t$$

1.8

$$R_1 = 10 \Omega$$

$$R_2 = 9 \Omega$$

$$R_3 = 15 \Omega$$

$$R_4 = 10 \Omega$$

$$U = 60 \text{ V}$$

a) $R_{\text{e}} = ?$

$$\text{a)} \quad R_p = \frac{R_3 R_4}{R_3 + R_4} = \frac{15 \cdot 10}{15 + 10} = \frac{150}{25} \Rightarrow R_p = 6 \Omega$$

b) $\text{Y} = ?$

$$R_D = R_p + R_2 \Rightarrow R_D = 15 \Omega$$

c) $\text{J}_2 = ?$

$$\text{Re} = \frac{R_1 R_D}{R_1 + R_D} = \frac{10 \cdot 15}{10 + 15} \Rightarrow \text{Re} = 6 \Omega$$

d) $U_{R_3} = ?$

$$\text{P}_{R_4} = ? \quad \text{e)} \quad U = \text{Y} \text{Re} \Rightarrow \text{Y} = \frac{U}{\text{Re}} \Rightarrow \text{Y} = 10 \text{ A}$$

c) $\text{Y} = \text{Y}_1 + \text{Y}_2$

$$0 = \text{Y}_1 R_1 + U \Rightarrow \text{Y}_1 = \frac{U}{R_1} \Rightarrow \text{Y}_1 = 6 \text{ A}$$

$$\text{Y}_2 = \text{Y} - \text{Y}_1 \Rightarrow \text{Y}_2 = 4 \text{ A}$$

$$\text{d)} \quad 0 = \text{Y}_2 R_2 + \text{Y}_3 R_3 - \text{Y}_1 R_1 \Rightarrow \text{Y}_3 = \frac{\text{Y}_1 R_1 - \text{Y}_2 R_2}{R_3} = \frac{10 \cdot 10 - 4 \cdot 9}{15} = 14 \text{ A} - 36 \text{ A} = 0$$

$$\text{Y}_3 = 1.6 \text{ A}$$

$$U_{R_3} = \text{Y}_3 R_3 \Rightarrow U_{R_3} = 24 \text{ V}$$

$$\text{P}_{R_4} = \text{Y}_4^2 R_4$$

$$\text{Y}_2 = \text{Y}_3 + \text{Y}_4 \Rightarrow \text{Y}_4 = 2.4 \text{ A}$$

$$\text{P}_{R_4} = 57.6 \text{ W}$$

1.9

$$R_1 = 4 \Omega$$

$$R_2 = 10 \Omega$$

$$R_3 = 15 \Omega$$

$$R_4 = 5 \Omega$$

$$U = 75 V$$


a) $R_E = ?$

b) $I = ?$

c) $I_3 = ?$

d) $U_{R2} = ?$

e) $P_{R4} = ?$

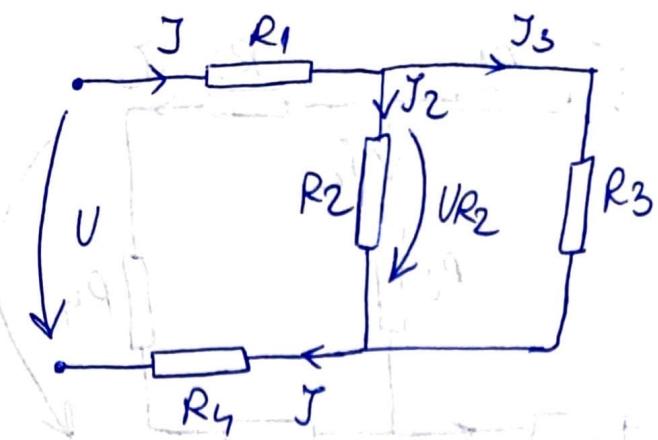

$$a) R_P = \frac{R_2 R_3}{R_2 + R_3} \Rightarrow R_P = \frac{10 \cdot 15}{10 + 15} \Rightarrow R_P = 6 \Omega$$

$$R_E = R_1 + R_P + R_4 \Rightarrow R_E = 15 \Omega$$

a)

$$U = I R_E \Rightarrow I = \frac{U}{R_E}$$

$$I = \frac{75}{15} = 5 A$$

$$c) I R_1 + I_2 R_2 + I R_4 = U$$

$$\Rightarrow I_2 = \frac{U - I(R_1 + R_4)}{R_2}$$

$$I_2 = \frac{75 - 5(4+5)}{10} = \frac{75 - 45}{10} = 3 A$$

$$I = I_2 + I_3 \Rightarrow I_3 = I - I_2 = 5 - 3 = 2 A$$

$$d) U_{R2} = I_2 R_2 \Rightarrow U_{R2} = 30 V$$

$$P_{R4} = I^2 R_4 \Rightarrow P_{R4} = 5 \cdot 5 \cdot 5 = 125 W$$

1.10

$$R_1 = 5 \Omega$$

$$R_2 = 3 \Omega$$

$$R_3 = 2 \Omega$$

$$R_4 = 1 \Omega$$

$$R_5 = 3 \Omega$$

$$R_6 = 3 \Omega$$


$$\text{a) } R_p = ?$$

$$\text{b) } J = ?$$

$$\text{c) } J_3 = ?$$

$$\text{d) } U_{R_4} = ?$$

$$P_{R_5} = ?$$

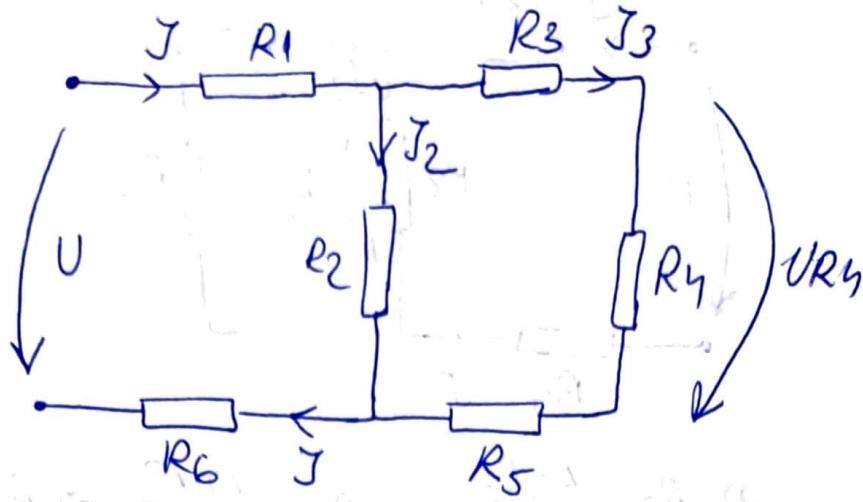

$$\text{a) } R_p = R_3 + R_4 + R_5 \Rightarrow R_p = 6 \Omega$$

$$R_p = \frac{R_3 R_2}{R_3 + R_2} \Rightarrow R_p = \frac{6 \cdot 3}{6 + 3} \Rightarrow R_p = 2 \Omega$$

$$R_p = R_1 + R_p + R_6 \Rightarrow R_p = 10 \Omega$$

$$\text{b) } J = \frac{U}{R_p} \Rightarrow J = \frac{U}{10}$$

$$J = \frac{30}{10} \Rightarrow J = 3 \text{ A}$$

$$\text{c) } 0 = JR_1 + J_2 R_2 + JR_6 - U \Rightarrow J_2 R_2 = U - JR_1 - JR_6$$

$$J_2 = \frac{U - J(R_1 + R_6)}{R_2} \Rightarrow J_2 = \frac{30 - 3(5 + 3)}{3} \Rightarrow J_2 = 2 \text{ A}$$


$$J = J_2 + J_3 \Rightarrow J_3 = J - J_2 \Rightarrow J_3 = 1 \text{ A}$$

$$\text{d) } U_{R_4} = J_3 R_4 \Rightarrow U_{R_4} = 1 \text{ V}$$

$$P_{R_5} = J^2 R_5 \Rightarrow P_{R_5} = 3 \text{ W}$$

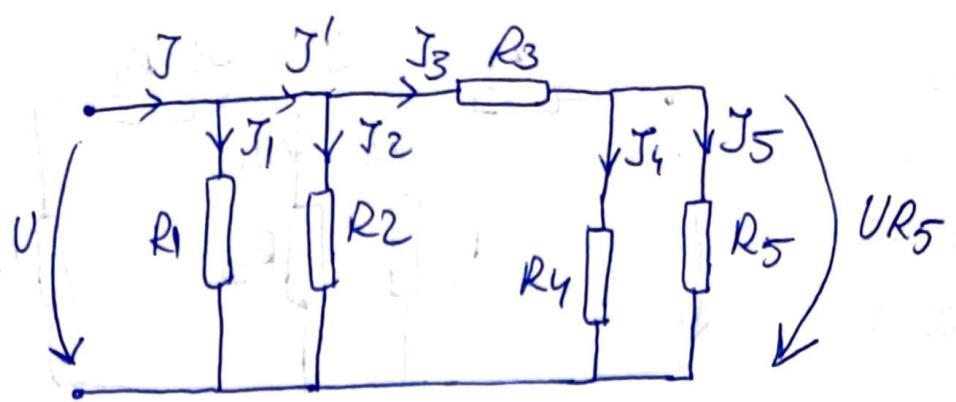1.11

$$\begin{aligned} R_1 &= 60 \Omega \\ R_2 &= 20 \Omega \\ R_3 &= 8 \Omega \\ R_4 &= 3 \Omega \\ R_5 &= 6 \Omega \\ U &= 120V \end{aligned}$$



a) $R_{p1} = \frac{R_4 R_5}{R_4 + R_5} \Rightarrow R_{p1} = \frac{3 \cdot 6}{3+6} \Rightarrow R_{p1} = 2 \Omega$

a) $R_{D1} = R_3 + R_{p1} \Rightarrow R_{D1} = 10 \Omega$

b) $J = ?$

$$R_{p2} = \frac{R_2 \cdot R_{D1}}{R_2 + R_{D1}} \Rightarrow R_{p2} = \frac{20 \cdot 10}{20+10}$$

c) $J_4 = ?$

$$\Rightarrow R_{p2} = \frac{20}{3} \Omega$$

d) $U_{R5} = ?$

$$R_E = \frac{R_1 R_{p2}}{R_1 + R_{p2}} \Rightarrow R_E = \frac{60 \cdot \frac{20}{3}}{60 + \frac{20}{3}} = \frac{20 \cdot 20}{200} = \frac{2}{3} \Omega$$

$$\Rightarrow R_E = 6 \Omega$$

e) $U = J R_E \Rightarrow J = \frac{U}{R_E} \Rightarrow J = \frac{120}{6} = 20A$

c) $U = J_1 R_1 \Rightarrow J_1 = \frac{120}{60} = 2A$

$$J = J_1 + J' \Rightarrow J' = J - J_1 \Rightarrow J' = 18A$$

$$U = J_3 (R_3 + R_{p1}) \Rightarrow J_3 = \frac{U}{R_3 + R_{p1}} \Rightarrow J_3 = \frac{120}{10} \Rightarrow J_3 = 12A$$

$$J' = J_3 + J_2 \Rightarrow J_2 = J' - J_3 \Rightarrow J_2 = 6A$$

$$J_4 R_4 = J_2 R_2 - J_3 R_3 \Rightarrow J_4 = \frac{J_2 R_2 - J_3 R_3}{R_4} \Rightarrow J_4 = \frac{6 \cdot 20 - 12 \cdot 8}{3}$$

$$J_3 = J_4 + J_5 \Rightarrow J_5 = 4A \Rightarrow J_5 = 8A$$

$$U_{R5} = J_5 R_5 \Rightarrow U_{R5} = 24V ; P_{R2} = J_2^2 R_2 \Rightarrow P_{R2} = 420W$$

1.12

$$R_1 = 9\Omega$$

$$R_2 = 60\Omega$$

$$R_3 = 20\Omega$$

$$R_4 = 6\Omega$$

$$R_5 = 4\Omega$$

$$U = 150V$$

a) $R_D = R_4 + R_5 \Rightarrow R_D = 10\Omega$

$$\frac{1}{R_P} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_D}$$

$$\frac{1}{R_P} = \frac{1}{60} + \frac{1}{20} + \frac{1}{10} = \frac{10}{60} \Rightarrow R_P = 6\Omega$$

b) $I = ?$

$$R_E = R_1 + R_P \Rightarrow R_E = 15\Omega$$

c) $I_3 = ?$

$$e) U = IR_E \Rightarrow I = \frac{U}{R_E} \Rightarrow I = \frac{150}{15} \Rightarrow I = 10A$$


$$c) I R_1 + I_2 R_2 - U = 0 \Rightarrow I_2 = \frac{U - I R_1}{R_2} \Rightarrow I_2 = \frac{150 - 10 \cdot 9}{60} \Rightarrow I_2 = 1A$$

$$I_2 R_2 = I_3 R_3 \Rightarrow I_3 = \frac{I_2 R_2}{R_3} \Rightarrow I_3 = \frac{60}{20} \Rightarrow I_3 = 3A$$


$$d) I' = I_3 + I_4 \Rightarrow I_4 = I_1 - I_3 \Rightarrow I_4 = 6A$$

$$U_{R_5} = I_4 R_5 \Rightarrow U_{R_5} = 24V$$
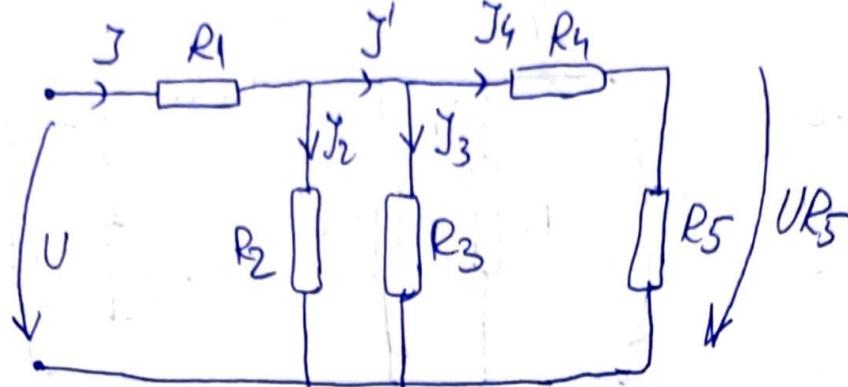
$$P_{R_4} = I_4^2 R_4 \Rightarrow P_{R_4} = 6 \cdot 6 \cdot 6 \Rightarrow P_{R_4} = 216W$$



1.13

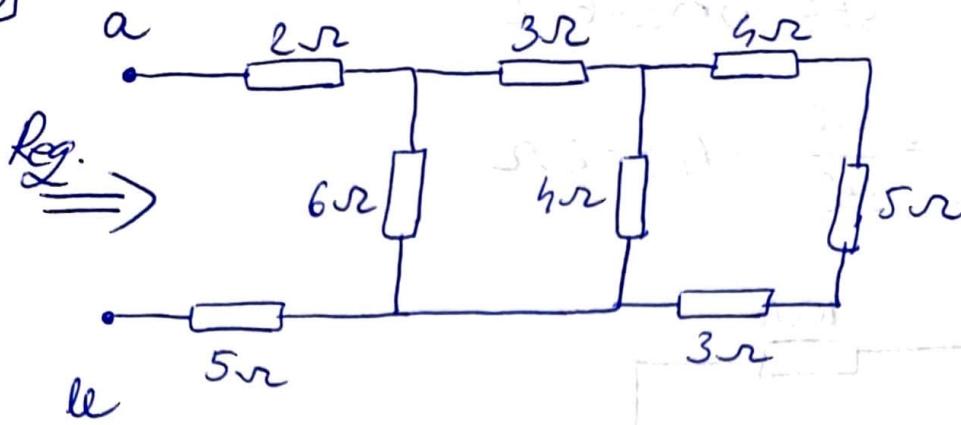

$$R_{S1} = 4 + 5 + 3 \Rightarrow R_{S1} = 12\Omega$$


$$R_{P1} = \frac{4 \cdot R_{S1}}{4+R_{S1}} = \frac{4 \cdot 12}{4+12} = \frac{4 \cdot 12}{16} \Rightarrow R_{P1} = 3\Omega$$

$$R_{S2} = 3 + R_{P1} = 3 + 3 \Rightarrow R_{S2} = 6\Omega$$

$$R_{P2} = \frac{6 \cdot R_{S2}}{6+R_{S2}} = \frac{6 \cdot 6}{6+6} = \frac{6 \cdot 6}{12} \Rightarrow R_{P2} = 3\Omega$$

$$R_{\text{reg}} = 2 + R_{P2} + 5 = 2 + 3 + 5 \Rightarrow R_{\text{reg}} = 10\Omega$$

1.14

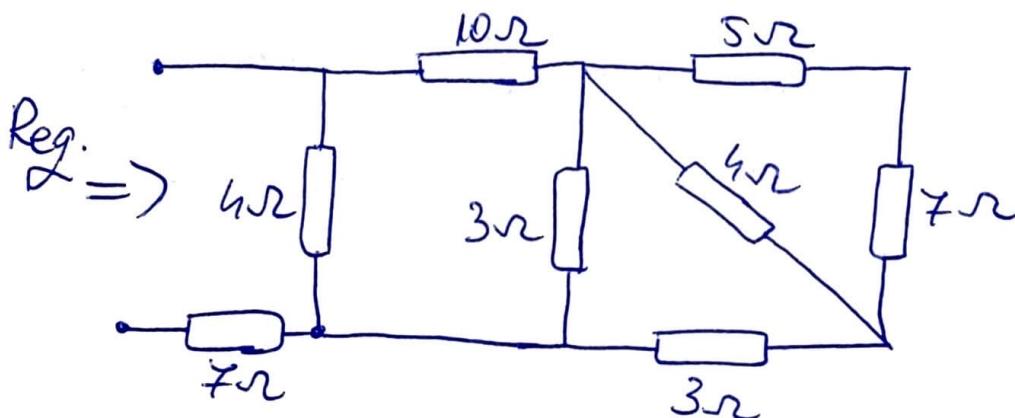


$$R_{S1} = 5 + 4 \Rightarrow R_{S1} = 12\Omega$$

$$R_{P1} = \frac{4 R_{S1}}{4+R_{S1}} = \frac{4 \cdot 12}{4+12} = \frac{4 \cdot 12}{16} \Rightarrow R_{P1} = 3\Omega$$

$$R_{D2} = R_{P1} + 3 = 3 + 3 \Rightarrow R_{D2} = 6\Omega$$
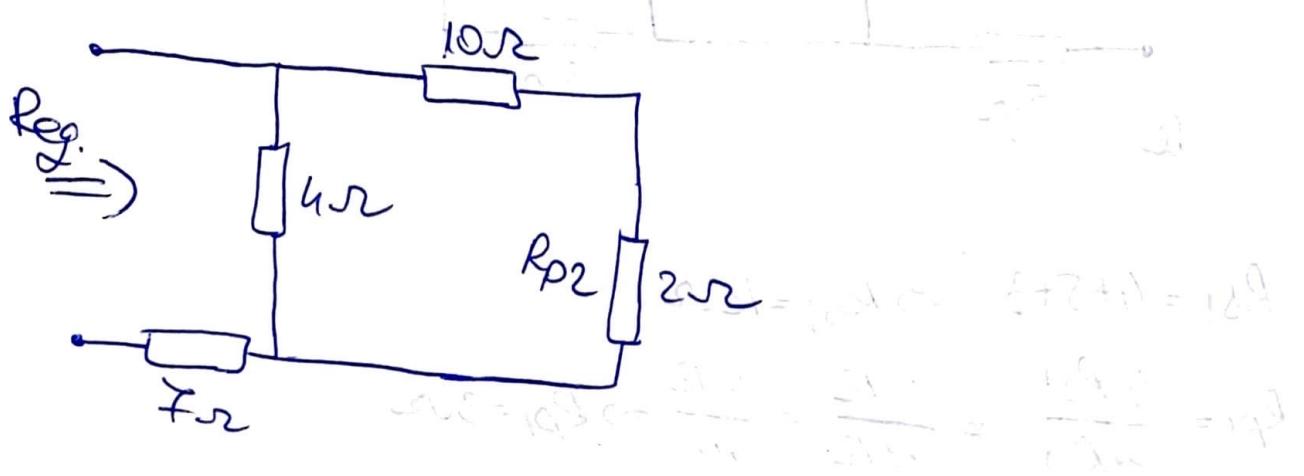
$$R_{P2} = \frac{3R_{D2}}{3+R_{D2}} = \frac{3 \cdot 6}{3+6} \Rightarrow R_{P2} = 2\Omega$$




$$R_{D3} = R_{P2} + 10 \Rightarrow R_{D3} = 12\Omega$$

$$R_{P3} = \frac{4R_{D3}}{4+R_{D3}} = \frac{4 \cdot 12}{4+12} \Rightarrow R_{P3} = 3\Omega$$

$$R_C = R_{P3} + \gamma \Rightarrow R_C = 10\Omega$$

1.15

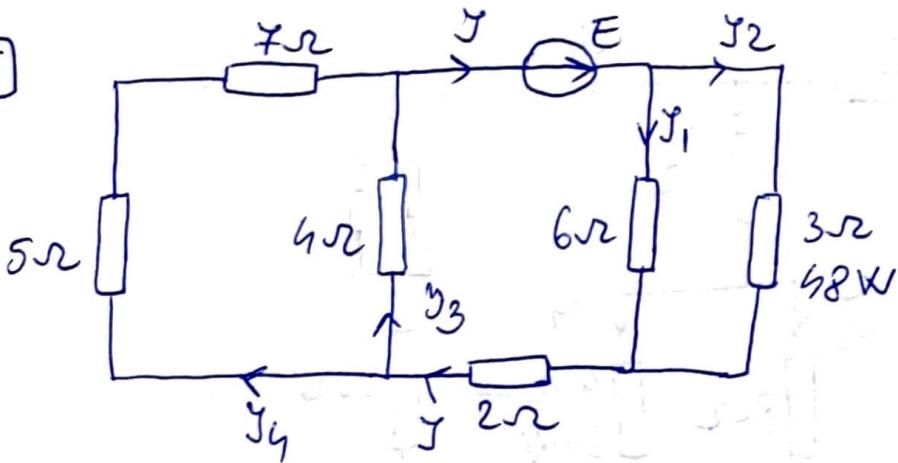

$$48 = J_2^2 \cdot 3 \Rightarrow J_2 = \sqrt{\frac{48}{3}} \Rightarrow J_2 = 4A$$

$$3J_2 = 6J_1 \Rightarrow J_1 = \frac{3J_2}{6} \Rightarrow J_1 = 2A$$

$$J = J_1 + J_2 \Rightarrow J = 6A$$

$$\left\{ \begin{array}{l} J = J_3 + J_4 \\ 4J_3 = 12J_4 \end{array} \right.$$

$$\Rightarrow J_3 = 3J_4$$

$$\Rightarrow J = J_3 + \frac{J_3}{3} / 3$$

$$3J = 3J_3 + J_3 \Rightarrow 3J = 4J_3$$


$$\Rightarrow J_3 = \frac{3J}{4} = \frac{3 \cdot 6}{4}$$

$$J_3 = \frac{9}{2} A$$

$$E = 6J_1 + 2J + 4J_3$$

$$E = 6 \cdot 2 + 2 \cdot 6 + 4 \cdot \frac{9}{2} = 12 + 12 + 18$$

$$\Rightarrow E = 42V$$

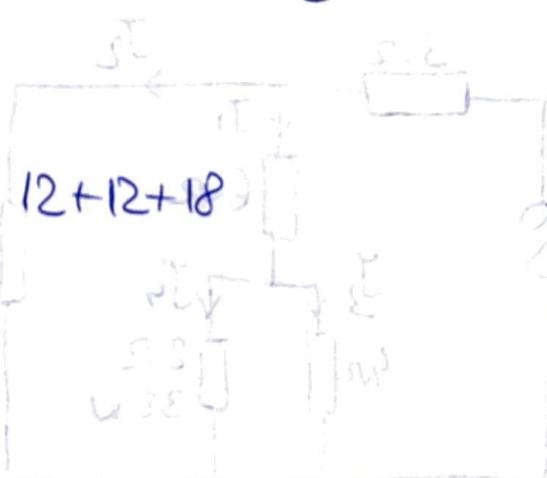


$$I_{16} = I - \frac{R_1 + R_2}{R_1} I$$

$$I_{16} = I - \frac{R_1 + R_2}{R_1} I = 5A - \frac{5 + 3}{5} \cdot 5A = 5A - 8A + 2A = -1A$$

Aus der Gleichung:

1.16

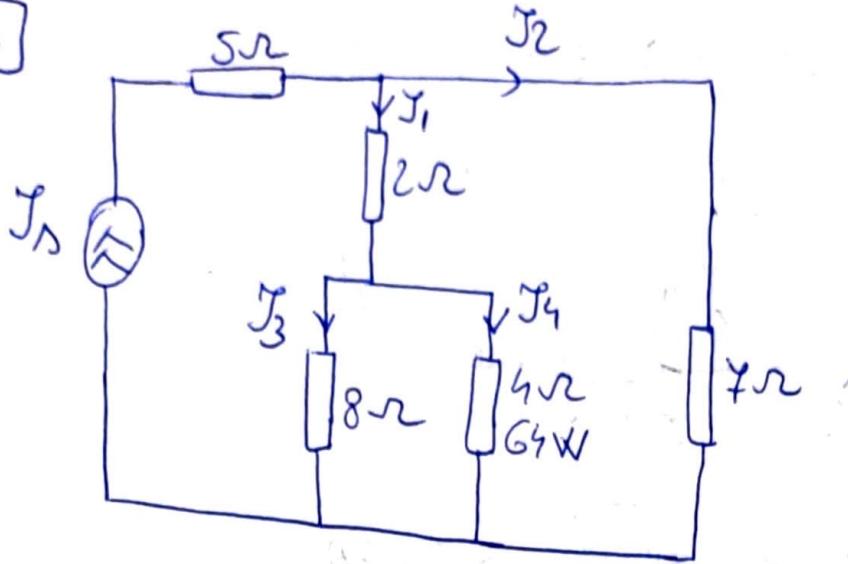

$$64 = J_4^2 \cdot 4 \Rightarrow J_4 = \sqrt{\frac{64}{4}} \Rightarrow J_4 = 4A$$

$$4J_4 = 8J_3 \Rightarrow J_3 = \frac{4J_4}{8} \Rightarrow J_3 = \frac{4 \cdot 4}{8} \Rightarrow J_3 = 2A$$


$$J_1 = J_3 + J_4 \Rightarrow J_1 = 6A$$

$$4J_2 = 4J_4 + 2J_1 \Rightarrow J_2 = \frac{4J_4 + 2J_1}{4}$$

$$J_2 = \frac{4 \cdot 4 + 2 \cdot 6}{4} = \frac{16 + 12}{4} \Rightarrow J_2 = 4A$$

$$J_1 = J_1 + J_2 \Rightarrow J_1 = 10A$$

1.17

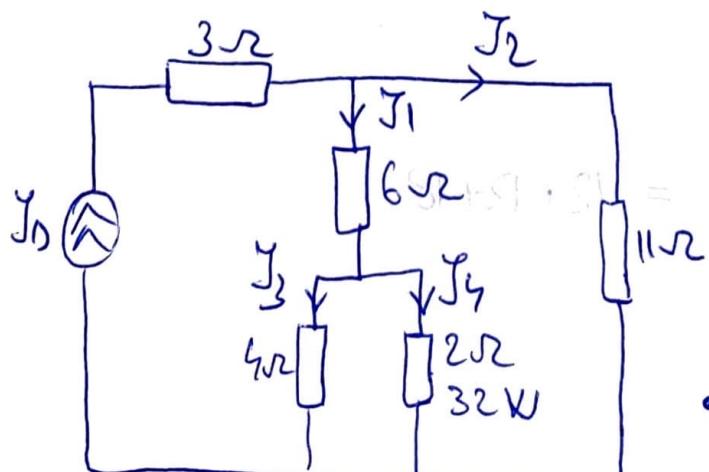

$$\bullet 32 = J_4^2 \cdot 2 \Rightarrow J_4 = \sqrt{\frac{32}{2}} \Rightarrow J_4 = 4A$$

$$\bullet 2J_4 = 4J_3 \Rightarrow J_3 = \frac{2J_4}{4}$$


$$J_3 = \frac{2 \cdot 4}{4} \Rightarrow J_3 = 2A$$

$$\bullet J_1 = J_3 + J_4 \Rightarrow J_1 = 6A$$

$$\bullet 11J_2 = 2J_4 + 6J_1 \Rightarrow J_2 = \frac{2J_4 + 6J_1}{11} \Rightarrow J_2 = 4A$$

$$\bullet J_1 = J_1 + J_2 \Rightarrow J_1 = 10A$$

1.18

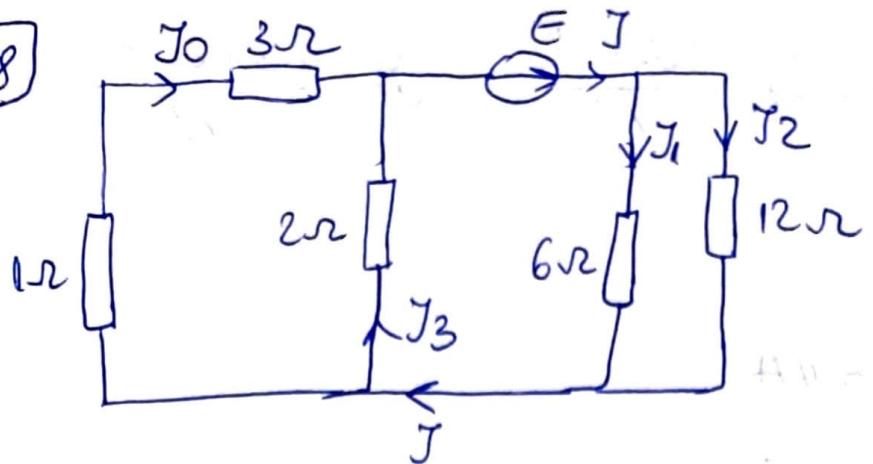


$$J_0 = 4 \text{ A}$$

$$4J_0 = 2J_3 \Rightarrow J_3 = \frac{4J_0}{2} = \Rightarrow J_3 = 8 \text{ A}$$


$$J = J_3 + J_0 \Rightarrow J = 12 \text{ A}$$
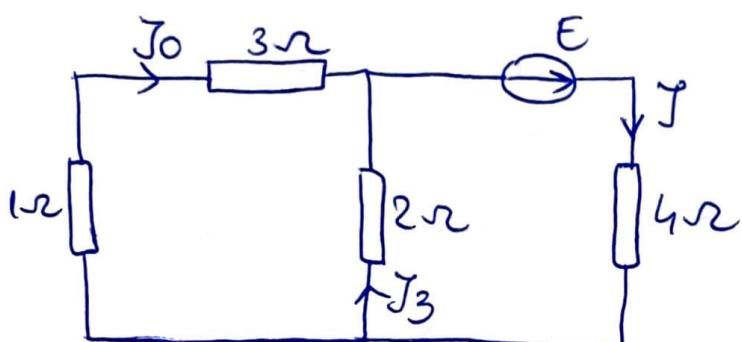
$$R_P = \frac{6 \cdot 12}{6+12} = \frac{6 \cdot 12}{18} \Rightarrow R_P = 4 \Omega$$



$$E = 4J + 2J_3 \Rightarrow E = 4 \cdot 12 + 2 \cdot 8 \Rightarrow E = 64 \text{ V}$$

1.19

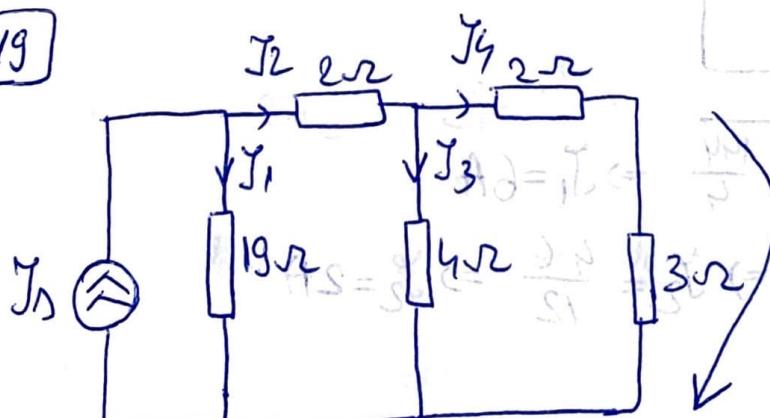

$$12 = 3 \cdot J_4 \Rightarrow J_4 = 4 \text{ A}$$

$$4J_3 = 5J_4 \Rightarrow J_3 = \frac{5J_4}{4} \Rightarrow J_3 = 5 \text{ A}$$

$$J_2 = J_3 + J_4 \Rightarrow J_2 = 9 \text{ A}$$

$$2A + 8A = 10A = 12V \Rightarrow 1A$$


$$V_{AB} = 12V - 12V = 0$$

$$19J_1 = 4J_3 + 2J_2 \Rightarrow J_1 = \frac{4J_3 + 2J_2}{19} \Rightarrow J_1 = \frac{4 \cdot 5 + 2 \cdot 9}{19}$$

$$\Rightarrow J_1 = 2A$$


$$J_3 = J_1 + J_2 \Rightarrow J_3 = 11A$$

1.20

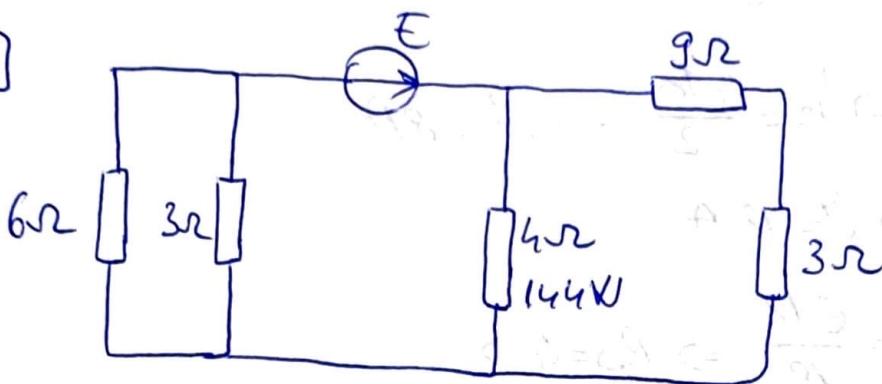

$$R_P = \frac{6 \cdot 3}{6+3} \Rightarrow R_P = 2\Omega$$
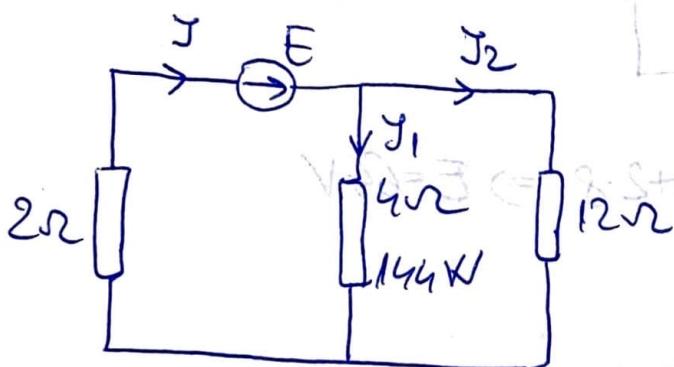
$$R_D = 9 + 3 \Rightarrow R_D = 12\Omega$$



$$144 = J_1^2 \cdot 4 \Rightarrow J_1 = \sqrt{\frac{144}{4}} \Rightarrow J_1 = 6A$$


$$12J_2 = 4J_1 \Rightarrow J_2 = \frac{4J_1}{12} \Rightarrow J_2 = \frac{4 \cdot 6}{12} \Rightarrow J_2 = 2A$$

$$J = J_1 + J_2 \Rightarrow J = 8A$$

$$E = 2J + 4J_1 = 2 \cdot 8 + 4 \cdot 6$$


$$\Rightarrow E = 40V$$

1.21

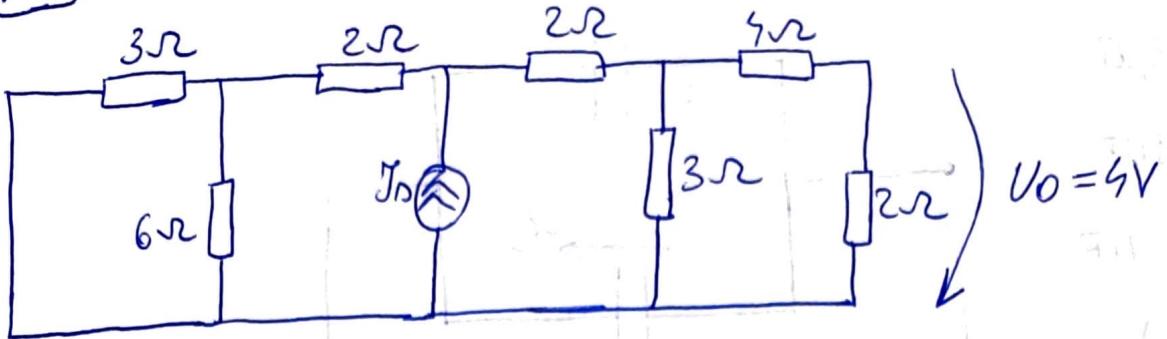

$$R_P = \frac{3 \cdot 6}{3+6} \Rightarrow R_P = 2\Omega$$
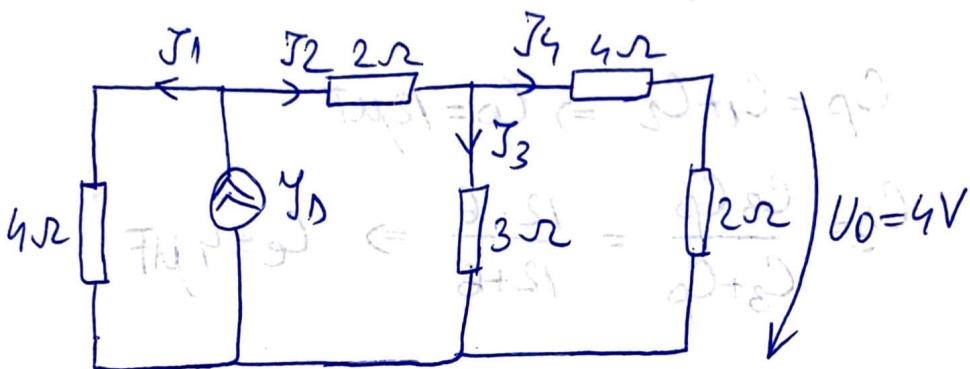
$$R_S = R_P + 2 \Rightarrow R_S = 4\Omega$$



$$\gamma = 2J_4 \Rightarrow J_4 = 2A$$

$$3J_3 = 6J_4 \Rightarrow J_3 = \frac{6J_4}{3} \Rightarrow J_3 = 4A$$

$$J_2 = J_3 + J_4 \Rightarrow J_2 = 6A$$

$$4J_1 = 3J_3 + 2J_2 \Rightarrow J_1 = \frac{3J_3 + 2J_2}{4}$$

$$J_1 = \frac{3 \cdot 4 + 2 \cdot 6}{4} = \frac{12 + 12}{4} = 6A$$

$$J_D = J_1 + J_2 \Rightarrow J_D = 12A$$

$$I_{D1} = 0.2 \text{ A} \quad I_{D2} = 0.2 \text{ A} \quad I_{D3} = 0.2 \text{ A}$$

$$P_{D1} = 0.2 \cdot 0.2 \cdot \frac{1}{2} = 0.02W \quad P_{D2} = 0.2 \cdot 0.2 \cdot \frac{1}{2} = 0.02W \quad P_{D3} = 0.2 \cdot 0.2 \cdot \frac{1}{2} = 0.02W$$

$$P_{D1} = 0.02W \quad P_{D2} = 0.02W \quad P_{D3} = 0.02W$$

$$P_{D1} = 0.02W \quad P_{D2} = 0.02W \quad P_{D3} = 0.02W$$

1.22

$$C_1 = 3 \mu F$$

$$C_2 = 9 \mu F$$

$$C_3 = 6 \mu F$$

$$U = 60 V$$


a) $C_e = ?$

b) $Q_e = ?$


c) $U_{C_2} = ?$

d) $Q_1 = ?$

e) $W_{C_3} = ?$

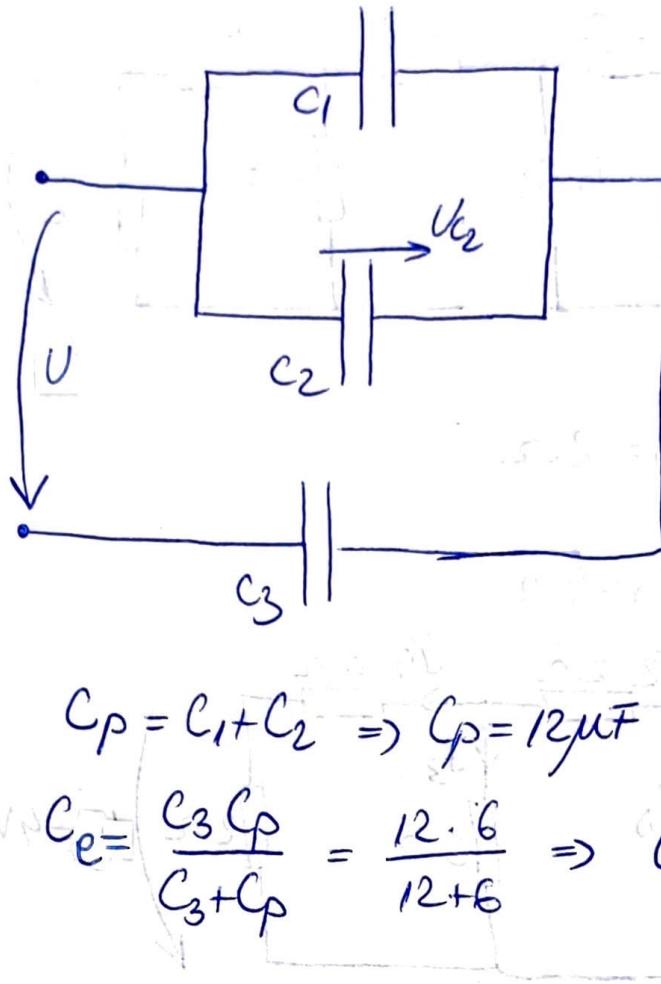

f)

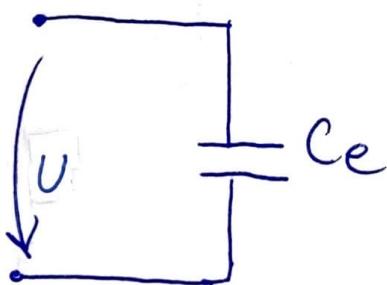

$$Q_e = C_e \cdot U$$

$$Q_e = 4 \cdot 60 \Rightarrow Q_e = 240 \mu C$$

c) $U_{C_2} = U_{C_1} = U_{C_P} = \frac{Q_e}{C_P} = \frac{240}{12} = 20 V$

d) $Q_1 = U_{C_1} \cdot C_1 = 20 \cdot 3 = 60 \mu C$

e) $W_{C_3} = \frac{1}{2} \cdot Q_3 \cdot U_{C_3}$

$$Q_3 = Q_e = 240 \mu C$$

$$U_{C_3} = \frac{Q_3}{C_3} = \frac{240}{6} = 40 V$$

$$\Rightarrow W_{C_3} = \frac{1}{2} \cdot 240 \cdot 40$$

$$W_{C_3} = 4800 \mu J$$

J.23

$$C_1 = 12 \mu F$$

$$C_2 = 6 \mu F$$

$$C_3 = 1 \mu F$$

$$C_4 = 5 \mu F$$

$$U = 24 V$$


a) $C_e = ?$

b) $Q_e = ?$

c) $U_{C2} = ?$

d) $Q_4 = ?$

e) $W_{C3} = ?$

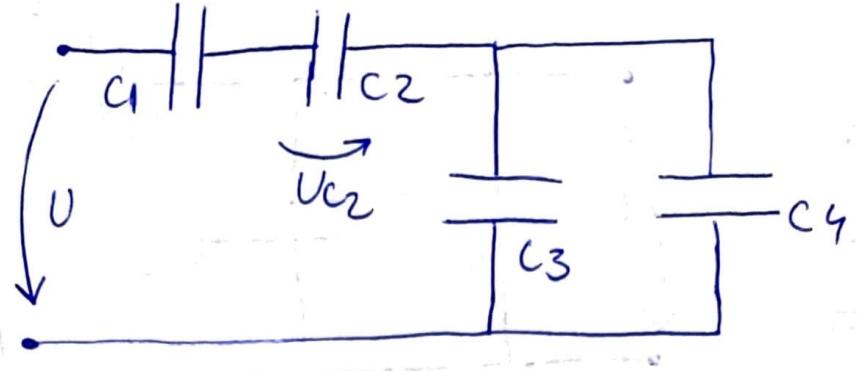

a) $C_p = C_3 + C_4 \Rightarrow C_p = 6 \mu F$

$$\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_p}$$

$$\frac{1}{C_e} = \frac{1}{12} + \frac{1}{4} + \frac{1}{6} \Rightarrow C_e = 2 \mu F$$

b) $Q_e = C_e \cdot U \Rightarrow Q_e = 2 \cdot 24 \Rightarrow Q_e = 48 \mu C$

c) $Q_1 = Q_2 = Q_3 = U \left(\frac{C_1 C_2}{C_1 + C_2} \right) = 24 \cdot 3 = 72 \mu C$

$$U_{C2} = \frac{Q_2}{C_2} = \frac{72}{4} = 18 V$$

d) $Q_4 = C_4 \cdot U \Rightarrow Q_4 = 5 \cdot 24 \Rightarrow Q_4 = 120 \mu C$

e) $W_{C3} = \frac{1}{2} \cdot Q_3 \cdot U_{C3}$

$$U_{C3} = U_{C4} \Rightarrow \frac{Q_3}{C_3} = \frac{Q_4}{C_4} \Rightarrow Q_3 = \frac{1 \cdot 120}{5} \Rightarrow Q_3 = 24 \mu C$$

$$U_{C3} = 24 V$$

$| W_{C3} = 288 \mu J$

U.24

$$C_1 = 5 \mu F$$

$$C_2 = 4 \mu F$$

$$C_3 = 12 \mu F$$

$$C_4 = 4 \mu F$$

$$U = 20 V$$


a) $C_e = ?$

b) $Q_e = ?$

c) $U_{C_3} = ?$

d) $Q_1 = ?$

e) $W_{C_4} = ?$

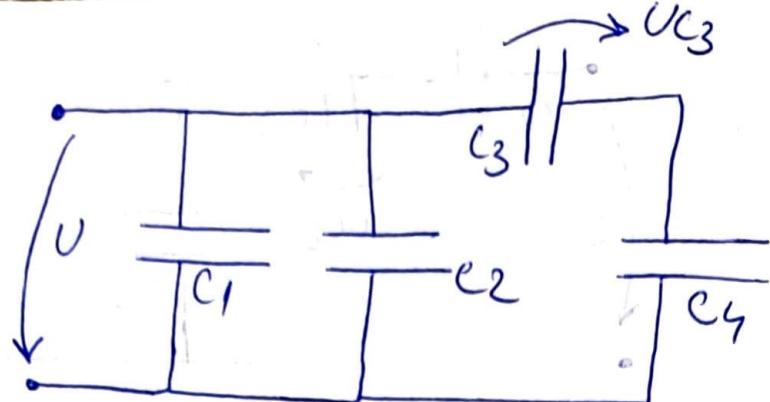

a) $C_s = \frac{C_3 C_4}{C_3 + C_4} \Rightarrow C_s = \frac{12 \cdot 4}{12 + 4} = 3 \mu F$

$C_{p1} = C_s + C_2 \Rightarrow C_{p1} = 10 \mu F$

$C_e = C_{p1} + C_1 \Rightarrow C_e = 15 \mu F$

b) $Q_e = C_e \cdot U = 15 \cdot 20 \Rightarrow Q_e = 300 \mu C$

c) $Q_3 = Q_4 = U \cdot C_s = 60 \mu C$

$$U_{C_3} = \frac{Q_3}{C_3} = \frac{60}{12} = 5 V$$

d) $U_{C_1} = U_{C_2} = \frac{Q_e}{C_1 + C_2} = 25 V$

$$U_{C_1} = \frac{Q_1}{C_1} \Rightarrow Q_1 = U_{C_1} \cdot C_1 \Rightarrow Q_1 = 125 \mu C$$

e) $W_{C_4} = \frac{1}{2} \cdot Q_4 \cdot U_{C_4} = \frac{1}{2} \cdot Q_4 \cdot \frac{Q_4}{C_4} = \frac{1}{2} \cdot 60 \cdot \frac{60}{4}$

$$W_{C_4} = 450 \mu J$$

2.1

$$R_1 = 5 \Omega$$

$$R_2 = 10 \Omega$$

$$R_3 = 6 \Omega$$

$$R_4 = 3 \Omega$$

$$R_5 = 2 \Omega$$

$$E_1 = 10V$$

$$E_2 = 5V$$


$$E_5 = 5V$$

a) currents using KL

b) currents using nodal analysis

c) currents using mesh analysis

d) verify power conservation theorem

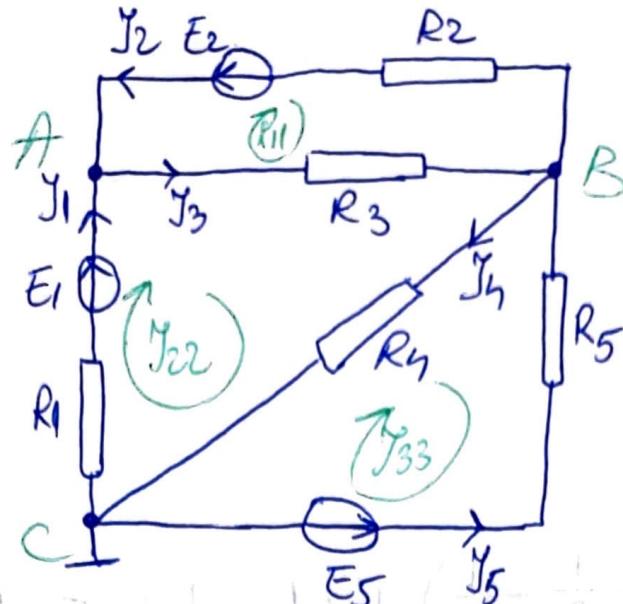

nodes: 3

branches: 5

$$\begin{cases} J_3 = J_1 + J_2 \\ J_4 = J_1 + J_5 \end{cases}$$

$$\begin{cases} E_1 = J_1 R_1 + J_3 R_3 + J_4 R_4 \\ E_2 = J_2 R_2 + J_3 R_3 \\ E_5 = J_5 R_5 + J_4 R_4 \end{cases} \Rightarrow \begin{cases} 10 = 5J_1 + 6J_3 + 3J_4 \\ 5 = 10J_2 + 6J_3 \\ 5 = 2J_5 + 3J_4 \end{cases}$$

$$\begin{cases} J_3 = J_1 + J_2 \\ J_4 = J_1 + J_5 \\ 10 = 5J_1 + 6J_3 + 3J_4 \\ 5 = 10J_2 + 6J_3 \\ 5 = 2J_5 + 3J_4 \end{cases} \Rightarrow \begin{cases} 10 = 5(1-J_5) + 6(1+J_1+J_2) + 3(1+J_1+J_5) \\ 5 = 10J_2 + 6(1+J_1+J_2) \\ 5 = 2J_5 + 3(1+J_1+J_5) \end{cases}$$

$$\Rightarrow \begin{cases} 10 = 5(1-J_5) + 6(1+J_1+J_2) + 3(1+J_1+J_5) \\ 5 = 10J_2 + 6(1+J_1+J_2) \\ 5 = 2J_5 + 3(1+J_1+J_5) \end{cases} \Rightarrow \begin{cases} 10 = 14J_1 + 6J_2 + 3J_5 \\ 5 = 16J_2 + 6J_1 \\ 5 = 5J_5 + 3J_1 \end{cases}$$

$$J_1 = \frac{5(1-J_5)}{3} ; J_2 = \frac{5-10(1-J_5)}{16} ; J_5 = 0,69A$$

$$J_1 = 0.51 \text{ A}$$

$$J_2 = 0.11 \text{ A}$$

$$J_3 = 0.62 \text{ A}$$

$$J_4 = 1.2 \text{ A}$$

$$(k) \quad A: V_A \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_B \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = E_1 \cdot \frac{1}{R_1} + E_2 \cdot \frac{1}{R_2}$$

$$B: V_B \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) - V_A \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = -E_2 \frac{1}{R_2} + E_5 \frac{1}{R_5}$$

$$\left\{ \begin{array}{l} V_A \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{6} \right) - V_B \left(\frac{1}{10} + \frac{1}{6} \right) = 10 \frac{1}{5} + 5 \frac{1}{10} \\ V_B \left(\frac{1}{10} + \frac{1}{6} + \frac{1}{3} + \frac{1}{2} \right) - V_A \left(\frac{1}{10} + \frac{1}{6} \right) = -5 \cdot \frac{1}{10} + 5 \cdot \frac{1}{2} \end{array} \right.$$

$$V_A = \frac{2955}{398} = 7.42 \text{ V}$$

$$V_B = \frac{420}{199} = 3.61 \text{ V}$$

$$V_A - V_C = E_1 - J_1 R_1 \Leftrightarrow V_A = E_1 - J_1 R_1 \Rightarrow J_1 = 0.51 \text{ A}$$

$$V_B - V_C = E_5 - J_5 R_5 \Leftrightarrow V_B = E_5 - J_5 R_5 \Rightarrow J_5 = 0.69 \text{ A}$$

$$V_B - V_A = J_4 R_4 \Leftrightarrow V_B = J_4 R_4 \Rightarrow J_4 = 1.2 \text{ A}$$

$$V_B - V_A = -E_2 + J_2 R_2 \Rightarrow J_2 = 0.11 \text{ A}$$

$$V_A - V_B = J_3 R_3 \Rightarrow J_3 = 0.62 \text{ A}$$

$$c) \quad J_1 = J_{22}$$

$$J_2 = -J_{11}$$

$$J_3 = J_{22} - J_{11}$$

$$J_4 = J_{22} - J_{33}$$

$$J_5 = -J_{33}$$

$$\text{mesh 1: } (R_2 + R_3)J_{11} - R_3 J_{22} = -E_2$$

$$\text{mesh 2: } (R_1 + R_3 + R_4)J_{22} - R_3 J_{11} - R_4 J_{33} = E_1$$

$$\text{mesh 3: } (R_4 + R_5)J_{33} - R_4 J_{22} = -E_5$$

$$\begin{cases} 16J_{11} - 6J_{22} = -5 \\ 14J_{22} - 6J_{11} - 3J_{33} = 10 \\ 5J_{33} - 3J_{22} = -5 \end{cases} \Rightarrow$$

$$J_{11} = -\frac{95}{496} = -0.11 \text{ A}$$

$$J_{22} = \frac{205}{398} = 0.51 \text{ A}$$

$$J_{33} = -\frac{245}{398} = -0.69 \text{ A}$$

$$J_1 = 0.51 \text{ A}$$

$$J_2 = 0.11 \text{ A}$$

$$J_3 = 0.62 \text{ A}$$

$$J_4 = 1.2 \text{ A}$$

$$J_5 = 0.69 \text{ A}$$

$$d) \quad P_f = E_1 \cdot J_1 + E_2 \cdot J_2 + E_5 J_5 = 9.1 \text{ W}$$

$$P_r = J_1^2 R_1 + J_2^2 R_2 + J_3^2 R_3 + J_4^2 R_4 + J_5^2 R_5$$

2.2

$$R_1 = 2 \Omega$$

$$R_2 = 2 \Omega$$

$$R_3 = 6 \Omega$$

$$R_4 = 2 \Omega$$

$$E_1 = 12V$$

$$E_3 = 6V$$


$$Y_5 = 4A$$

a) currents:
~~KCL~~

b) nodal analysis

c) mesh analysis

d) verify power
 cons. theorem

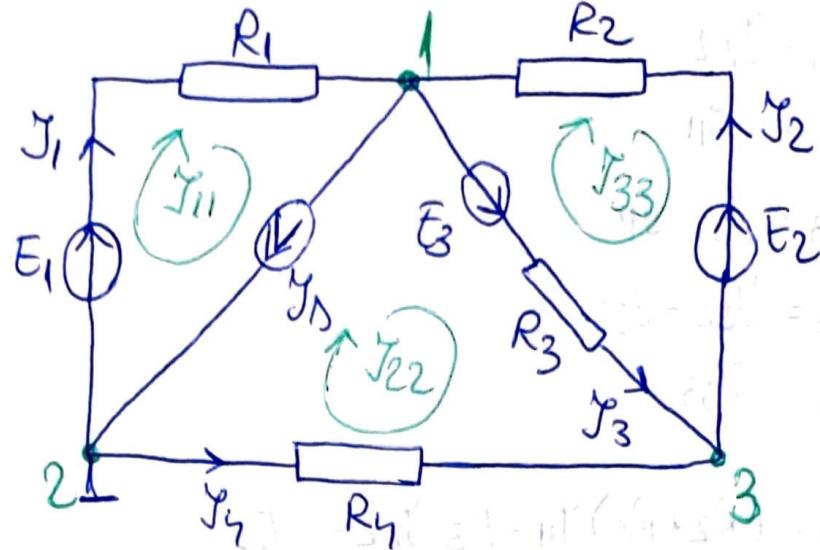

$$\left. \begin{array}{l} Y_1 + Y_2 = 4 + Y_3 \\ Y_1 + Y_4 = 4 \\ Y_2 = Y_3 + Y_4 \end{array} \right\}$$

$$E_1 = Y_1 R_1 \Rightarrow Y_1 = 6A$$

$$E_3 = Y_3 R_3 - Y_4 R_4$$

$$E_2 + E_3 = Y_2 R_2 + Y_3 R_3$$

$$\left. \begin{array}{l} 6 + Y_2 = 4 + Y_3 \\ 6 + Y_4 = 4 \\ Y_2 = Y_3 + Y_4 \end{array} \right\} \Rightarrow Y_4 = -2A$$

$$Y_2 = -1.7A$$

$$Y_3 = 0.3A$$

$$E_2 = -7.6V$$

e) Node 2 is the ground $\Rightarrow V_2 = 0V$

$$\text{node 1: } V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_3 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = E_1 \cdot \frac{1}{R_1} - E_3 \cdot \frac{1}{R_3} + E_2 \cdot \frac{1}{R_2} - Y_1$$

$$\text{node 3: } V_3 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - V_1 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = E_3 \cdot \frac{1}{R_3} - E_2 \cdot \frac{1}{R_2}$$

$$\begin{cases} V_1\left(\frac{1}{2} + \frac{1}{2} + \frac{1}{6}\right) - V_3\left(\frac{1}{2} + \frac{1}{6}\right) = 12 \cdot \frac{1}{2} - 6 \cdot \frac{1}{6} - 4,6 \cdot \frac{1}{2} - 4 \\ V_3\left(\frac{1}{2} + \frac{1}{6} + \frac{1}{2}\right) - V_1\left(\frac{1}{2} + \frac{1}{6}\right) = 6 \cdot \frac{1}{6} + 4,6 \cdot \frac{1}{2} \end{cases}$$

$$V_1 = -\frac{36}{47} = -0,76 \text{ V}$$

$$V_2 = \frac{6 \cdot 2}{235} = 2,85 \text{ V}$$

$$V_1 = E_1 - J_1 R_1 \Rightarrow J_1 = 6 \text{ A}$$

$$V_3 - V_1 = J_2 R_2 - E_2 \Rightarrow J_2 = -1,4 \text{ A}$$

$$V_1 - V_3 = J_3 R_3 - E_3 \Rightarrow J_3 = 0,3 \text{ A}$$

$$V_3 - V_2 = -J_4 R_4 \Rightarrow J_4 = -2 \text{ A}$$

$$c) J_1 = J_{11}$$

$$J_2 = J_{33}$$

$$J_3 = J_{22}$$

$$J_4 = J_{33} - J_{22}$$

$$J_1 R_1 = E_1 \Rightarrow J_{11} R_1 = E_1 \Rightarrow J_{11} = 6 \text{ A} \Rightarrow J_1 = 6 \text{ A}$$

$$J_4 R_4 - J_3 R_3 = -E_3 \Rightarrow J_{22} \cdot 2 - (J_{33} - J_{22}) \cdot 6 = -6$$

$$J_3 R_3 + J_2 R_2 = E_2 + E_3 \Rightarrow (J_{33} - J_{22}) \cdot 6 + J_{22} \cdot 2 = 6 - 4,6$$

$$\Rightarrow 8J_{22} - 6J_{33} = -6$$

$$J_2 = -1,4 \text{ A}$$

$$J_3 = 0,3 \text{ A}$$

$$\Rightarrow 8J_{33} - 6J_{22} = 1,6$$

$$J_2 = -2 \text{ A}$$

2.3

$$R_1 = 2 \Omega$$

$$R_2 = 2 \Omega$$

$$R_3 = 6 \Omega$$

$$R_4 = 2 \Omega$$


$$E_1 = 12V$$

$$E_3 = 6V$$

$$E_5 = 10V$$

currents:

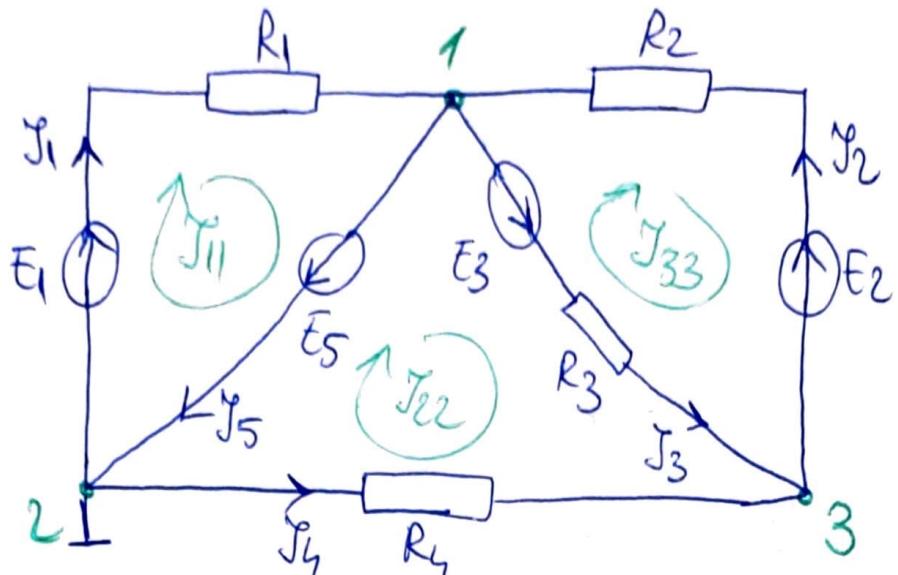- a) KL
- b) nodal analysis
- c) mesh analysis
- d) verify power conservation theorem



$$\left. \begin{array}{l} J_1 + J_2 = J_3 + J_5 \\ J_5 = J_1 + J_4 \\ J_2 = J_3 + J_4 \end{array} \right\}$$

$$\bullet E_1 + E_5 = J_1 R_1 \Rightarrow J_1 = 11A$$

$$\bullet E_3 - E_5 = J_3 R_3 - J_4 R_4 \Rightarrow$$

$$\Rightarrow -4 = 6J_3 - 2J_4 \Rightarrow J_3 = \frac{2J_4 - 4}{6}$$

$$\bullet E_3 + E_2 = J_2 R_2 + J_3 R_3$$

$$\bullet E_1 - E_2 = J_1 R_1 - J_2 R_2 - J_4 R_4$$

$$\bullet E_1 + E_3 = J_1 R_1 + J_3 R_3 - J_4 R_4$$

$$\left. \begin{array}{l} 11 + J_2 = \frac{2J_4 - 4}{6} + J_5 \\ J_5 = 11 + J_4 \\ J_2 = \frac{2J_4 - 4}{6} + J_4 \end{array} \right\}$$


$$11 + J_2 = \frac{2J_4 - 4}{6} + 11 + J_4$$

$$J_2 = \frac{2J_4 - 4}{6} + J_4$$

Not enough equations.

2.4

$$y_1 = ? \quad y_2 = ? \quad y_3 = ?$$

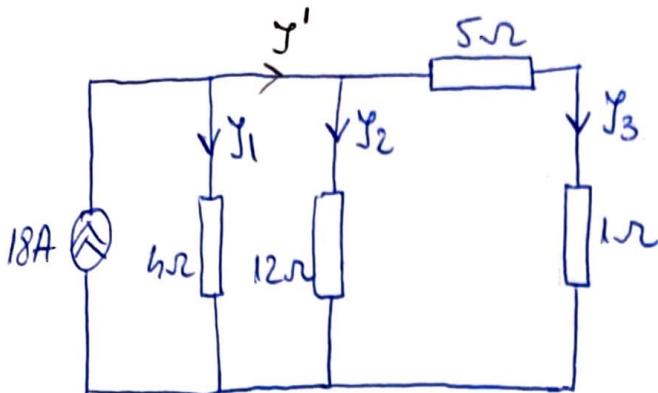

verify power
cons. theorem

$$y_s = y_1 + y' \Rightarrow \begin{cases} y_1 + y' = 18 \\ y' = y_2 + y_3 \end{cases}$$

$$12y_2 = 6y_3 \Rightarrow y_3 = 2y_2$$

$$\begin{cases} y_1 + y' = 18 \\ y' = 3y_2 \end{cases}$$

$$y_1 = 12y_2 \Rightarrow y_1 = 3y_2$$

$$\begin{cases} 3y_2 + y' = 18 \\ y' = 3y_2 \end{cases} \Rightarrow 6y_2 = 18 \Rightarrow y_2 = 3A$$

$$y' = 9A$$

$$y_1 + 9 = 18 \Rightarrow y_1 = 9A$$

$$y_3 = 6A$$


$$\frac{1}{R_e} = \frac{1}{6} + \frac{1}{12} + \frac{1}{5+1} \Rightarrow R_e = 2\Omega$$

$$P_g = y_s^2 \cdot R_e = 18^2 \cdot 2 \Rightarrow P_g = 648W$$

$$P_r = y_1^2 R_1 + y_2^2 R_2 + y_3^2 (R_3 + R_4) \Rightarrow P_r = 648W$$

$$\Rightarrow P_g = P_r$$

2.5

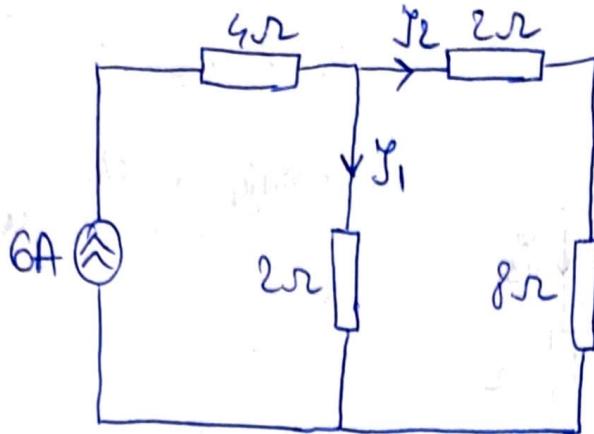


$$\mathfrak{Y}_1 + \mathfrak{Y}_2 = 6$$

$$2\mathfrak{Y}_1 = 10\mathfrak{Y}_2 \Rightarrow \mathfrak{Y}_1 = 5\mathfrak{Y}_2$$

$$5\mathfrak{Y}_2 + \mathfrak{Y}_2 = 6 \Rightarrow \mathfrak{Y}_2 = 1A$$

$$P_{8\Omega} = \mathfrak{Y}_2^2 \cdot 8 \Rightarrow P_{8\Omega} = 8W$$

2.6

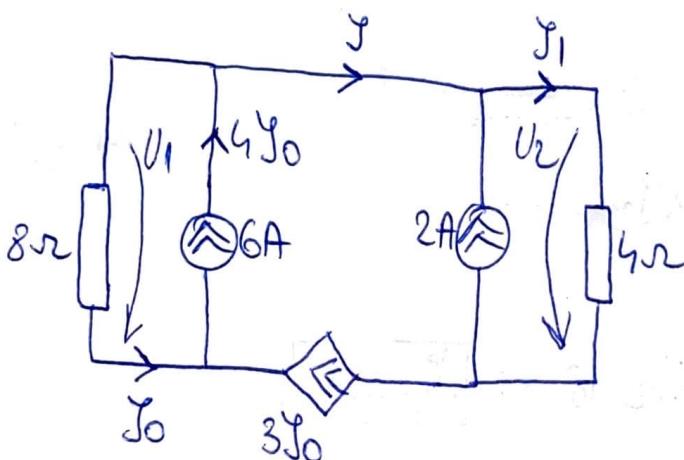

$$\mathfrak{Y}_0 + 3\mathfrak{Y}_0 = 4\mathfrak{Y}_0$$

$$4\mathfrak{Y}_0 = 6A \Rightarrow \boxed{\mathfrak{Y}_0 = 1.5A}$$

$$4\mathfrak{Y}_0 = \mathfrak{Y}_0 + \mathfrak{Y} \Rightarrow 3\mathfrak{Y}_0 = \mathfrak{Y} \Rightarrow \boxed{\mathfrak{Y} = 4.5A}$$


$$\mathfrak{Y}_1 = \mathfrak{Y} + 2 \Rightarrow \boxed{\mathfrak{Y}_1 = 6.5A}$$

$$P_R = \mathfrak{Y}_0^2 \cdot 8 + \mathfrak{Y}_1^2 \cdot 4 = 18W$$

$$P_g = 6U_1 + 2U_2 + 4.5(U_2 - U_1) = 18W \quad \left. \right\} \Rightarrow P_R = P_g$$

$$U_1 = \mathfrak{Y}_0 \cdot 8 = 12V; \quad U_2 = \mathfrak{Y}_1 \cdot 4 = 26V$$

2.7

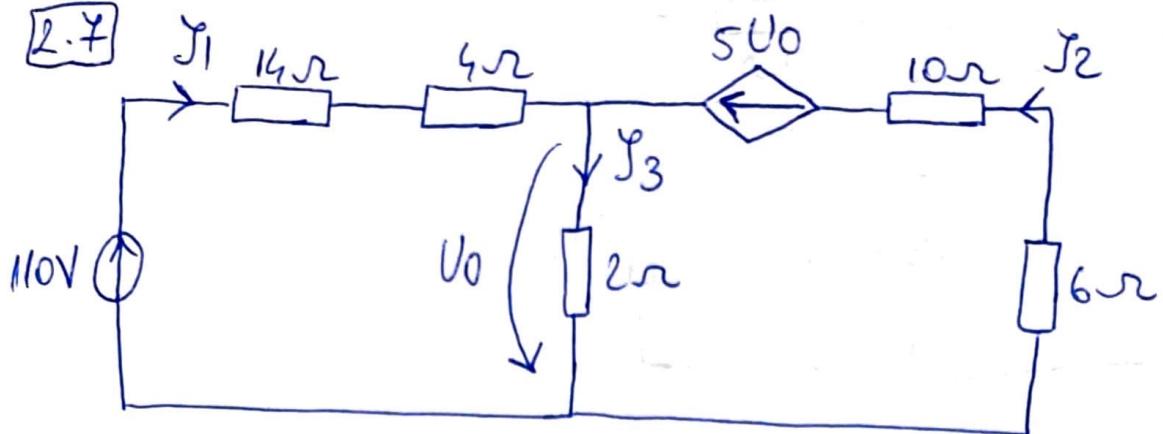

$$Y_3 = Y_1 + Y_2$$

$$110 = 18Y_1 + 2Y_3 \quad \text{so} \quad 110 = 18Y_1 + U_0$$

$$5U_0 = 16Y_2 + 2Y_3 \quad \text{so} \quad 5U_0 = 16Y_2 + U_0 \Rightarrow 4U_0 = 16Y_2 \Rightarrow U_0 = 4Y_2$$

$$110 = 18Y_1 + 4Y_2$$

$$Y_3 = Y_1 + Y_2$$

$$110 = 18Y_1 + 2Y_3$$

$$18Y_1 + 4Y_2 = 18Y_1 + 2Y_3 \Rightarrow Y_3 = 2Y_2$$

$$2Y_2 = Y_1 + Y_2 \Rightarrow Y_1 = Y_2$$

$$110 = 18Y_2 + 4Y_2 \Rightarrow 110 = 22Y_2 \Rightarrow Y_2 = 5A$$

$$Y_1 = 5A$$


$$Y_3 = 10A$$

$$U_0 = 20V$$

$$P_g = 110Y_1 + 5 \cdot U_0 \cdot Y_2 = 1050W$$

$$P_r = Y_1^2 \cdot 18 + Y_3^2 \cdot 2 + Y_2^2 \cdot 16 = 1050W \quad \left. \right\} \Rightarrow P_g = P_r$$

[29]

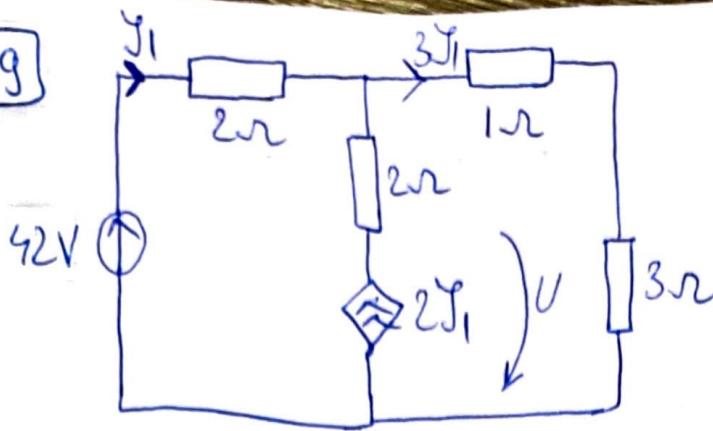

$$J_1 + 2J_1 = 3J_1$$

$$42 = 2J_1 + 3J_1 + 3J_1 \cdot 3$$

$$42 = 14J_1 \Rightarrow J_1 = 3A$$


$$U = 3J_1 + 3J_1 \cdot 3 + 4J_1$$

$$U = 16J_1 \Rightarrow U = 48V$$

$$P_g = 42 \cdot J_1 + U \cdot 2J_1 = 414W$$

$$P_r = J_1^2 \cdot 2 + (2J_1)^2 \cdot 2 + (3J_1)^2 \cdot 4 = 414W \quad \} \Rightarrow P_g = P_r$$

[2.8]

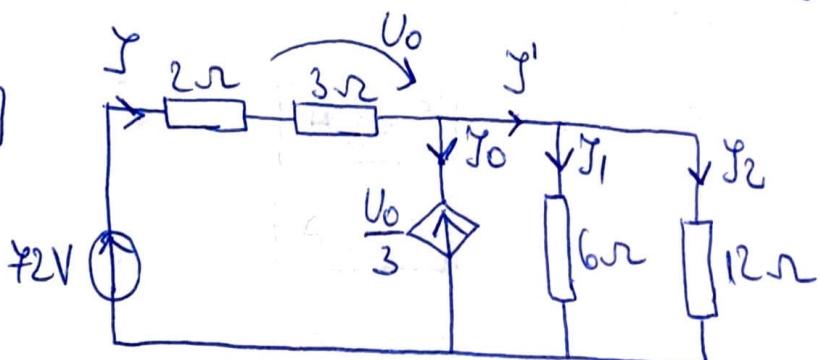

$$\begin{aligned} J &= J_0 + J' \\ J' &= J_1 + J_2 \end{aligned} \quad \} \Rightarrow J = J_0 + J_1 + J_2$$

$$U_0 = 3J$$

$$42 = 2J + U_0 + \frac{U_0}{3} \Rightarrow 42 = 2J + 3J + \frac{3J}{3} \Rightarrow 42 = 6J$$

$$\Rightarrow J = 12A$$

$$6Y_1 = 12Y_2 \Rightarrow Y_1 = 2Y_2$$

$$\frac{U_0}{3} = 6Y_1 \Rightarrow Y = 6Y_1 \Rightarrow Y_1 = 2A$$


$$Y_2 = 1A$$

$$Y_0 = 9A$$

$$P_g = \varphi_2 Y + \frac{U_0}{3} \cdot Y_0 = \varphi_2 \cdot 12 + 12 \cdot 9 = 9\varphi_2 W$$

$$P_r = \varphi^2 \cdot 5 + Y_1 \cdot 6 + Y_2 \cdot 12 = 756 W$$

2.10

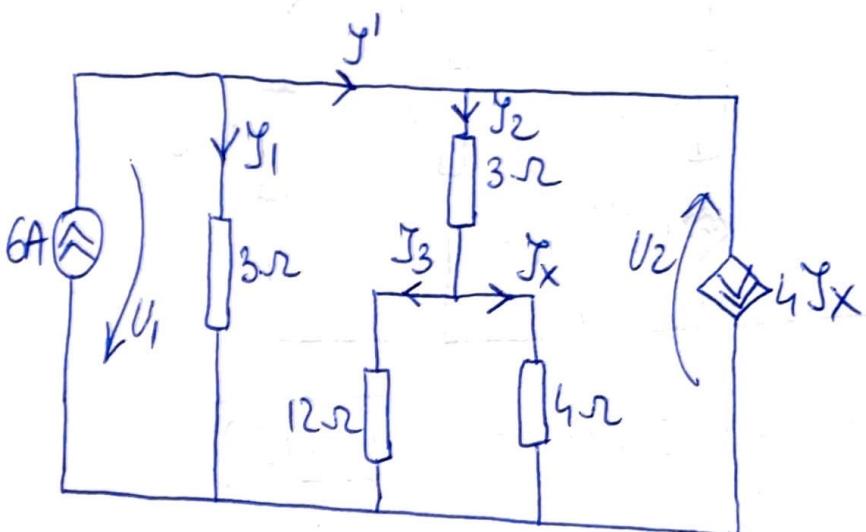

$$\left. \begin{array}{l} 6 = Y_1 + Y' \\ Y' = Y_2 + 4Y_x \\ Y_2 = Y_3 + Y_x \end{array} \right\} \Rightarrow \left. \begin{array}{l} 6 = Y_1 + Y_2 + 4Y_x \\ Y_2 = Y_3 + Y_x \end{array} \right\}$$

$$3Y_1 - 12Y_3 - 3Y_2 = 0 \Rightarrow Y_1 = Y_2 + 4Y_3$$


$$12Y_3 = 4Y_x \Rightarrow Y_x = 3Y_3$$

$$\left. \begin{array}{l} Y_1 + Y_2 + 4Y_x = 6 \\ Y_2 = Y_3 + Y_x \\ Y_1 = Y_2 + 4Y_3 \\ Y_x = 3Y_3 \end{array} \right\} \quad \begin{array}{l} Y_1 = 2A \\ Y_2 = 1A \\ Y_3 = 0,25A \\ Y_x = 0,75A \end{array}$$

$$U_1 = 3J_1 = 6V$$

$$U_2 = 3J_2 + 4J_x = 6V$$
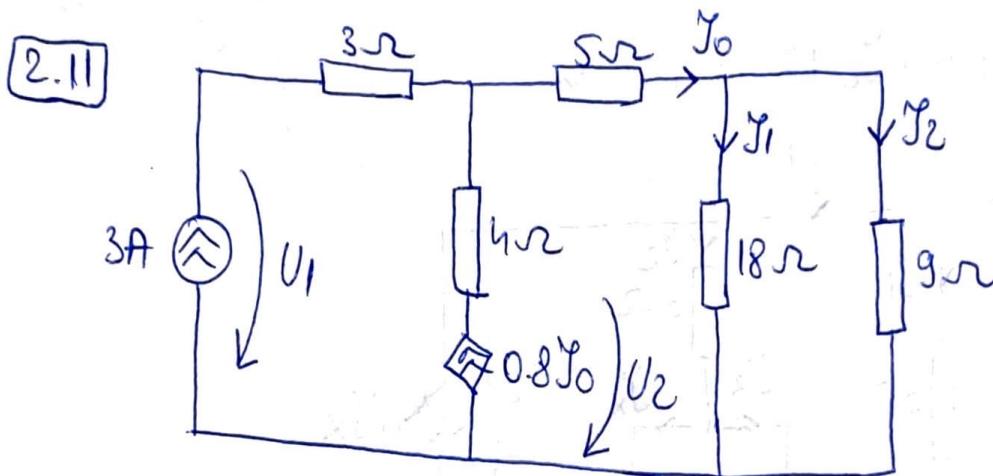
$$\begin{aligned} P_g &= 6U_1 + 4J_x U_2 = 54W \\ P_R &= 3J_1 + 3J_2 + 12J_3 + 4J_x = 15W \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow P_g \neq P_R$$



$$3A + 0.8J_0 = J_0 \Rightarrow 0.2J_0 = 3 \Rightarrow J_0 = 15A$$

$$\left. \begin{array}{l} J_0 = J_1 + J_2 \\ 18J_1 = 9J_2 \Rightarrow J_2 = 2J_1 \end{array} \right.$$

$$J_0 = J_1 + 2J_1 \Rightarrow J_0 = 3J_1 \Rightarrow J_1 = 5A$$

$$J_2 = 10A$$


$$U_1 = 3 \cdot 3 + 5J_0 + 18J_1 = 144V$$

$$U_2 = 12 \cdot 4 + 5J_0 + 18J_1 = 213V$$

$$P_g = 3U_1 + 0.8J_0 U_2 = 3048W$$

$$\begin{aligned} P_R &= 3^2 \cdot 3 + (0.8 \cdot 15)^2 \cdot 4 + 15^2 \cdot 5 + 5^2 \cdot 18 + 10^2 \cdot 9 = 3048W \\ \Rightarrow P_g &= P_R \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

E.12

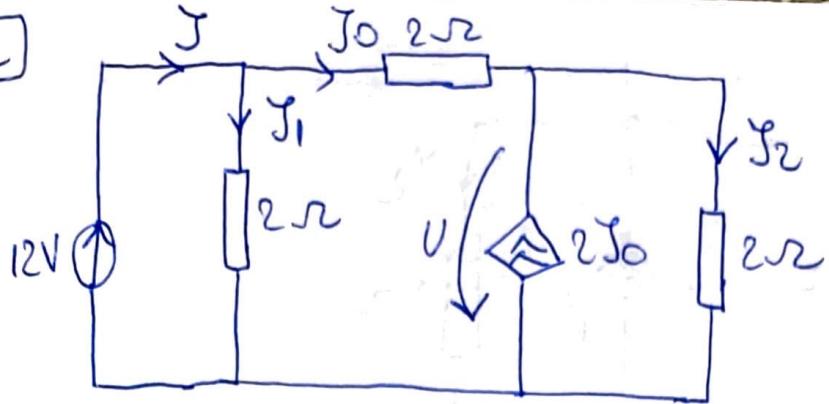

$$\begin{cases} J = J_0 + J_1 \\ J_0 + 2J_0 = J_2 \end{cases} \Rightarrow \begin{cases} J = J_0 + J_1 \\ J_2 = 3J_0 \end{cases}$$

$$12 = 2J_0 + 2J_2$$

$$12 = 2J_0 + 6J_0 \Rightarrow 12 = 8J_0 \Rightarrow J_0 = 1.5A$$

$$J_2 = 4.5A$$

$$2J_1 - 2J_0 = 0 \Rightarrow J_1 = J_0 \Rightarrow J_1 = 1.5A$$


$$J = 3A$$

$$U = -2J_0 + 2J_1 \Rightarrow U = 0$$

$$P_g = 12J \Rightarrow P_g = 36W$$

$$P_r = 2J_1 + 2J_0 + 2J_2 = 2(J_1 + J_0 + J_2) = 15W \quad \left\{ \Rightarrow P_g \neq P_r \right.$$

2.13

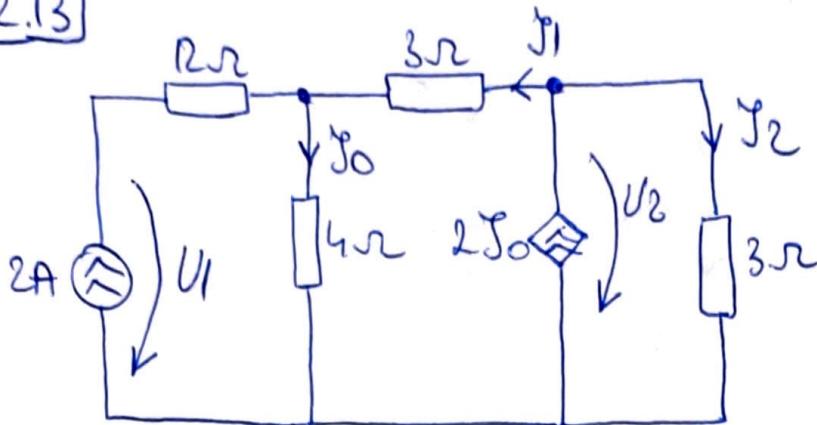

$$\left\{ \begin{array}{l} J_0 = 2 + J_1 \\ 2J_0 = J_1 + J_2 \\ 4J_0 + 3J_1 = 3J_2 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} 2(2 + J_1) = J_1 + J_2 \\ 4(2 + J_1) + 3J_1 = 3J_2 \end{array} \right.$$

$$\Rightarrow \left\{ \begin{array}{l} 4 + 2J_1 = J_1 + J_2 \\ 8 + 4J_1 + 3J_1 = 3J_2 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} J_2 - J_1 = 4 \Rightarrow J_2 = 4 + J_1 \\ 3J_2 - 4J_1 = 8 \end{array} \right.$$

$$3(4 + J_1) - 4J_1 = 8$$

$$12 + 3J_1 - 4J_1 = 8 \Rightarrow -J_1 = 8 - 12 \Rightarrow J_1 = 1 \text{ A}$$

$$J_2 = 5 \text{ A}$$

$$J_0 = 3 \text{ A}$$


$$U_1 = 2 \cdot 12 + 4J_0 = 36 \text{ V}$$

$$U_2 = 3J_2 = 15 \text{ V}$$

$$P_g = 2U_1 + 2J_0U_2 = 162 \text{ W}$$

$$P_r = 2^2 \cdot 12 + J_0^2 \cdot 4 + J_1^2 \cdot 3 + J_2^2 \cdot 3 = 162 \text{ W} \quad \Rightarrow P_g = P_r$$

2.14

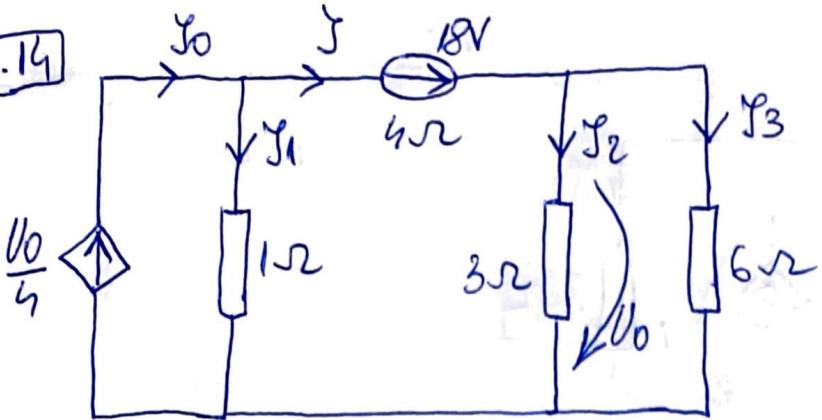

$$\begin{cases} \gamma_0 = \gamma + \gamma_1 \\ \gamma = \gamma_2 + \gamma_3 \end{cases}$$

$$U_0 = 3\gamma_2$$

$$3\gamma_2 = 6\gamma_3 \Rightarrow \gamma_3 = \frac{\gamma_2}{2}$$

$$\gamma = \gamma_2 + \frac{\gamma_2}{2} \Rightarrow \gamma = \frac{3\gamma_2}{2}$$

$$\frac{U_0}{\gamma} + 18 = 3\gamma_2 \Rightarrow \frac{U_0}{\gamma} + 18 = U_0 | \cdot 4 \Rightarrow U_0 + \gamma_2 = 4U_0$$

$$3U_0 = \gamma_2 \Rightarrow U_0 = 14V$$

$$\gamma_2 = 8A$$

$$\gamma_3 = 4A$$

$$\gamma = 12A$$


$$\frac{U_0}{\gamma} = 1 \cdot \gamma_1 \Rightarrow \gamma_1 = 6A$$

$$\gamma_0 = 18A$$

$$P_g = \frac{U_0}{\gamma} \cdot \gamma_0 + 18\gamma = 324W$$

$$P_R = \gamma_1^2 \cdot 1 + \gamma_2^2 \cdot 3 + \gamma_3^2 \cdot 6 \quad \Rightarrow P_g = P_R$$

2.15

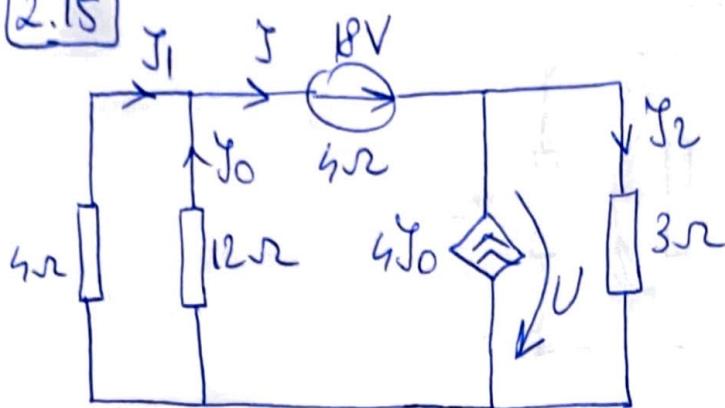

$$\begin{cases} J = J_1 + J_0 \\ J_2 = J + 4J_0 \end{cases}$$

$$18 = 12J_0 \Rightarrow J_0 = 1.5 \text{ A}$$

$$\begin{cases} J = J_1 + 1.5 \\ J_2 = J + 6 \end{cases}$$

$$18 = 4J_1 \Rightarrow J_1 = 4.5 \text{ A}$$

$$J = 6 \text{ A}$$

$$J_2 = 12 \text{ A}$$


$$U = 3J_2 = 36 \text{ V}$$

$$P_g = 18J + 4J_0U = 324 \text{ W}$$


$$P_r = J_1^2 \cdot 4 + J_0^2 \cdot 12 + J_2^2 \cdot 3 = 540 \text{ W}$$

$$\Rightarrow P_g \neq P_r$$

Q.16

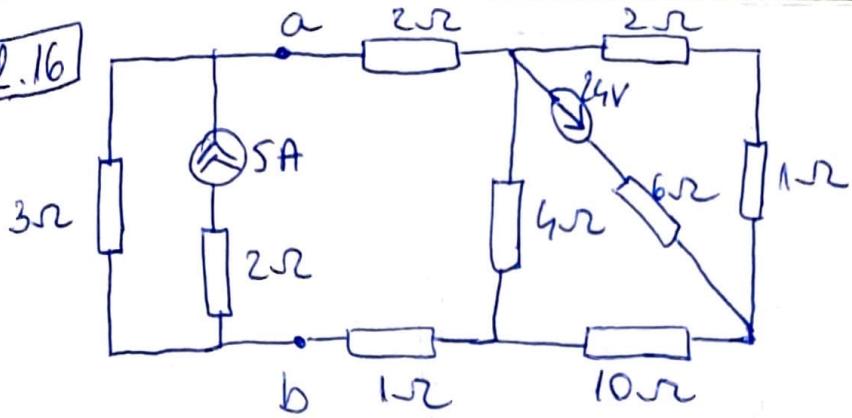

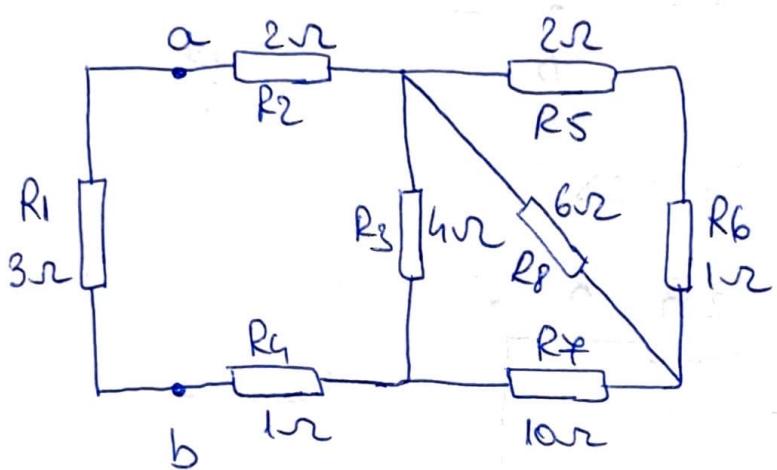Suppress all the sources = parallelize all the sources.



$$R_{D1} = R_5 + R_6 = 3\Omega$$

$$R_{P1} = \frac{R_{D1} R_8}{R_{D1} + R_8} = \frac{3 \cdot 6}{3+6} = 2\Omega$$


$$R_{D2} = R_{P1} + R_7 = 12\Omega$$

$$R_{P2} = \frac{R_3 R_{D2}}{R_3 + R_{D2}} = \frac{4 \cdot 12}{4+12} = 3\Omega$$


$$R_{D3} = R_2 + R_{P2} + R_4 = 6\Omega$$

$$R_e = \frac{R_1 R_{D3}}{R_1 + R_{D3}} = \frac{3 \cdot 6}{3+6} = 2\Omega$$

$R_e = 2\Omega$

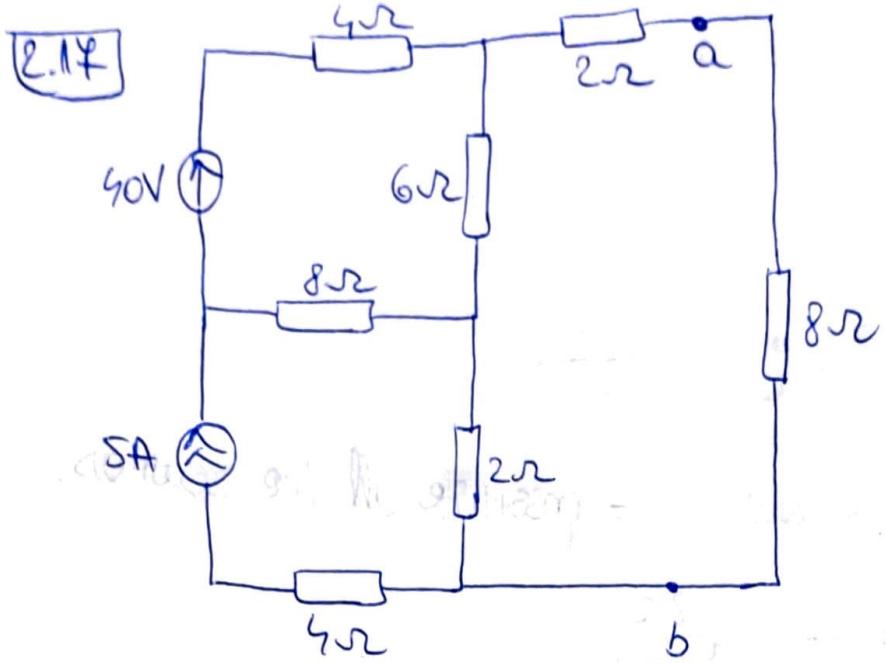

Suppress all the sources

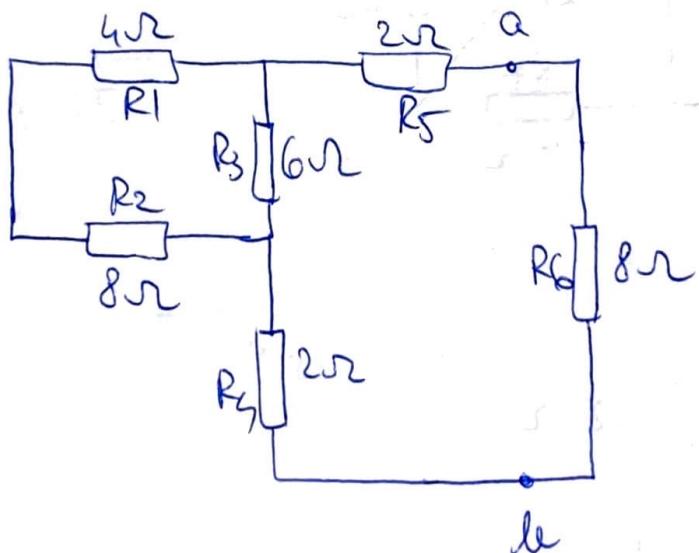

$$R_{S1} = R_1 + R_2 = 12\Omega$$


$$R_{P1} = \frac{R_{S1} R_3}{R_{S1} + R_3} = \frac{12 \cdot 6}{12 + 6} = 4\Omega$$

$$R_{S2} = R_5 + R_{P1} + R_4 = 8\Omega$$


$$R_e = \frac{R_{S2} \cdot R_6}{R_{S2} + R_6} = \frac{8 \cdot 8}{8 + 8} = 4\Omega$$

Re = 4Ω

2.18

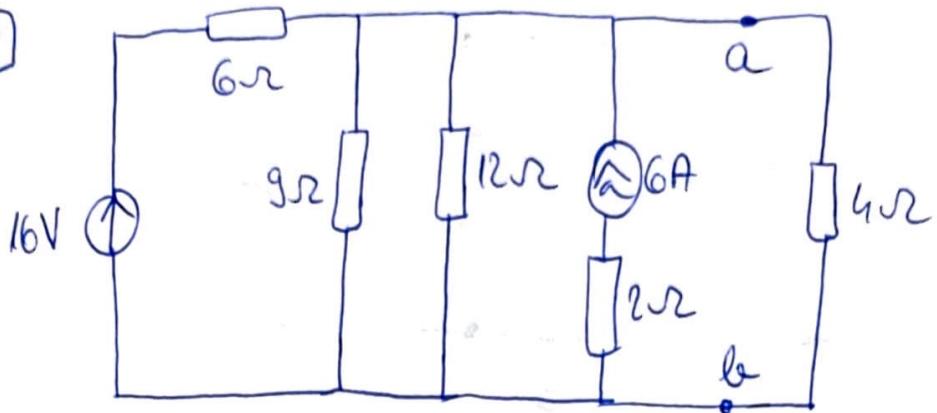

Suppress all the sources

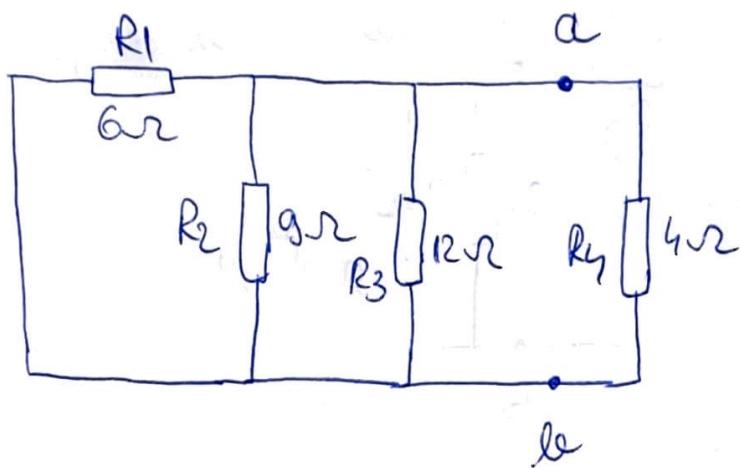


$$\frac{1}{R_{\text{e}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_{\text{e}}} = \frac{1}{6} + \frac{1}{9} + \frac{1}{12} + \frac{1}{4}$$


$$R_{\text{e}} = 1.63 \Omega$$



2.19

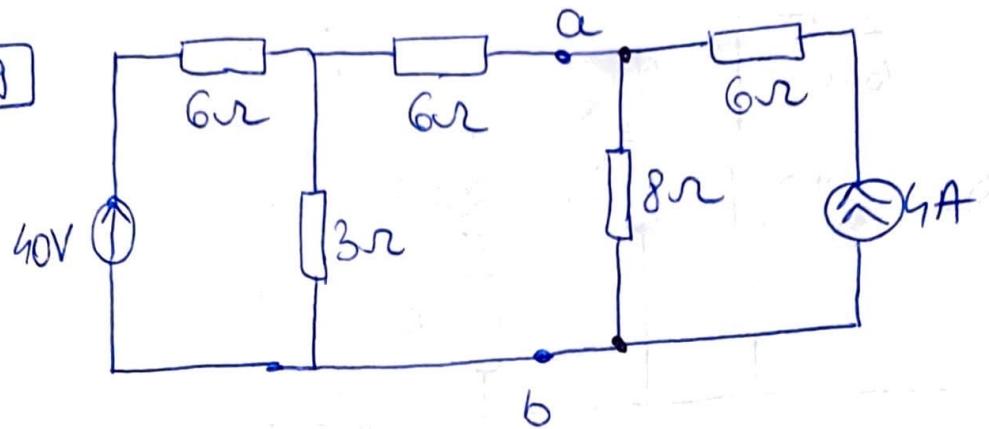

Suppress all the sources

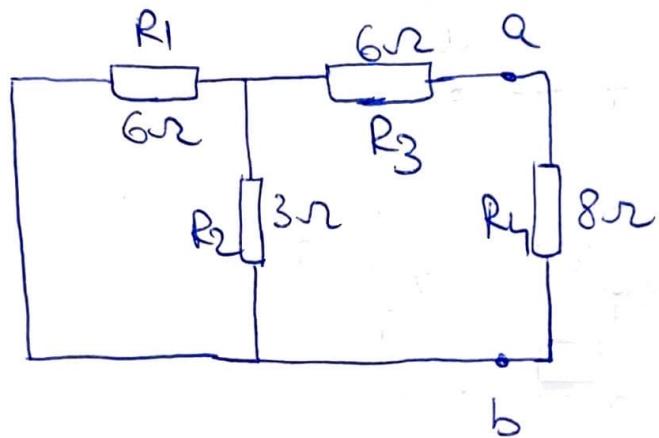


$$R_{P1} = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \cdot 3}{6+3} = 2\Omega$$

$$R_{S1} = R_{P1} + R_3 = 2 + 6 = 8\Omega$$


$$R_e = \frac{R_{S1} R_4}{R_{S1} + R_4} = \frac{8 \cdot 8}{8+8} = 4\Omega$$

$$(R_e = 4\Omega)$$

2.20

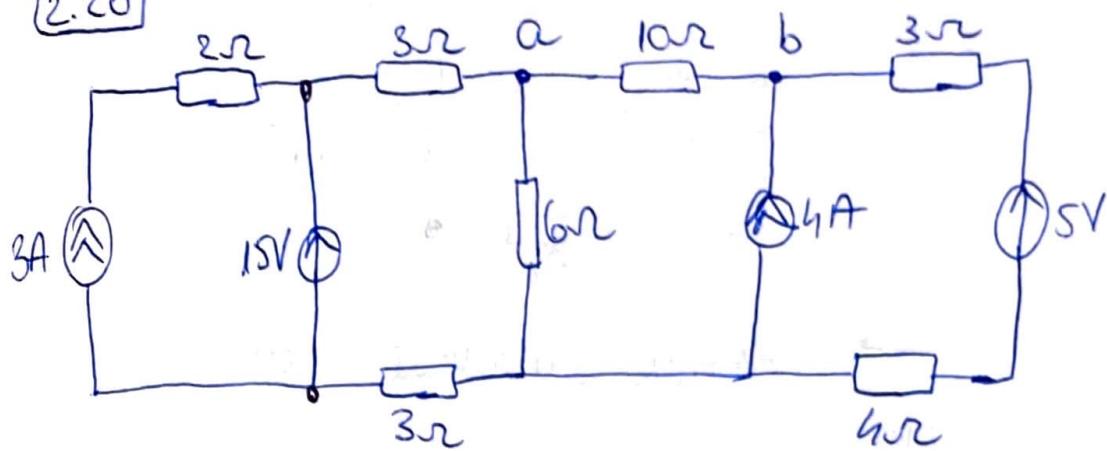

Simplify all the sources

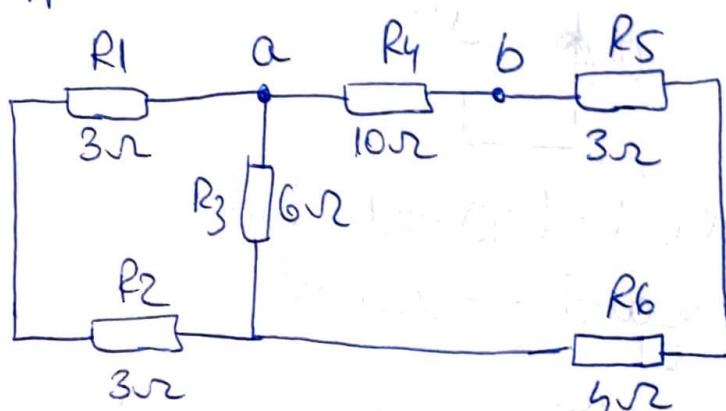

$$R_{D1} = R_1 + R_2 = 6\Omega$$

$$R_{P1} = \frac{R_{D1} R_3}{R_{D1} + R_3} = \frac{6 \cdot 6}{6+6} = 3\Omega$$

$$R_{D2} = R_5 + R_6 = 4\Omega$$

$$R_{D3} = R_{P1} + R_{D2} = 10\Omega$$

$$R_E = \frac{R_{D3} R_4}{R_{D3} + R_4} = \frac{10 \cdot 10}{10+10} = 5\Omega$$

$$R_E = 5\Omega$$

2.21

$\text{Reg} = ?$ $U_0 = ?$ $I = ?$


load is R

$$E = 15V$$


$$R_1 = 22\Omega$$

$$R_2 = 15\Omega$$


$$R_3 = R_4 = R = 100\Omega$$

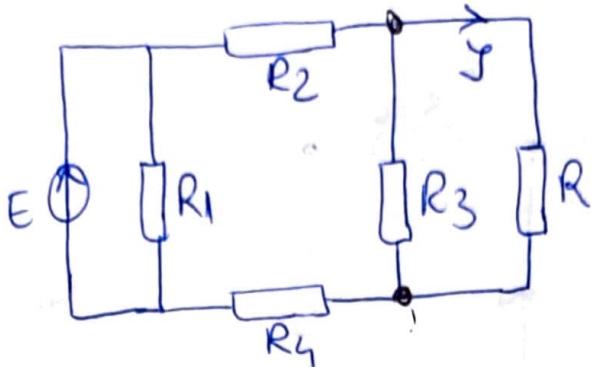

Thevenin equivalent circuit:

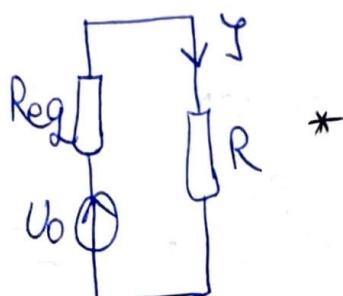

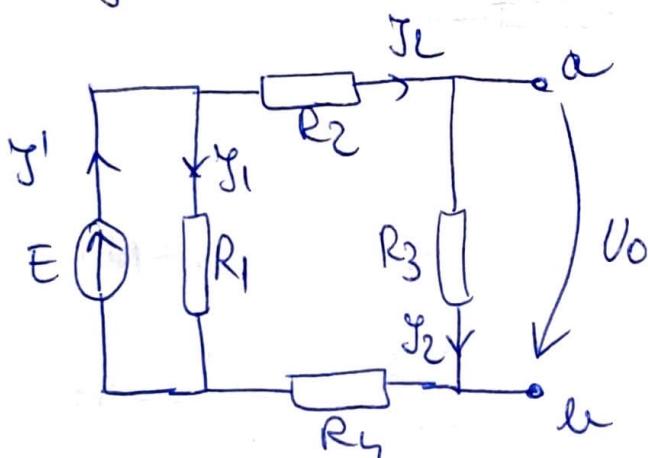Firstly, we remove the load (R) and calculate the voltage between the a and b terminals.




$$E = I_2(R_2 + R_3 + R_4)$$

$$\Rightarrow I_2 = \frac{E}{R_2 + R_3 + R_4} = \frac{3}{70} A$$

$$U_0 = I_2 R_3 = \frac{3}{70} \cdot 100$$

$$\Rightarrow U_0 = 4.28V$$

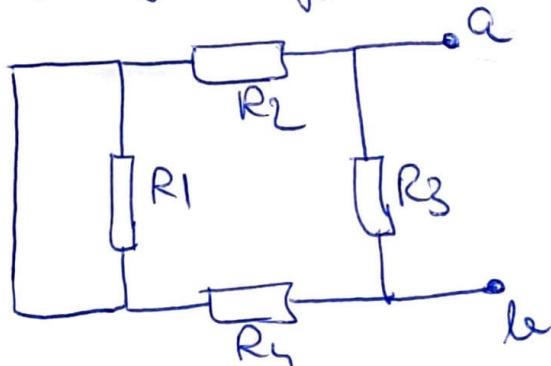Next, to find Reg , we have to suppress all sources.



$$R_D = R_1 + R_2 + R_4 = 47\Omega$$

$$\text{Reg} = \frac{R_D R_3}{R_D + R_3} = \frac{47 \cdot 100}{47 + 100}$$



$$\text{Reg} = 82.45 \Omega$$

From * $U_0 = I(\text{Reg} + R) \Rightarrow I = \frac{U_0}{\text{Reg} + R} = \boxed{I = 0.023A}$

2.22

$Reg = ?$ $U_0 = ?$ $\gamma = ?$

load is 4Ω 's resistance

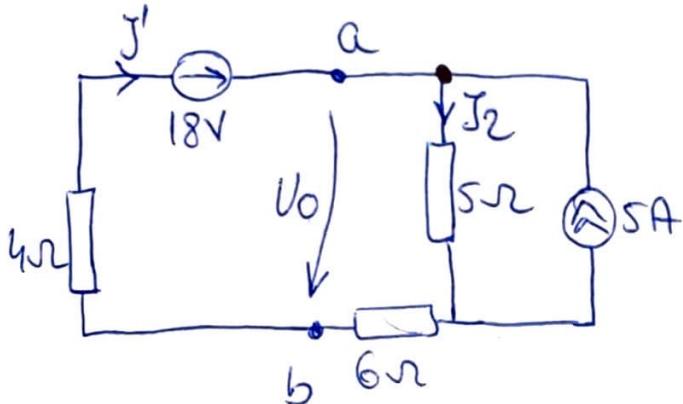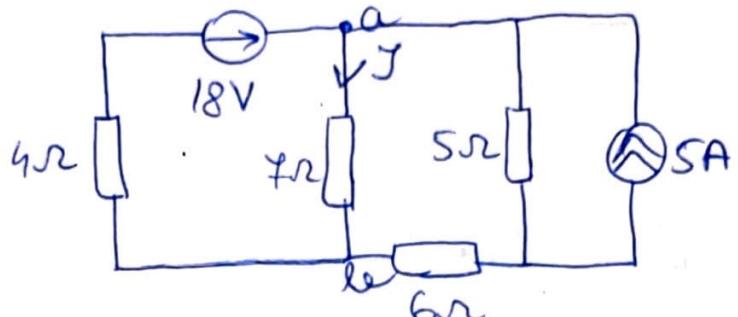

$$\gamma_2 = \gamma' + 5$$

$$18 = (4+6)\gamma' + 5\gamma_2$$


$$18 = 10\gamma' + 5(\gamma' + 5)$$

$$18 = 15\gamma' + 25$$

$$15\gamma' = -7 \Rightarrow \gamma' = -\frac{7}{15} A$$

$$18 = 4\gamma' + U_0 \Rightarrow U_0 = 18 - 4\gamma' = 19.86 V$$


$$\Rightarrow U_0 = 19.86 V$$

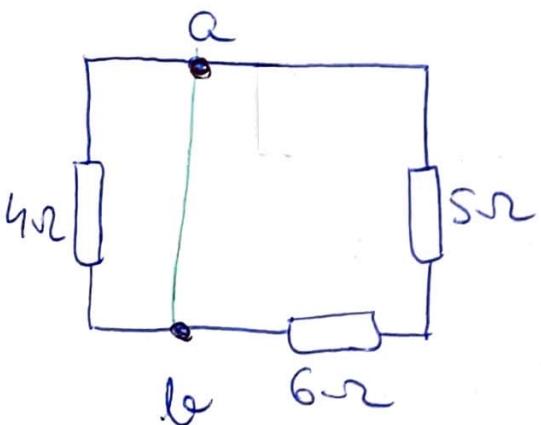

$$R_S = 5 + 6 = 11\Omega$$

$$Reg = \frac{R_S \cdot 4}{R_S + 4} = \frac{11 \cdot 4}{11 + 4}$$

$$Reg = 2.93 \Omega$$

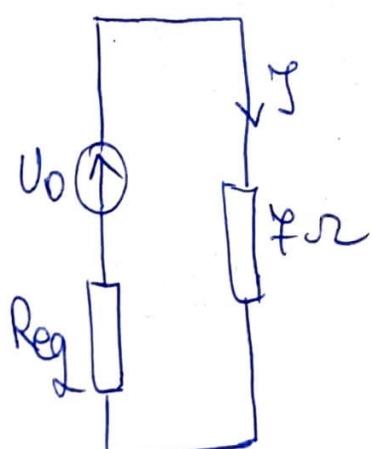

$$U_0 = I(7 + Reg)$$





$$I = \frac{19.86}{2.93}$$

$$I = 2 A$$

2.23

$$R_{\text{eq}} = ? \quad U_0 = ? \quad I = ?$$

load: 10Ω resist.

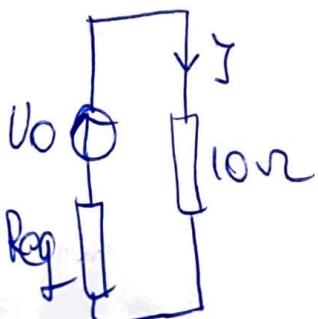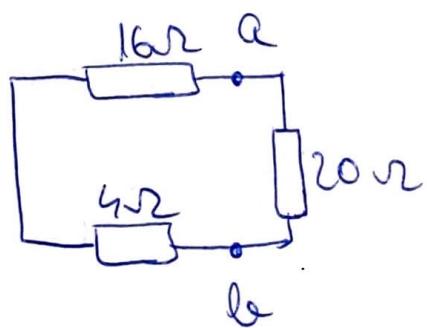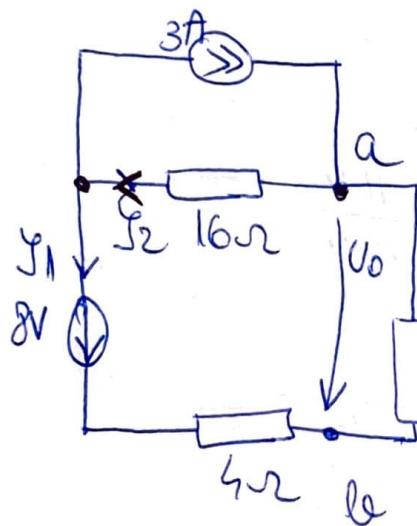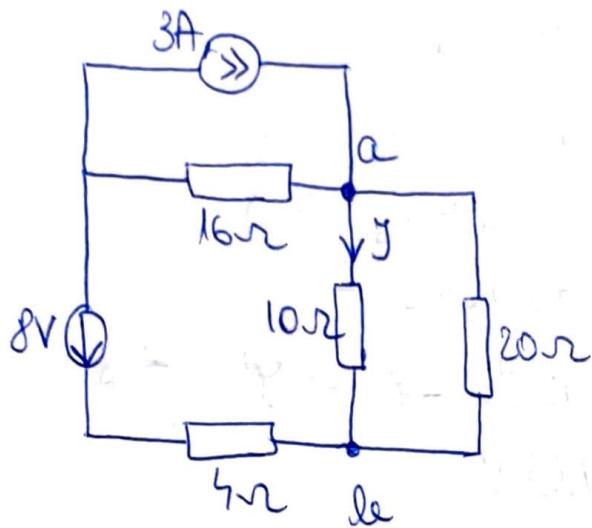

$$I_2 = I_1 + 3$$

$$8 = (4+20)I_1 - 16I_2$$

$$8 = 24I_1 - 16(I_1 + 3)$$

$$8 = 24I_1 - 16I_1 - 48$$

$$56 = 8I_1 \Rightarrow I_1 = 7A$$

$$U_0 = 20I_1 \Rightarrow U_0 = 140V$$

$$R_S = 16 + 4 = 20\Omega$$



$$R_{\text{eq}} = \frac{R_S \cdot 20}{R_S + 20} = \frac{20 \cdot 20}{20 + 20} \Rightarrow R_{\text{eq}} = 10\Omega$$

$$U_0 = I(10 + R_{\text{eq}})$$

$$\boxed{I = 7A}$$

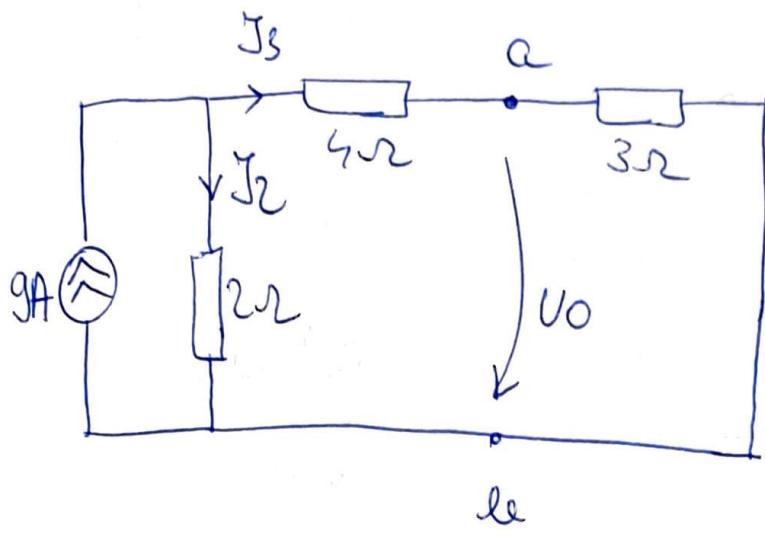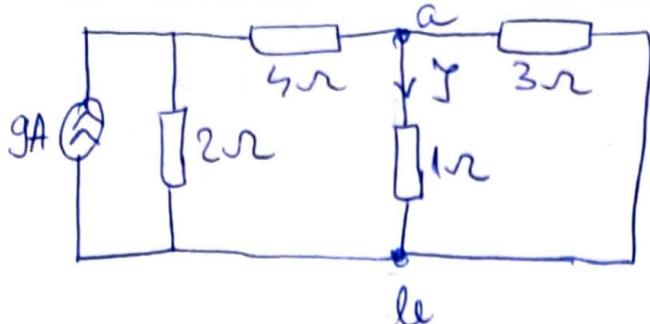2.24

$R_{\text{eq}} = ?$ $U_0 = ?$ $\gamma = ?$
ley 1rs Resist.




$$\gamma_2 + \gamma_3 = 9$$

$$0 = (4+3)\gamma_3 - 2\gamma_2$$

$$\begin{cases} 2\gamma_2 = 7\gamma_3 \\ \gamma_2 + \gamma_3 = 9 \end{cases}$$

$$\gamma_2 = 7A ; \gamma_3 = 2A$$


$$U_0 = 3\gamma_3 \Rightarrow U_0 = 6V$$

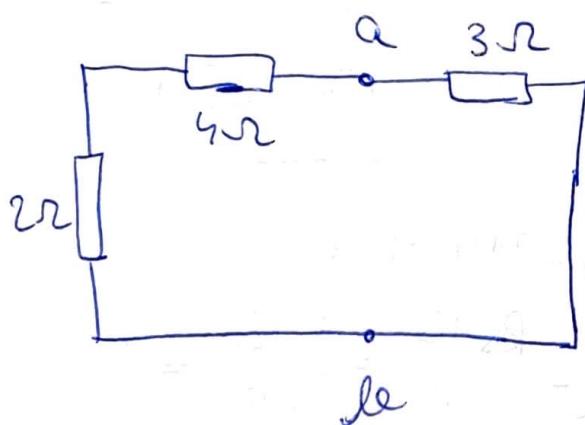

$$R_D = 2+4 = 6\Omega$$

$$R_{\text{eq}} = \frac{R_D \cdot 3}{R_D + 3} = \frac{6 \cdot 3}{6+3} = 2\Omega$$

$$R_{\text{eq}} = 2\Omega$$


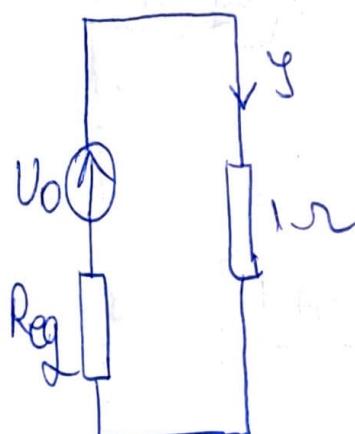


$$U_0 = \gamma(1+R_{\text{eq}})$$

$$\gamma = 2A$$

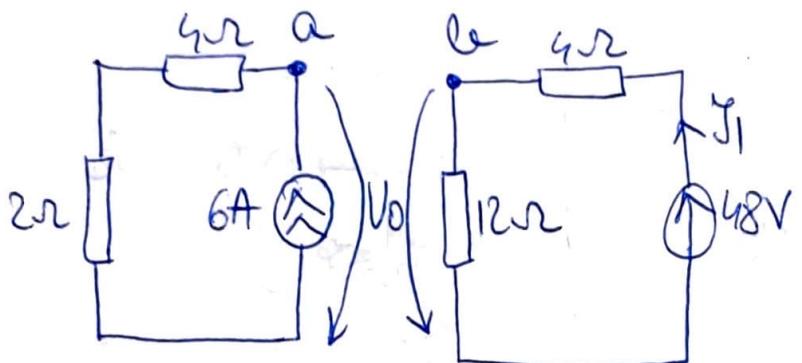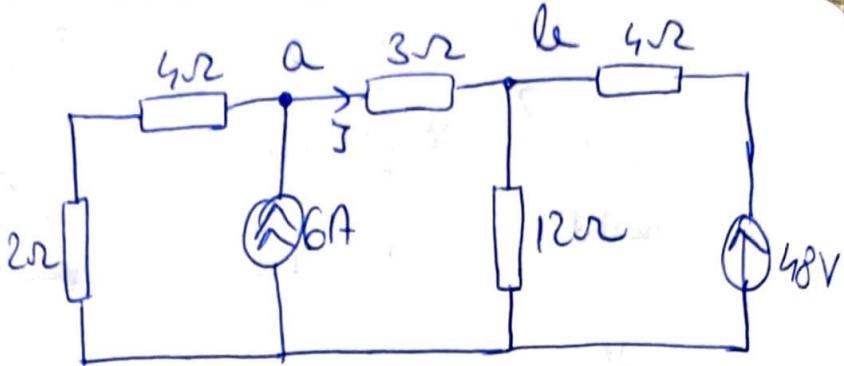2.25

$R_{\text{eq}} = ?$ $U_0 = ?$ $I = ?$
load: 3Ω resist.




$$\begin{cases} 48 = (12+4)I_1 \Rightarrow I_1 = 3A \\ U_0 = 12I_1 \Rightarrow U_0 = 36V \end{cases}$$

right circuit

$$U_0 = (2+4) \cdot 6 = 36V$$

left circuit


$$U_0 = 36V$$

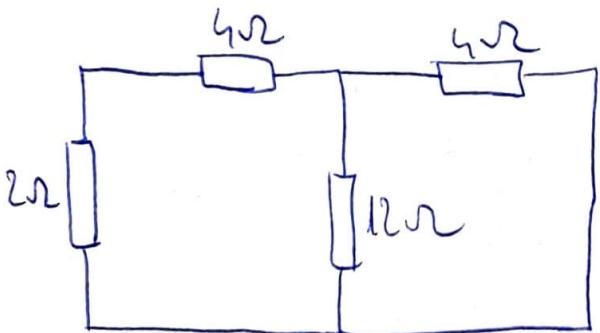

$$R_S = 2+4 = 6\Omega$$

$$R_P = \frac{R_S \cdot 12}{R_S + 12} = \frac{6 \cdot 12}{6 + 12} = 4\Omega$$
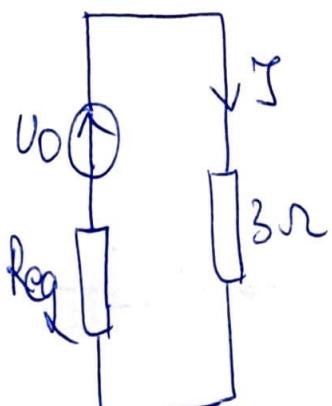
$$R_{\text{eq}} = R_P + R_S \Rightarrow R_{\text{eq}} = 8\Omega$$





$$U_0 = I(3 + R_{\text{eq}})$$

$$I = \frac{36}{3+8} \Rightarrow I = 3A$$

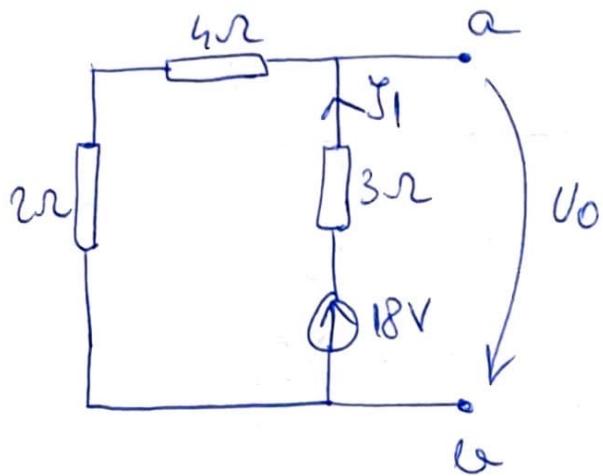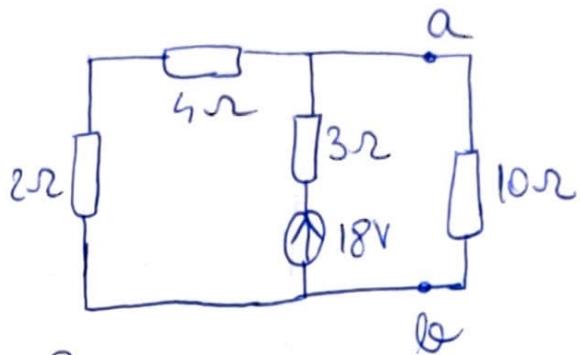
12.26

$R_{eq} = ?$ $U_0 = ?$ $I = ?$
by 10Ωs resist.



$$18 = (4+2+3)I_1 \Rightarrow I_1 = 2A$$

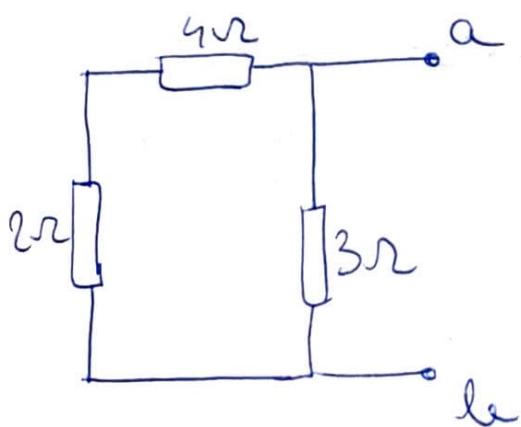
$$18 = 3I_1 + U_0 \Rightarrow \boxed{U_0 = 12V}$$



$$R_D = 2+4 = 6\Omega$$

$$R_{eq} = \frac{3R_S}{3+R_S} = \frac{3 \cdot 6}{3+6} = 2\Omega$$



$$\Rightarrow \boxed{R_{eq} = 2\Omega}$$

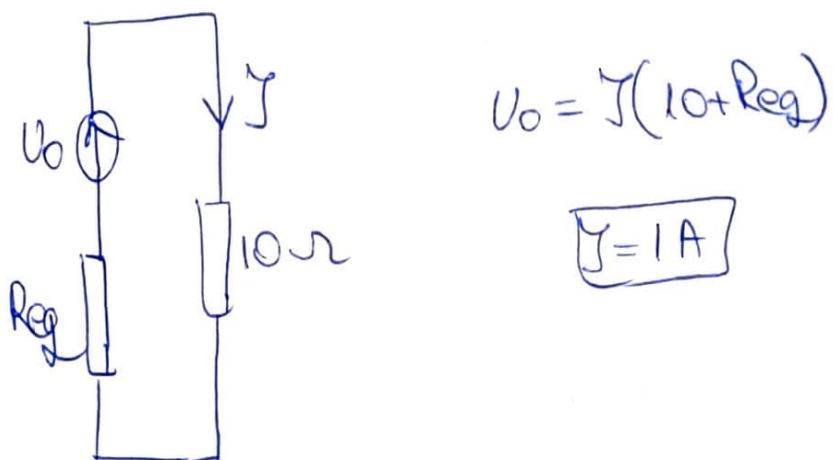

2.27

$Reg = ?$ $U_0 = ?$ $\mathcal{I} = ?$

by 10Ωs resist.

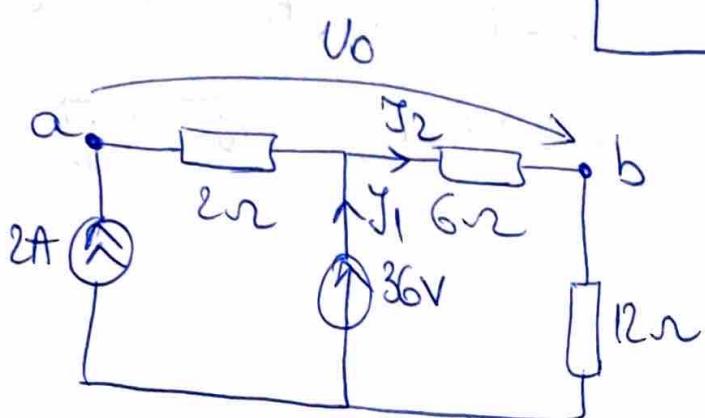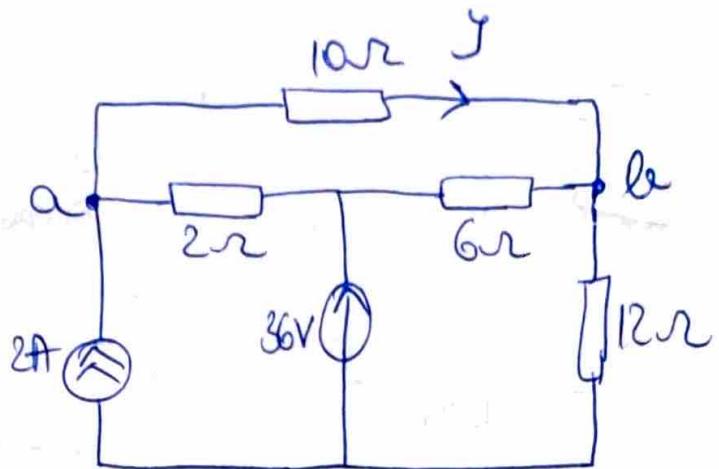


$$\mathcal{I}_2 = \mathcal{I}_1 + 2$$

$$36 = (6 + 12)\mathcal{I}_2$$

$$\Rightarrow \mathcal{I}_2 = 2A$$

$$0 = 2 \cdot 2 + 6\mathcal{I}_2 - U_0$$


$$\Rightarrow U_0 = 16V$$

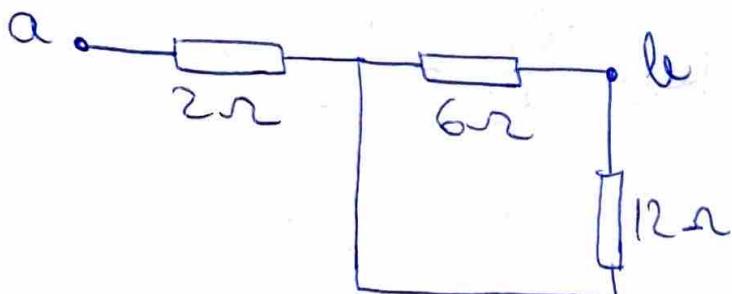

$$R_p = \frac{6 \cdot 12}{6+12} = 4\Omega$$

$$Reg = R_p + 2$$



$$Reg = 6\Omega$$

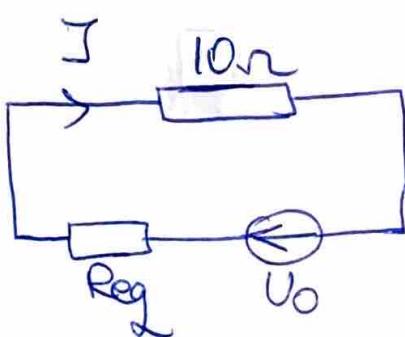

$$U_0 = \mathcal{I}(10 + Reg)$$

$$\mathcal{I} = \frac{16}{16} \Rightarrow \mathcal{I} = 1A$$

2.28

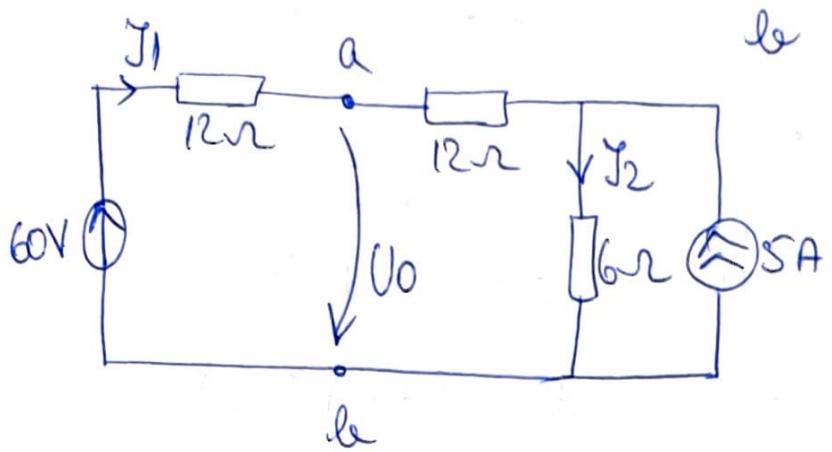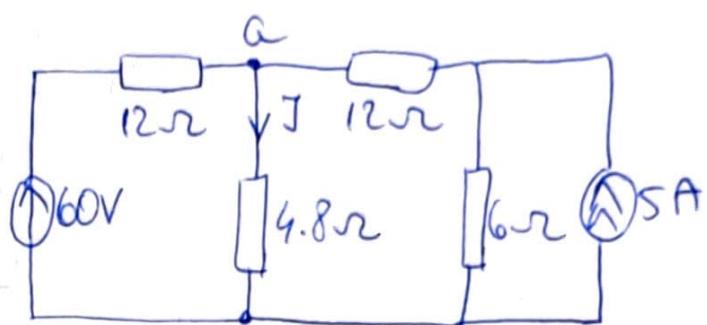 $R_{\text{eq}} = ?$ $U_0 = ?$ $\gamma = ?$ load: 4.8Ω s resist.


$$\gamma_2 = \gamma_1 + 5$$

$$60 = 24J_1 + 6\gamma_2$$

$$60 = 24J_1 + 6(\gamma_1 + 5)$$

$$60 = 30\gamma_1 + 30 \Rightarrow \gamma_1 = 1A$$

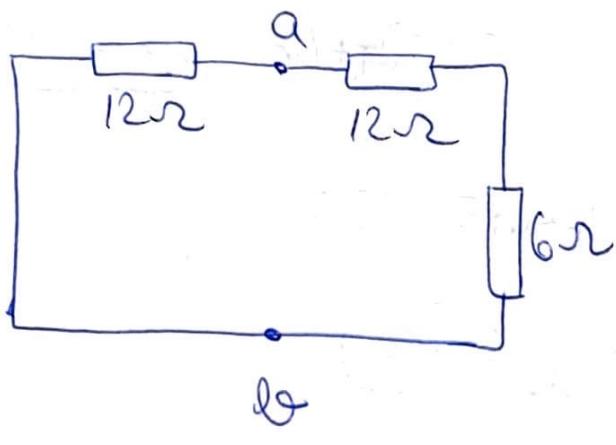
$$60 = 12J_1 + 6\gamma_1 \Rightarrow U_0 = 48V$$



$$R_S = 12 + 6 = 18\Omega$$

$$R_{\text{eq}} = \frac{12R_S}{12+R_S} = \frac{12 \cdot 18}{12+18}$$

$$R_{\text{eq}} = 4.2\Omega$$

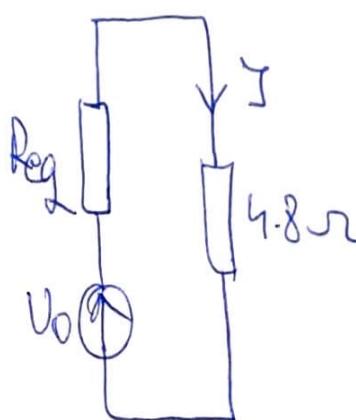



$$U_0 = \gamma(4.8 + R_{\text{eq}})$$

$$\boxed{\gamma = 4A}$$

2.29

$\text{Reg} = ?$ $U_0 = ?$ $I = ?$

by 6 Ω s resist.

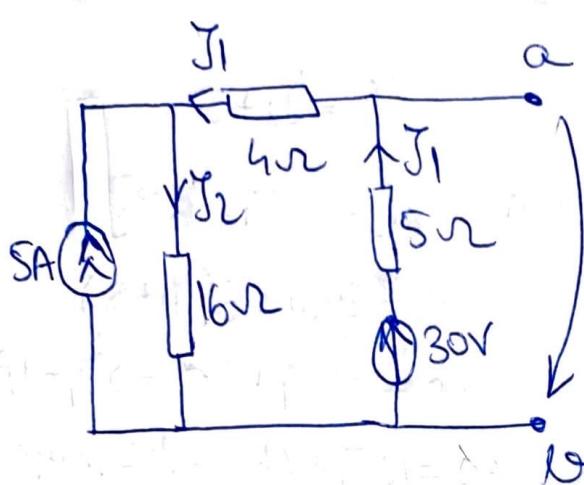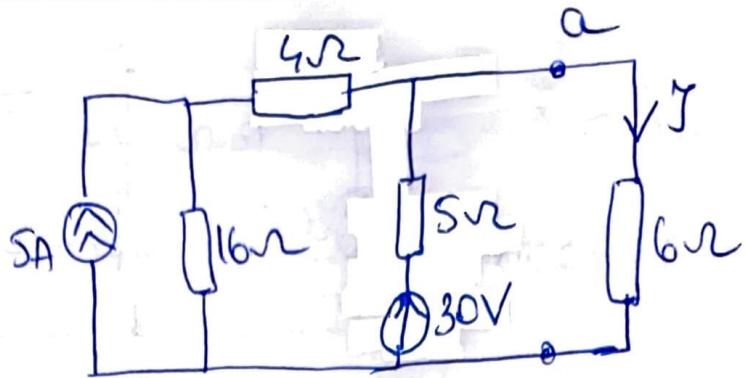


$$J_2 = J_1 + 5$$

$$30 = 9J_1 + 16J_2$$

$$30 = 9J_1 + 16(J_1 + 5)$$


$$30 = 25J_1 + 80 \Rightarrow J_1 = -2A$$
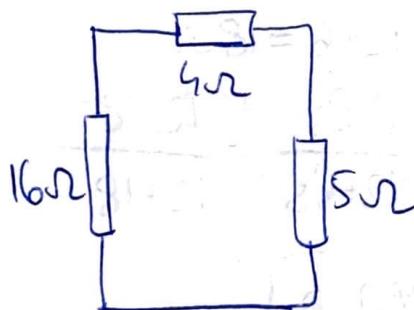
$$30 = 5J_1 + U_0 \Rightarrow U_0 = 40V$$



$$\text{Reg} = 16 + 4 + 5 = 25\Omega$$

$$\boxed{\text{Reg} = 25\Omega}$$

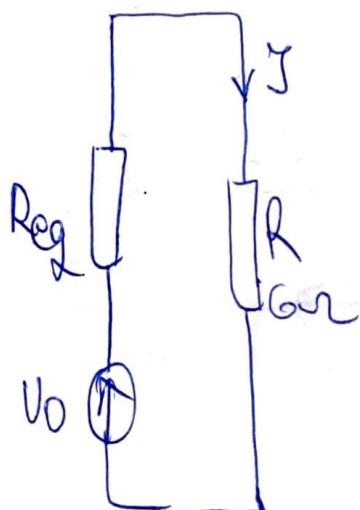


$$U_0 = I(6 + \text{Reg})$$

$$\boxed{I = 1.3A}$$

L.30

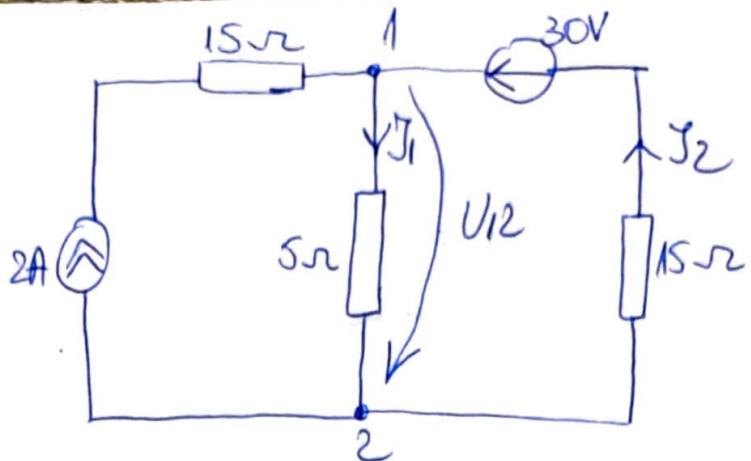- a) currents
 b) $\text{J}_2 = ?$ using Thévenin
 $U_{12} = ?$
 c) verify power cons. theorem



a) $\text{J}_1 = \text{J}_2 + 2$

$$30 = 15\text{J}_2 + 5\text{J}_1$$

$$30 = 15\text{J}_2 + 5(\text{J}_2 + 2)$$


$$30 = 20\text{J}_2 + 10$$

$$20 = 20\text{J}_2 \Rightarrow \boxed{\text{J}_2 = 1\text{A}}$$

$$\boxed{\text{J}_1 = 3\text{A}}$$

b) $U_{12} = 5\text{J}_1 \Rightarrow \boxed{U_{12} = 15\text{V}}$

Thévenin theorem:

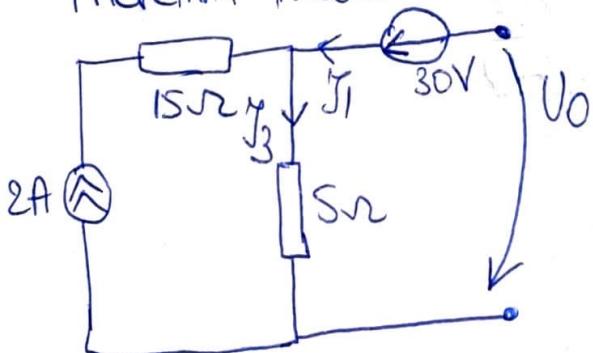

$$\text{J}_3 = \text{J}_1 + 2$$

$$5\text{J}_3 = 30 \Rightarrow \text{J}_3 = 6\text{A}$$

$$\text{J}_1 = 4\text{A}$$

$$U_0 = 0$$

$$\text{Req} = 5\Omega$$

2.31

$$R_1 = R_4 = 4\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 6\Omega$$

$$R_5 = 3\Omega$$


$$R_S = 10\Omega$$

$$E_1 = E_3 = 6V$$

$$E_4 = 3V$$

$$E_5 = 4V$$

$$J_D = 2A$$

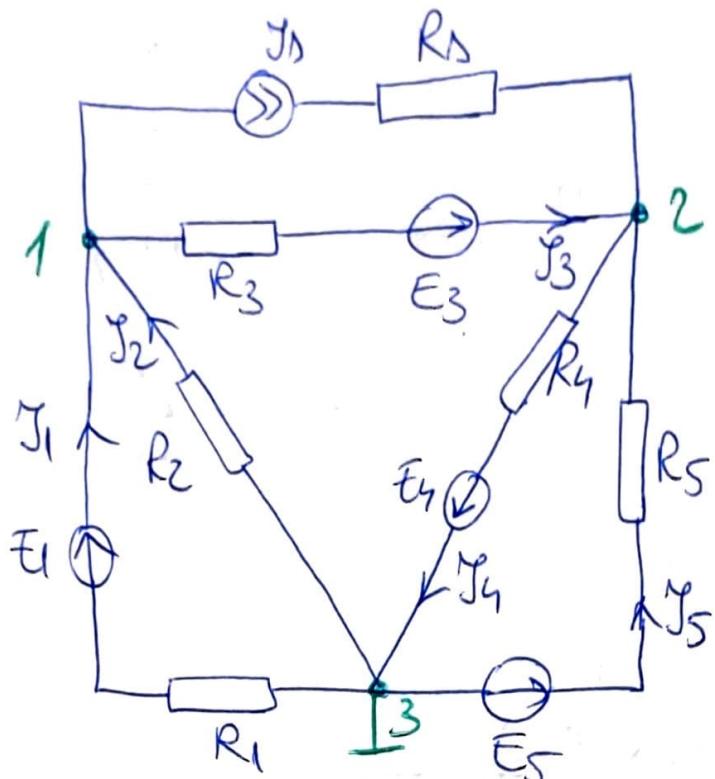

node 3 = reference node $\Rightarrow V_3 = 0V$

$$\text{node 1: } V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_2 \cdot \frac{1}{R_3} = E_1 \frac{1}{R_1} - E_3 \frac{1}{R_3} - J_D$$

$$\text{node 2: } V_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) - V_1 \cdot \frac{1}{R_3} = E_3 \frac{1}{R_3} + E_5 \frac{1}{R_5} - E_4 \frac{1}{R_4}$$

$$\begin{cases} 11V_1 - 2V_2 = -18 \\ 9V_2 - 2V_1 = 43 \end{cases} \Rightarrow \boxed{\begin{array}{l} V_1 = -0.8V \\ V_2 = 4.6V \end{array}}$$

$$V_3 - V_1 = J_1 R_1 - E_1 \Rightarrow \boxed{J_1 = 1.4A}$$


$$V_1 - V_2 = J_3 R_3 - E_3 \Rightarrow \boxed{J_3 = 0.1A}$$

$$V_2 - V_3 = J_4 R_4 - E_4 \Rightarrow \boxed{J_4 = 1.9A}$$

$$V_3 - V_2 = J_5 R_5 - E_5 \Rightarrow \boxed{J_5 = -0.2A}$$

$$V_3 - V_1 = J_2 R_2 \Rightarrow \boxed{J_2 = 0.4A}$$

2.32

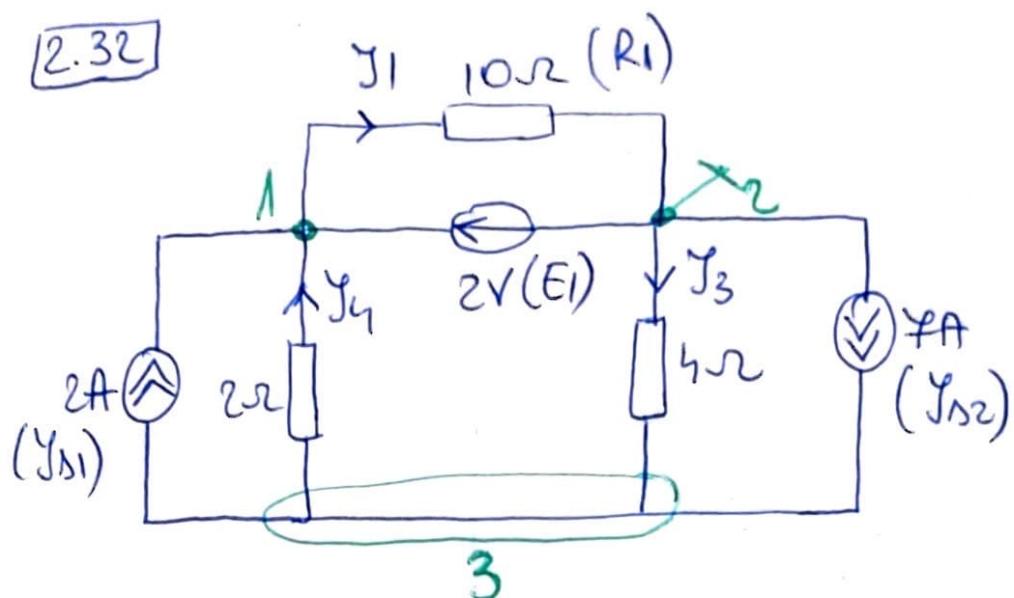

Because between 1 and 2 we only have a voltage source, we have a supernode.

$$\text{Reference node: } 2 \Rightarrow V_2 = 0V$$

$$V_1 - V_2 = E_1 \Rightarrow V_1 = 2V$$

$$\text{node 3: } V_3 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - \mathcal{Y}_1 \cdot \frac{1}{R_2} = \mathcal{Y}_{S2} - \mathcal{Y}_{S1} \Rightarrow V_3 = 8V$$


$$V_1 - V_2 = \mathcal{Y}_1 R_1 \Rightarrow \mathcal{Y}_1 = 0.2A$$

$$V_3 - V_1 = \mathcal{Y}_4 R_2 \Rightarrow \mathcal{Y}_4 = 3A$$

$$\mathcal{Y}_{S1} + \mathcal{Y}_4 = \mathcal{Y}_1 + \mathcal{Y}_2 \Rightarrow \mathcal{Y}_2 = 4.8A$$

$$\mathcal{Y}_1 + \mathcal{Y}_2 = \mathcal{Y}_3 + \mathcal{Y}_{S2} \Rightarrow \mathcal{Y}_3 = -2A$$

2.33

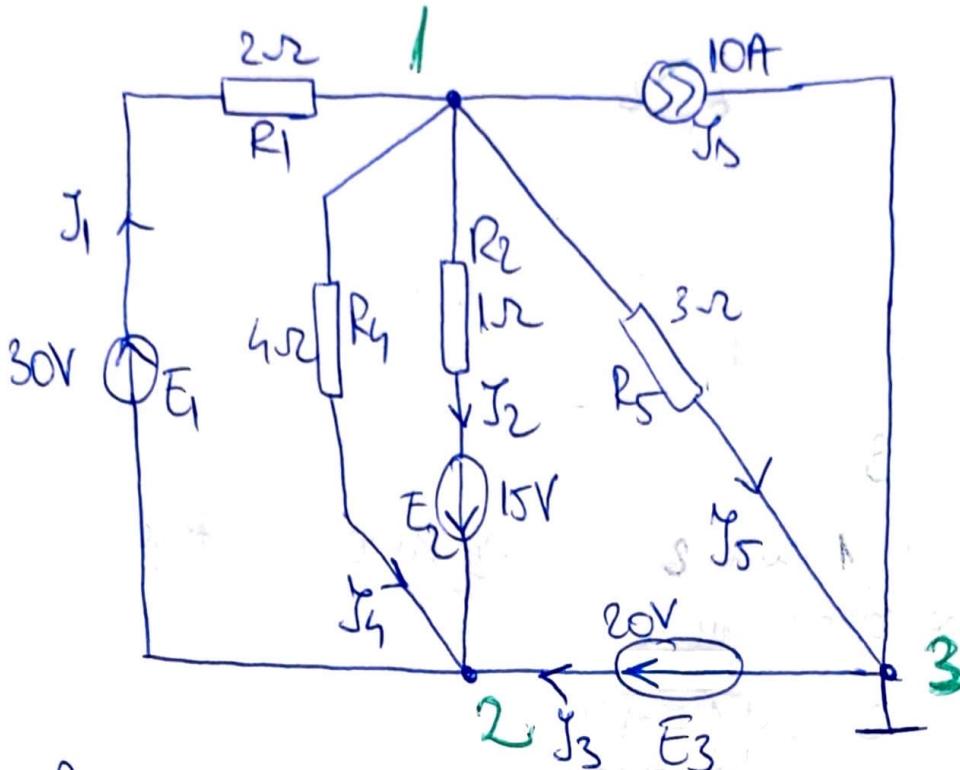

Because between 2 and 3 there is no resistance (only a voltage source), we have a supernode.

$$\text{Reference} = \text{node 3} \Rightarrow V_3 = 0V$$

$$V_2 - V_3 = E_3 \Rightarrow V_2 = 20V$$

$$\begin{aligned} \text{mode 1: } V_1 & \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right) - V_2 \left(\frac{1}{R_2} + \frac{1}{R_4} \right) \\ & = E_1 \frac{1}{R_1} - E_2 \cdot \frac{1}{R_2} - J_1 \end{aligned}$$

$$\Rightarrow V_1 = 4.2V$$

$$V_1 - V_2 = J_2 R_2 - E_2 \Rightarrow J_2 = 2.2A$$


$$V_2 - V_1 = J_1 R_1 - E_1 \Rightarrow J_1 = 21.4A$$

$$V_1 - V_3 = J_5 R_5 \Rightarrow J_5 = 2.4A$$

$$J_3 = J_5 + 10 \Rightarrow J_3 = 12.4A$$

$$J_4 = J_6 + J_2 + J_3 \Rightarrow J_4 = 6.8A$$

2.34

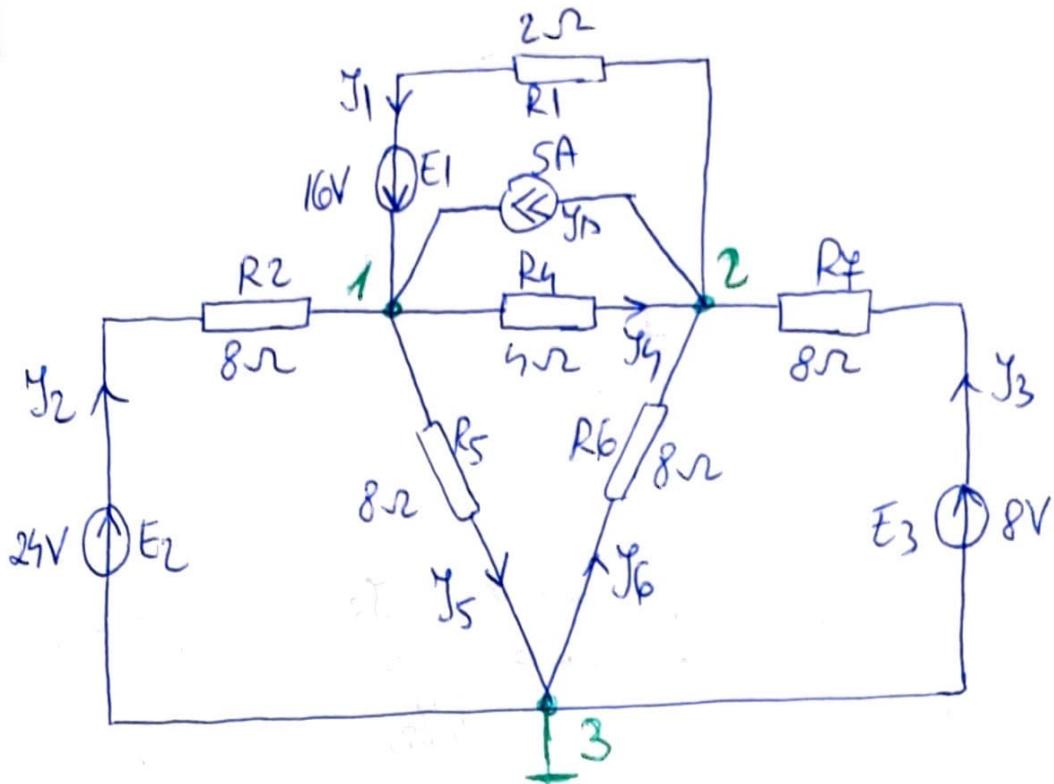

Reference mode = 3 $V_3=0V$

$$\text{mode 1: } V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right) - V_2 \left(\frac{1}{R_1} + \frac{1}{R_4} \right) = E_1 \cdot \frac{1}{R_1} + E_2 \cdot \frac{1}{R_2} + J_1$$

$$\text{mode 2: } V_2 \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_6} \right) - V_1 \left(\frac{1}{R_1} + \frac{1}{R_4} \right) = -E_1 \frac{1}{R_1} + E_3 \frac{1}{R_3} - J_1$$

$$\begin{cases} 12V_1 - 9V_2 = 192 \\ -12V_1 + 16V_2 = -192 \end{cases} \Rightarrow \begin{cases} V_2 = 0V \\ V_1 = 16V \end{cases}$$

$$V_3 - V_1 = J_2 R_2 - E_2 \Rightarrow J_2 = 1A$$

$$V_2 - V_1 = J_1 R_1 - E_1 \Rightarrow J_1 = 0A$$


$$V_3 - V_2 = J_3 R_3 - E_3 \Rightarrow J_3 = 1A$$

$$V_1 - V_2 = J_4 R_4 \Rightarrow J_4 = 4A$$


$$J_1 + J_2 + J_3 = J_5 + J_4 \Rightarrow J_5 = 2A$$

$$J_3 + J_4 + J_6 = J_1 + J_5 \Rightarrow J_6 = 0A$$


[2.35]

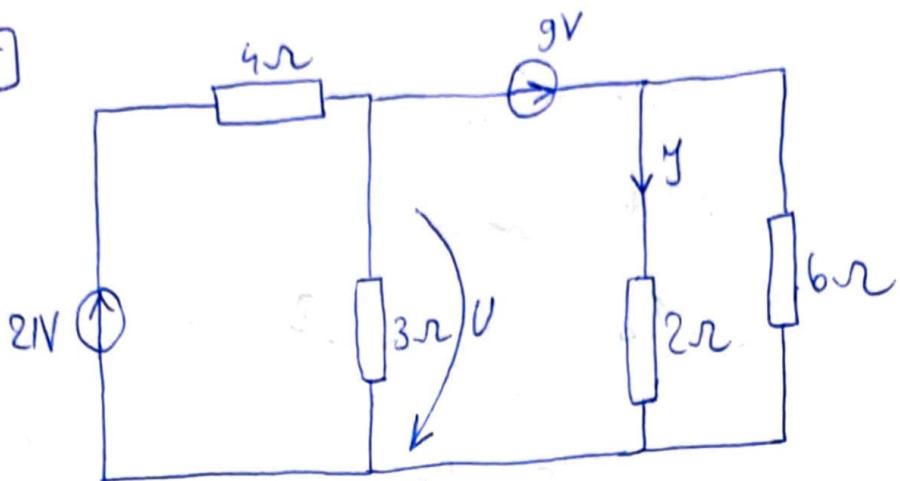

a)

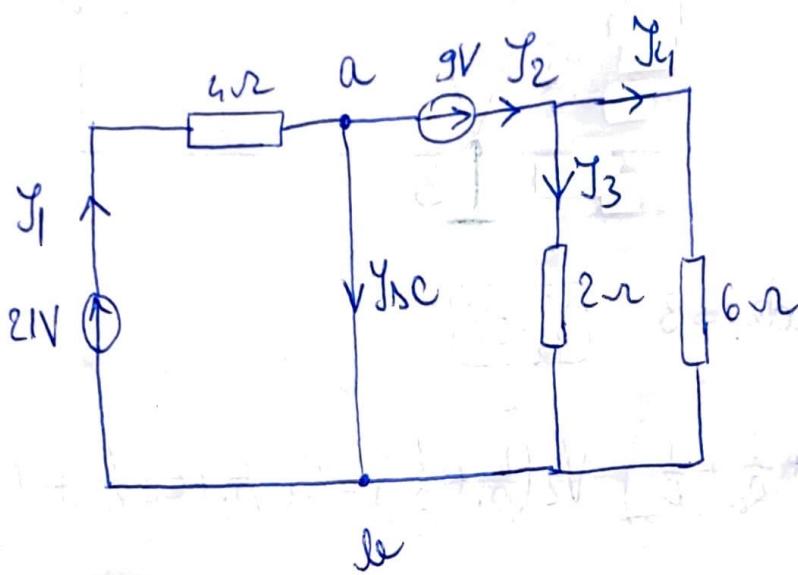
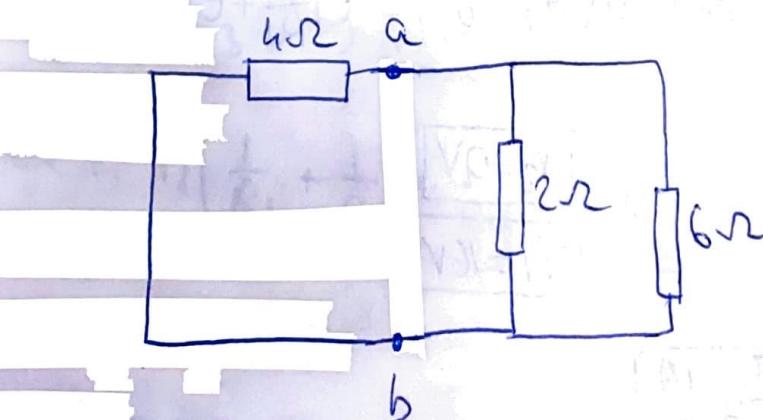
$$\begin{cases} Y_2 = Y_1 + Y_{SC} \\ Y_2 = Y_3 + Y_4 \\ 2I = 4Y_1 \Rightarrow Y_1 = 0.5A \\ 9 = 2Y_3 \Rightarrow Y_3 = 4.5A \\ 2Y_3 = 6Y_4 \Rightarrow Y_4 = 1.5A \\ Y_2 = 6A \\ Y_{SC} = 0.75A \end{cases}$$




$$G_O = \frac{1}{6} + \frac{1}{2} + \frac{1}{4}$$

$$G_O = 0.917$$

$$G = \frac{1}{R} = \frac{1}{3}$$

$$G = 0.333$$
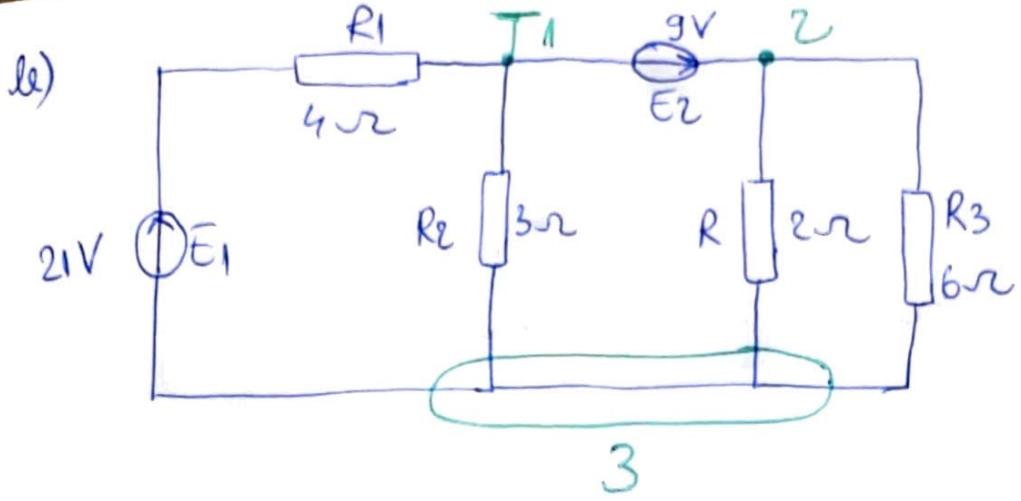
$$U = \frac{Y_{SC}}{G+G_O} \Rightarrow U = 0.60V$$



Reference mode = 1 $\Rightarrow V_1 = 0V$


$$\text{mode 3: } V_3 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R} + \frac{1}{R_3} \right) - V_2 \left(\frac{1}{R} + \frac{1}{R_3} \right) = -E_1 \frac{1}{R_1}$$

$$\Rightarrow V_3 = -\varphi V$$

$$V_2 - V_1 = E \Rightarrow V_2 = 21V$$

$$U = V_1 - V_3 = -\varphi V \Rightarrow U = -\varphi V$$

c) Thévenin

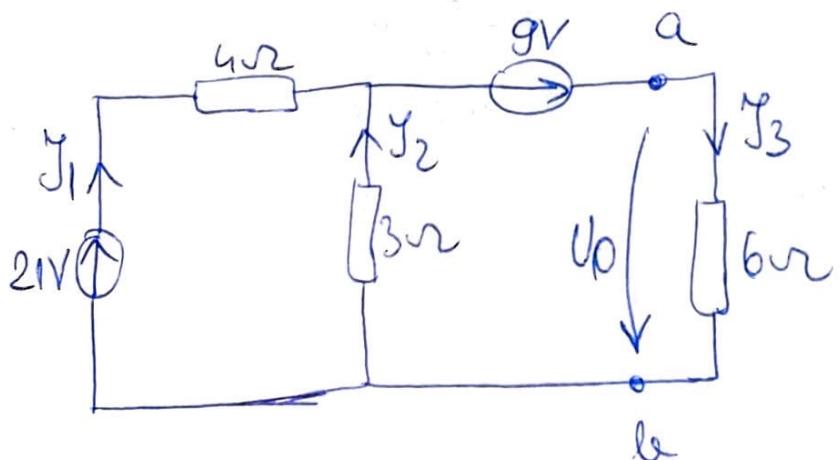

$$Y_3 = Y_1 + Y_2$$


$$2I = 4Y_1 - 3Y_2$$

$$g = 6Y_3 + 3J_2$$

$$Y_1 = 4A ; Y_2 = -1.66A ; Y_3 = 2.33A$$

$$U_0 = J_3 R_3 \Rightarrow U_0 = 14V$$

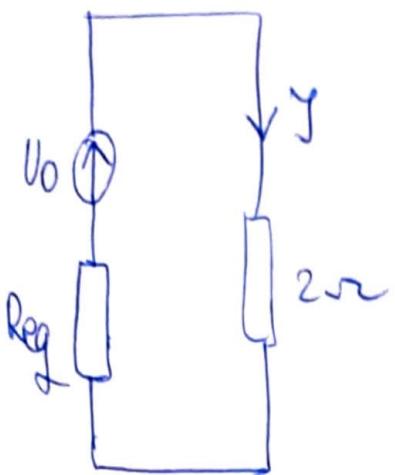
$$\text{from Norton} \Rightarrow R_{eq} = \frac{1}{60} = \frac{1}{9}\Omega$$



$$Y = \frac{U_0}{2 + R_{reg}}$$

$$\Rightarrow Y = 4.2 \text{ A}$$

2.36

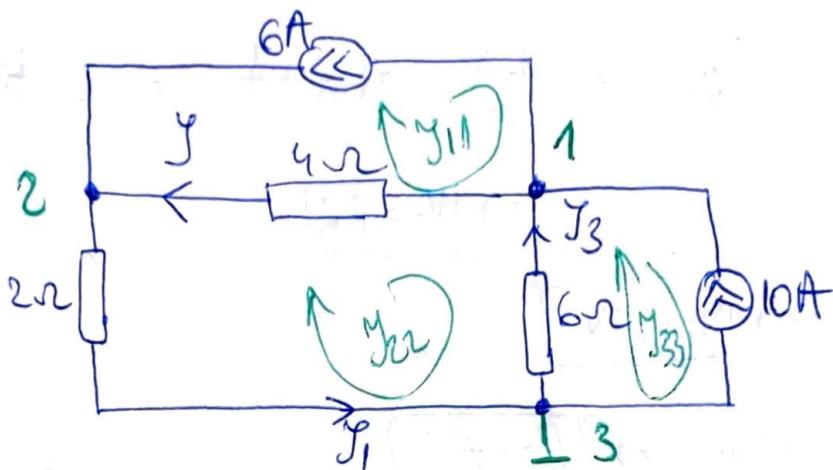

- a) Kirchhoff laws
- b) modal analysis
- c) mesh analysis

verify Y by Thévenin

Verify power cons. theorem

$$\begin{aligned} a) \quad Y + 6 &= Y_3 + 10 \\ Y + 6 &= Y_1 \\ Y_1 &= Y_3 + 10 \end{aligned}$$

$$Y_1 R_1 + Y_3 R_3 + Y R_2 = 0$$

$$\Rightarrow Y_1 + 3Y_3 + 2Y = 0$$

$$Y_1 = 4 \text{ A}$$

$$Y = 1 \text{ A}$$

$$Y_3 = -3 \text{ A}$$

b) Node 3 is the ground $\Rightarrow Y_3 = 0 \text{ V}$

$$\left. \begin{aligned} V_1 \left(\frac{1}{4} + \frac{1}{6} \right) - V_2 \cdot \frac{1}{4} &= 10 - 6 \\ V_2 \left(\frac{1}{4} + \frac{1}{6} \right) - V_1 \cdot \frac{1}{4} &= 6 \end{aligned} \right\} \Rightarrow \begin{aligned} V_1 &= 18 \text{ V} \\ V_2 &= 14 \text{ V} \end{aligned}$$

$$V_1 - V_2 = J R_2 \Rightarrow J = 1 A$$

$$V_1 - V_3 = -J R_3 \Rightarrow J_3 = -3 A$$

$$V_2 - V_3 = J_1 R_1 \Rightarrow J_1 = 7 A$$

c) $J_{11} = 6 A$

$J_{33} = 10 A$

$J = J_{11} - J_{22} = J_{22} - 6$

$J_1 = J_{22}$

$J_3 = J_{22} - J_{33} = J_{22} - 10$

$$J_1 R_1 + J_3 R_3 + J = 0 \Rightarrow 2J_{22} + 6(J_{22} - 10) + 4(J_{22} - 6) = 0$$


$$\Rightarrow J_{22} = 4 A$$


$J_1 = 4 A$

$J = 1 A$

$J_3 = -3 A$

2.34

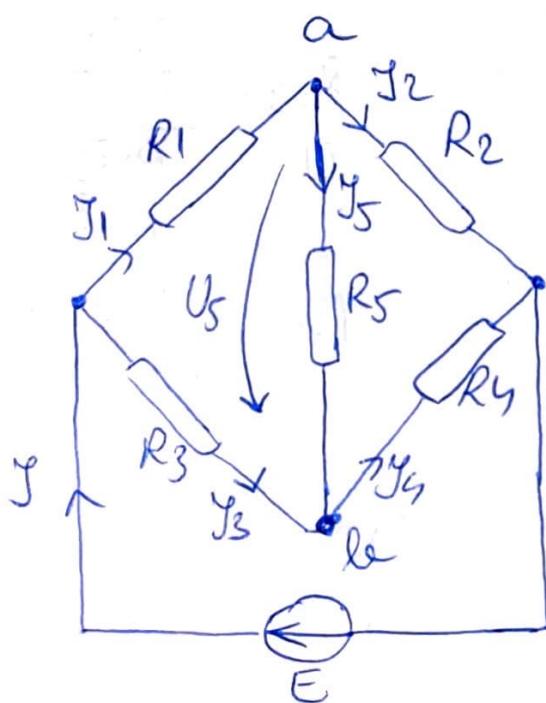

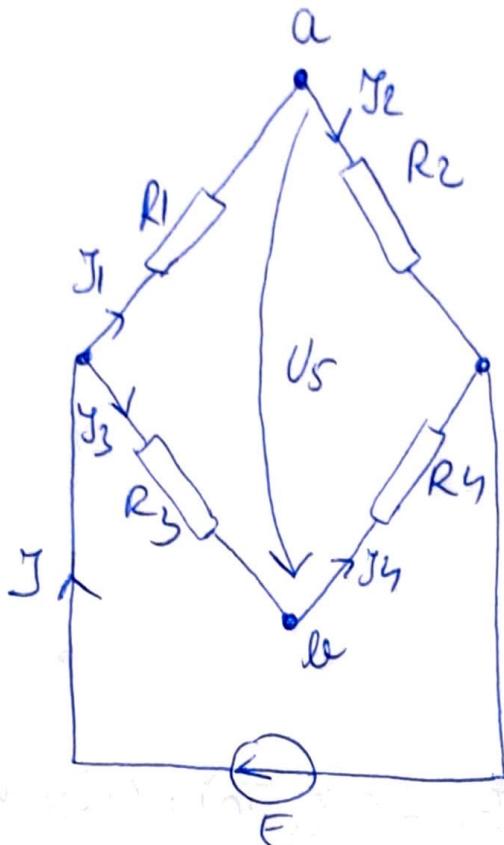

$$\begin{aligned} Y &= Y_1 + Y_3 \quad \left\{ \Rightarrow Y = Y_1 + Y_2 + Y_3 + Y_4 \right\} \\ Y &= Y_2 + Y_4 \end{aligned}$$


$$E = Y_1 R_1 + Y_2 R_2$$

$$E = Y_3 R_3 + Y_4 R_4$$

$$Y_1 R_1 + Y_2 R_2 = Y_3 R_3 + Y_4 R_4$$

$$U_5 = Y_2 R_2 - Y_4 R_4$$

$$U_5 = Y_3 R_3 - Y_1 R_1$$

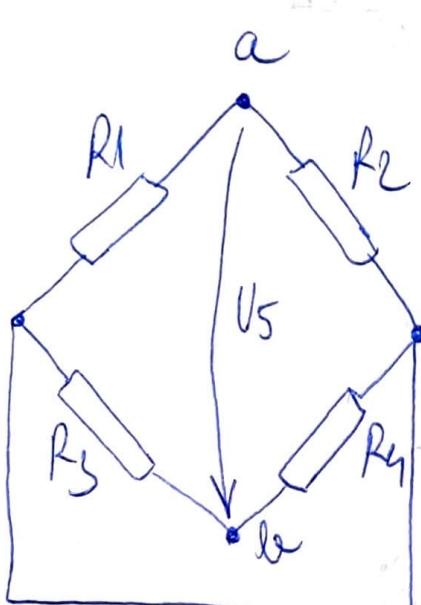


$$R_{P1} = \frac{R_1 R_3}{R_1 + R_3}$$

$$R_{P2} = \frac{R_2 R_4}{R_2 + R_4}$$

$$\text{Reg} = \frac{\frac{R_1 R_3}{R_1 + R_3} \cdot \frac{R_2 R_4}{R_2 + R_4}}{\frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4}}$$
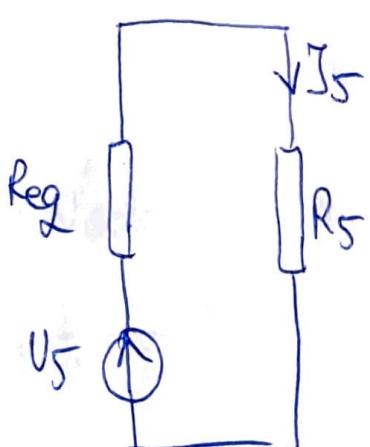
$$\text{Reg} = \frac{R_1 R_2 R_3 R_4}{R_1 R_3 (R_2 + R_4) + R_2 R_4 (R_1 + R_3)}$$




$$U_5 = Y_5 (\text{Reg} + R_5)$$

$$Y_5 = \frac{U_5}{\text{Reg} + R_5}$$

$$Y_5 = \frac{Y_2 R_2 - Y_4 R_4}{\frac{R_1 R_2 R_3 R_4}{R_1 R_3 (R_2 + R_4) + R_2 R_4 (R_1 + R_3)} + R_5}$$

2.38

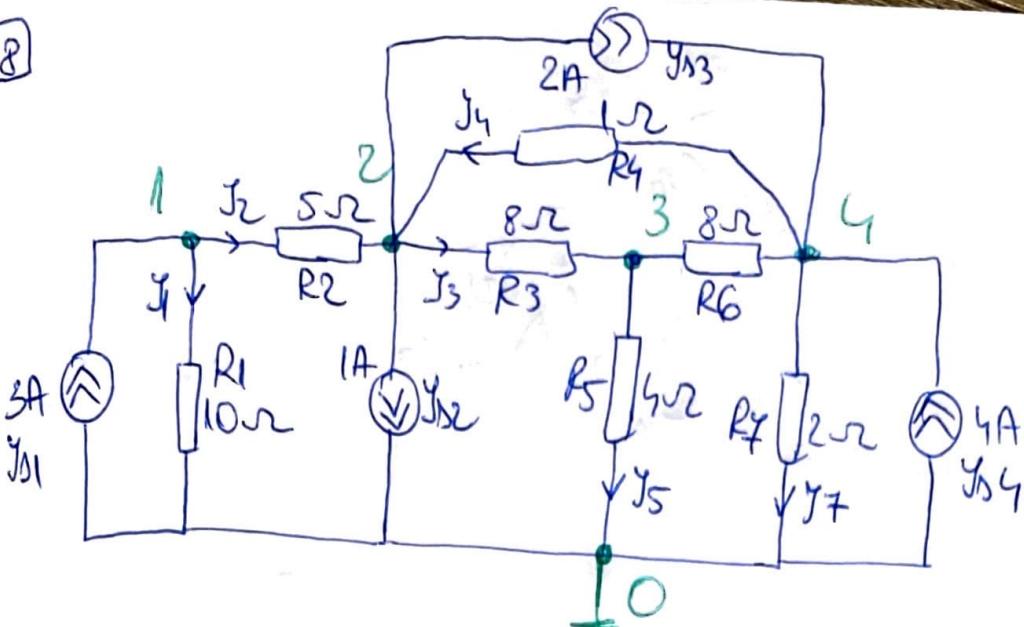

Let node 0 be the ground $\Rightarrow V_0 = 0V$

$$\begin{cases} V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \cdot \frac{1}{R_2} = J_{S1} \\ V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - V_1 \cdot \frac{1}{R_2} - V_3 \cdot \frac{1}{R_3} - V_4 \cdot \frac{1}{R_4} = -J_{S2} - J_{S3} \\ V_3 \left(\frac{1}{R_3} + \frac{1}{R_5} + \frac{1}{R_6} \right) - V_2 \cdot \frac{1}{R_3} - V_4 \cdot \frac{1}{R_6} = 0 \\ V_4 \left(\frac{1}{R_4} + \frac{1}{R_6} + \frac{1}{R_7} \right) - V_3 \cdot \frac{1}{R_6} - V_2 \cdot \frac{1}{R_7} = J_{S4} + J_{S3} \end{cases}$$

$$V_1 = 12.4V$$

$$V_2 = 3.69V$$

$$V_3 = 2.46V$$

$$V_4 = 6.15V$$

$$V_1 - V_0 = J_1 R_1 \Rightarrow J_1 = 1.24A$$

$$V_1 - V_2 = J_2 R_2 \Rightarrow J_2 = 1.45A$$

$$V_2 - V_3 = J_3 R_3 \Rightarrow J_3 = 0.15A$$


$$V_4 - V_2 = J_4 R_4 \Rightarrow J_4 = 2.46A$$

$$V_3 - V_0 = J_5 R_5 \Rightarrow J_5 = 0.61A$$

$$V_4 - V_3 = J_6 R_6 \Rightarrow J_6 = 0.61A$$

$$V_4 - V_0 = J_7 R_7 \Rightarrow J_7 = 3.07A$$

L.89

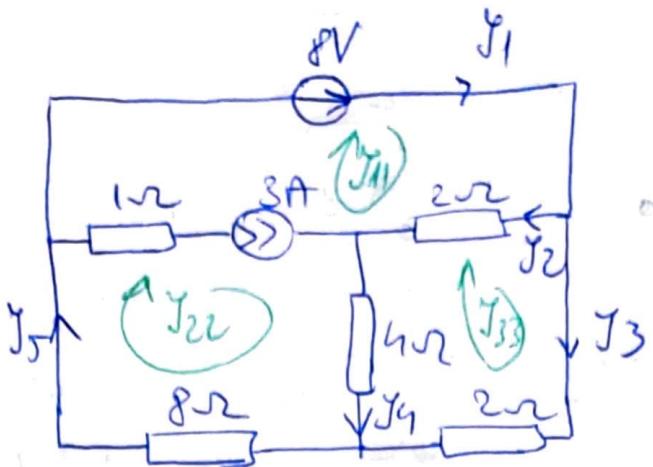

$$J_1 = J_{11}$$

$$J_2 = J_{11} - J_{33}$$

$$J_3 = J_{33}$$

$$J_4 = J_{22} - J_{33}$$

$$J_5 = J_{22}$$

$$8 = 2J_2 - 3 \Rightarrow J_2 = 5.5 \text{ A} \Rightarrow J_{11} - J_{33} = 5.5$$

$$0 = 3 + 4J_4 + 8J_5 \Rightarrow 0 = 3 + 4(J_{22} - J_{33}) + 8J_{22}$$

$$\Rightarrow 12J_{22} - 4J_{33} = -3$$

$$0 = 2J_3 - 4J_4 - 2J_2 \Rightarrow 0 = 2J_{33} - 4(J_{22} - J_{33}) - 2(\underbrace{J_{11} - J_{33}}_{5.5})$$

$$\Rightarrow 6J_{33} - 4J_{22} = 11$$

$$\begin{cases} 12J_{22} - 4J_{33} = -3 \\ 6J_{33} - 4J_{22} = 11 \end{cases} \Rightarrow J_{22} = 0.46 \text{ A}$$

$$J_{33} = 2.14$$

$$J_{11} = 7.64 \text{ A}$$


$$J_3 = 2.14 \text{ A}$$

$$J_4 = -1.67 \text{ A}$$

$$J_5 = 0.46 \text{ A}$$

$$J_1 = 7.64 \text{ A}$$

2.40

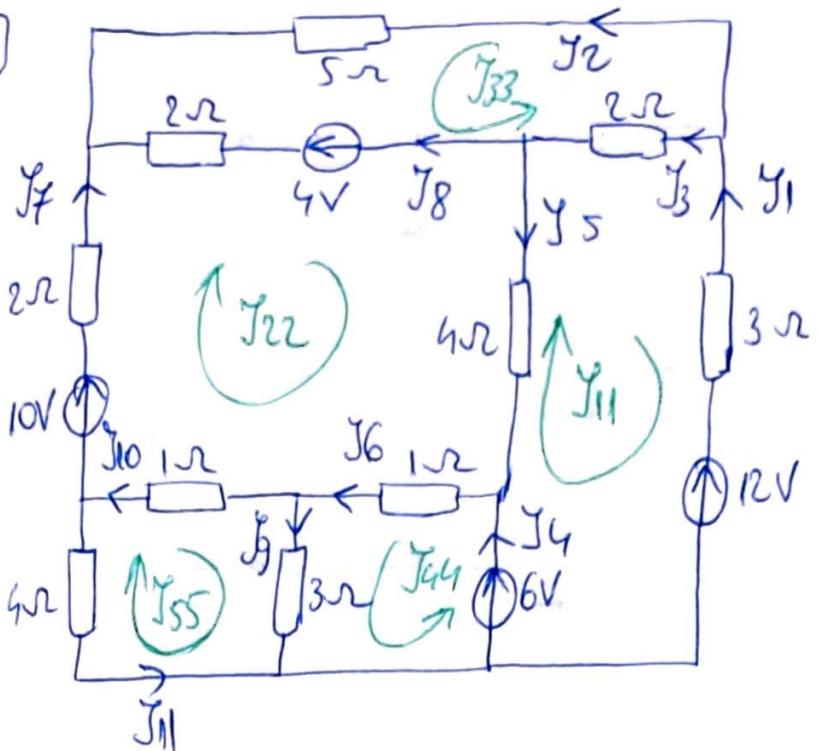

$$\begin{aligned}
 Y_1 &= -J_{11} \\
 Y_2 &= J_{33} \\
 Y_3 &= -J_{11} - J_{33} \\
 Y_4 &= J_{11} + J_{44} \\
 Y_5 &= J_{11} - J_{22} \\
 Y_6 &= J_{22} + J_{44} \\
 Y_7 &= J_{22} \\
 Y_8 &= -J_{22} - J_{33} \\
 Y_9 &= J_{44} + J_{55} \\
 J_{10} &= J_{22} - J_{55} \\
 J_{11} &= -J_{55}
 \end{aligned}$$

$$\text{mesh 1: } (4+2+3)J_{11} - 4J_{22} + 2J_{33} = 6 - 12$$

$$9J_{11} - 4J_{22} + 2J_{33} = -6$$

$$\text{mesh 2: } (1+1+2+2+4)J_{22} - 4J_{11} + 2J_{33} + J_{44} - J_{55} = 10 - 4$$

$$10J_{22} - 4J_{11} + 2J_{33} + J_{44} - J_{55} = 6$$

$$\text{mesh 3: } (2+2+5)J_{33} + 2J_{11} + 2J_{22} = -4$$

$$9J_{33} + 2J_{11} + 2J_{22} = -4$$

$$\text{mesh 4: } (3+1)J_{44} + J_{22} + 3J_{55} = 6$$

$$4J_{44} + J_{22} + 3J_{55} = 6$$

$$\text{mesh 5: } (4+1+3)J_{55} - J_{22} + 3J_{44} = 0$$

$$8J_{55} - J_{22} + 3J_{44} = 0$$

$$J_{11} = -0.4A$$

$$J_{22} = 0.2A$$

$$J_{33} = -0.3A$$

$$J_{44} = 1.9A$$

$$J_{55} = -0.4A$$

$$\Rightarrow$$

$$J_1 = 0.4A$$

$$J_2 = -0.3A$$

$$J_3 = 0.8A$$

$$J_4 = 1.4A$$

$$J_5 = -0.6A$$

$$J_6 = 2.1A$$

$$J_7 = 0.2A$$



$$J_8 = 0.1A$$

$$J_9 = 1.2A$$

$$J_{10} = 0.9A$$

$$J_{11} = 0.4A$$

2.41

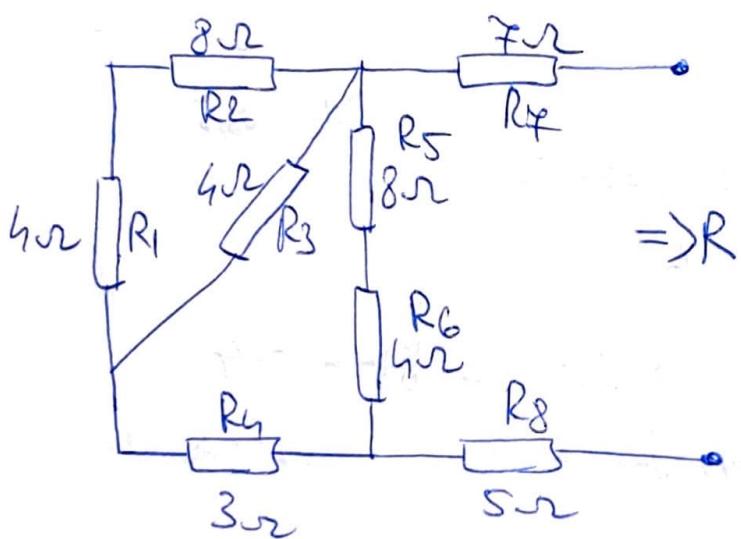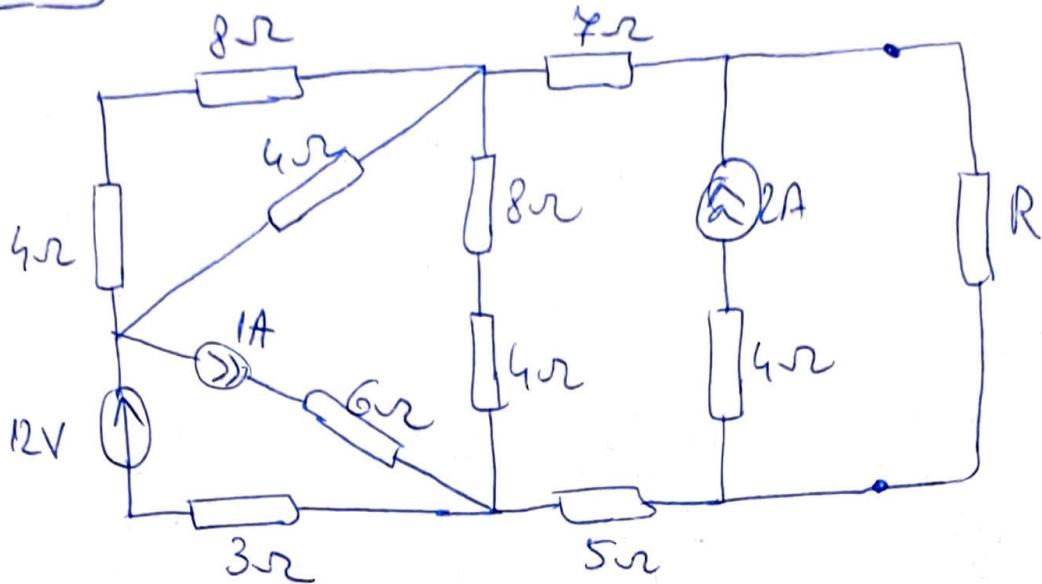

$$R_{S1} = R_1 + R_2 = 12\Omega$$

$$R_{P1} = \frac{R_{S1} R_3}{R_{S1} + R_3} = \frac{12 \cdot 4}{12 + 4} = 3\Omega$$


$$R_{S2} = R_{P1} + R_4 = 6\Omega$$

$$R_{S3} = R_5 + R_6 = 12\Omega$$

$$R_{P2} = \frac{R_{S2} R_{S3}}{R_{S2} + R_{S3}} = \frac{6 \cdot 12}{6 + 12} = 4\Omega$$

$$R = R_7 + R_{P2} + R_8 \Rightarrow R = 16\Omega$$

2.42

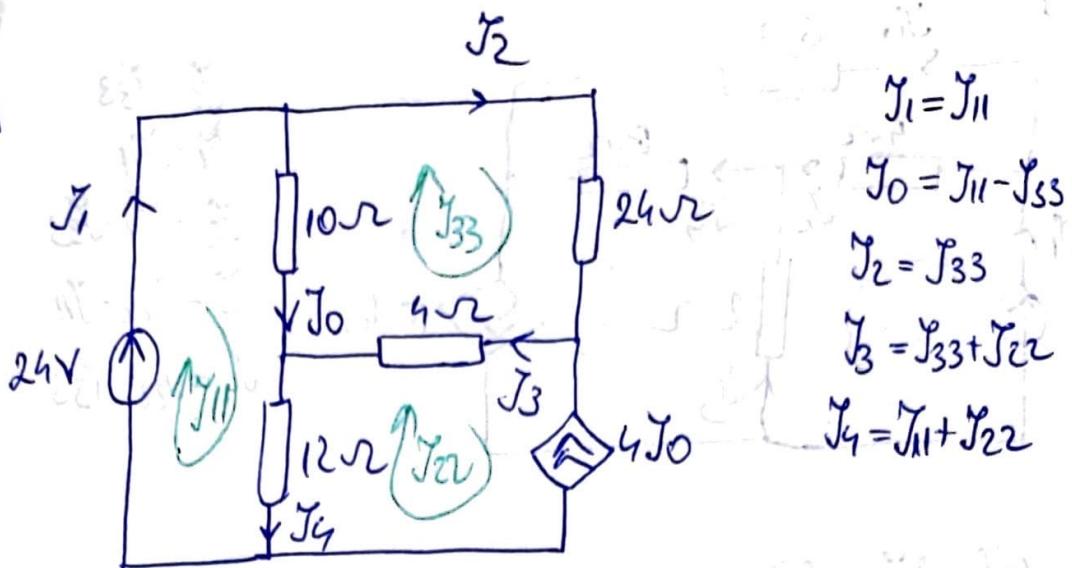

$$1: 24 = 10Y_0 + 12Y_4$$

$$24 = 10Y_{11} - 10Y_{33} + 12Y_{11} + 12Y_{22}$$

$$24 = 22Y_{11} + 12Y_{22} - 10Y_{33}$$

$$2: Y_{22} = 4Y_{11} - 4Y_{33}$$

$$4Y_{11} - Y_{22} - Y_{33} = 0$$

$$3: -10Y_{11} + 4Y_{22} + 38Y_{33} = 0$$

$$Y_{11} = 0.2A$$

$$Y_{22} = 1.4A$$

$$Y_{33} = -0.07A$$

$$Y_1 = 0.2A$$

$$Y_0 = 0.3A$$

$$Y_2 = -0.07A$$

$$Y_3 = 1.3A$$

$$Y_4 = 1.7A$$

$$0 = \tilde{J}_1^2 - \tilde{J}_0\tilde{J}_4 - \tilde{J}_3\tilde{J}_2$$

$$0 = (\tilde{J}_1^2 - \tilde{J}_0\tilde{J}_4)S + (\tilde{J}_1\tilde{J}_3 - \tilde{J}_0\tilde{J}_2)S$$

$$0 = \tilde{J}_1^2S - \tilde{J}_0\tilde{J}_4S + \tilde{J}_1\tilde{J}_3S - \tilde{J}_0\tilde{J}_2S$$

$$0 = (\tilde{J}_1^2 - \tilde{J}_0\tilde{J}_4)S + (\tilde{J}_1\tilde{J}_3 - \tilde{J}_0\tilde{J}_2)S$$

$$0 = \tilde{J}_1^2S - \tilde{J}_0\tilde{J}_4S + \tilde{J}_1\tilde{J}_3S - \tilde{J}_0\tilde{J}_2S$$

$$AB2 = \sqrt{2}$$

$$AP = \sqrt{2}$$

$$AE = \sqrt{2}$$


$$AC2 = \sqrt{2}$$

$$AE2 = \sqrt{2}$$

$$AS2 = \sqrt{2}$$

$$AT2 = \sqrt{2}$$

2.43

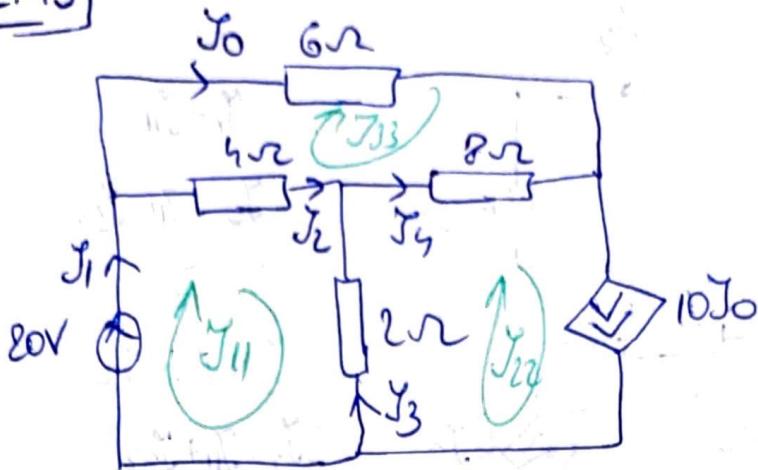

$$J_0 = J_{33}$$

$$J_1 = J_{11}$$

$$J_2 = J_{11} - J_{33}$$

$$J_3 = J_{22} - J_{11}$$

$$J_4 = J_{22} - J_{33}$$

$$1: 4J_2 - 2J_3 = 20$$

$$4(J_{11} - J_{33}) - 2(J_{22} - J_{11}) = 20$$

$$6J_{11} - 2J_{22} - 4J_{33} = 0$$

$$2: 2J_3 + 8J_4 = 0$$

$$2(J_{22} - J_{11}) + 8(J_{22} - J_{33}) = 0$$

$$-2J_{11} + 10J_{22} - 8J_{33} = 0$$

$$3: 6J_0 - 8J_4 - 4J_2 = 0$$

$$6J_{33} - 8(J_{22} - J_{33}) - 4(J_{11} - J_{33}) = 0$$

$$-4J_{11} - 8J_{22} + 18J_{33} = 0$$

$$J_{11} = 6.9 \text{ A}$$

$$J_{22} = 4 \text{ A}$$

$$J_{33} = 3.3 \text{ A}$$

$$J_0 = 3.3 \text{ A} = J_3$$


$$J_1 = 6.9 \text{ A}$$

$$J_2 = 3.5 \text{ A}$$

$$J_3 = -2.8 \text{ A}$$

$$J_4 = 0.7 \text{ A}$$

2.44

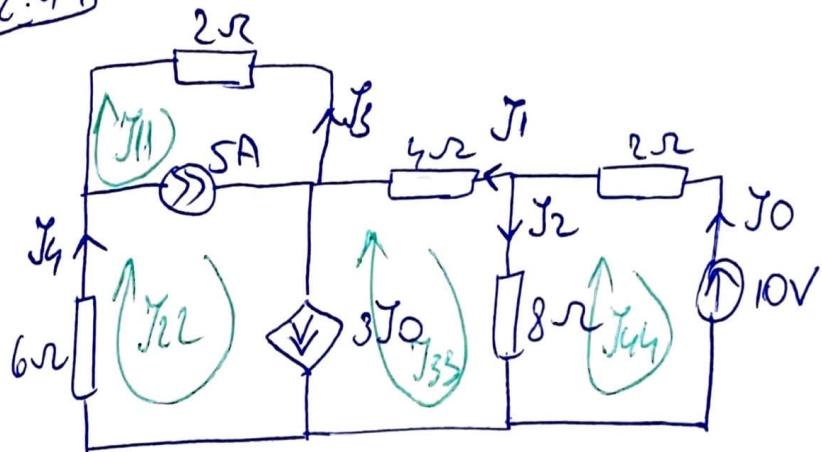

$$J_0 = -J_{44}$$

$$J_1 = -J_{33}$$

$$J_2 = J_{33} - J_{44}$$

$$J_3 = -J_{11}$$

$$J_4 = J_{22}$$

$$4: 2J_0 + 8J_2 = 0$$

$$8J_{33} - 10J_{44} = 10$$

$$3: 8J_2 - 4J_1 = 0$$

$$12J_{33} - 8J_{44} = 0$$

$$2: J_4 = 0A$$

$$1: J_3 = 0A$$

$$J_{22} = 0A$$

$$J_{11} = 0A$$

$$J_{33} = 0.4A$$

$$J_{44} = 0.6A$$

$$J_1 = -0.4A$$

$$J_0 = -0.6A$$

$$J_2 = -0.2A$$

AC Proposed Problems

3.1 $A(t) = 10 \sin(10\pi t - 45^\circ)$ $A(t) = a_m \sin(\omega t - \phi)$

$$= 10 \sin(10\pi t - \frac{\pi}{4})$$

$a_m = 10 \text{ V}$ \rightarrow amplitude

$A = \frac{a_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 \text{ V}$ \rightarrow rms value

$\omega = 10\pi \frac{\text{rad}}{\text{s}}$ \rightarrow angular frequency

$\omega = 2\pi f \Rightarrow 10\pi = 2\pi f \Rightarrow f = 5 \text{ Hz} \rightarrow$ frequency

$\omega = \frac{2\pi}{T} \Rightarrow T = \frac{2\pi}{\omega} = \frac{2\pi}{10\pi} \Rightarrow T = 0.2 \text{ s} \rightarrow$ period

$\phi = -45^\circ \rightarrow$ phase angle

3.2 $u_1(t) = 200\sqrt{2} \sin(5t + 30^\circ)$
 $u_2(t) = 50 \cos(5t)$

we use: $-\cos \alpha = \sin(\alpha - 90^\circ)$

$\cos \alpha = \sin(90^\circ - \alpha)$

$u_1(t) = 200\sqrt{2} \sin(5t + 30^\circ)$

$u_2(t) = 50 \sin(+5t + 90^\circ)$

$\phi_1 = 30^\circ ; \phi_2 = 90^\circ$

$\phi_{12} = \phi_1 - \phi_2 = 30^\circ - 90^\circ = -60^\circ$

$u_1(t)$ lags $u_2(t)$ by the angle of 60°

$u_2(t)$ leads $u_1(t)$ by the angle of 60°

3.3

$$j_1(t) = -4 \sin(41\pi t + 30^\circ)$$

$$j_2(t) = -2 \cos(41\pi t - 35^\circ)$$

$$j_1(t) = -4 \sin(41\pi t + 30^\circ) = 4 \sin(41\pi t + 30^\circ - 180^\circ) = 4 \sin(41\pi t - 150^\circ)$$

$$j_2(t) = 2 \sin(41\pi t - 35^\circ - 90^\circ) = 2 \sin(41\pi t - 125^\circ)$$

$$\varphi_1 = 150^\circ, \varphi_2 = 125^\circ$$

$$\varphi_{12} = \varphi_1 - \varphi_2 = 25^\circ > 0 \Rightarrow j_1(t) \text{ leads } j_2(t)$$

3.4 $(2 - j3)\text{mA} + j4\text{mA} \cdot jk = (+)i \leftarrow j^2 + 3j = 1$

$$j_1(t) = 2\sqrt{2} \sin(\omega t + 45^\circ) A$$

$$j_2(t) = 2\sqrt{2} \cos(\omega t - 45^\circ) A$$

$$i(t) = j_1(t) + j_2(t) = ??$$

$$j_1(t) = 2\sqrt{2} \sin(\omega t + 45^\circ) A \quad \left(\frac{\sqrt{2}}{2} = \frac{1}{2} \cdot \frac{\sqrt{2}}{\sqrt{2}} = \frac{1}{2} \right)$$

$$j_2(t) = 2\sqrt{2} \sin(\omega t - 45^\circ + 90^\circ) A \quad \left(\frac{\sqrt{2}}{2} = \left(\frac{1}{2} \cdot \frac{\sqrt{2}}{\sqrt{2}} \right) \right)$$

$$j(t) = 4\sqrt{2} \sin(\omega t + 45^\circ) A$$

3.5

$$u_1(t) = 20\sqrt{2} \sin(\omega t + 45^\circ) V$$

$$u_2(t) = -10\sqrt{2} \cos(\omega t - 30^\circ) V = 10\sqrt{2} \sin(\omega t - 120^\circ) V$$

$$u(t) = u_1(t) + u_2(t) = ??$$

$$U_1 = 20 \frac{\sqrt{2}}{2} + 20 \frac{\sqrt{2}}{2} j = 10\sqrt{2} + 10\sqrt{2} j$$

$$U_2 = 10 \cdot \left(-\frac{1}{2}\right) + 10 \cdot \left(-\frac{\sqrt{3}}{2}\right) j = -5 - 5\sqrt{3} j$$

$$U = U_1 + U_2 = 5(2\sqrt{2} - 1) + 5j(2\sqrt{2} - \sqrt{3})$$

3.6

a) $\underline{U} = -10 e^{j30^\circ} V$

b) $\underline{I} = 2\sqrt{2} (\cos 45^\circ - j \sin 45^\circ) A$

c) $\underline{I} = j(5 - j12) A$

a) $u(t) = -10\sqrt{2} \sin(\omega t + 30^\circ)$
 $= 10\sqrt{2} \sin(\omega t - 150^\circ)$

b) $i(t) = 2 \sin(\omega t - 45^\circ)$

c) $\underline{I} = 12 + 5j \Rightarrow i(t) = 13\sqrt{2} \sin(\omega t + \arctg \frac{5}{13})$

3.7

$$4i(t) + 8 \int i(t) dt - 3 \frac{di(t)}{dt} = 50\sqrt{2} \sin(2t + 75^\circ)$$

$$\frac{4}{\sqrt{2}} \underline{I} + \frac{8}{\sqrt{2}} \cdot \frac{1}{j} \underline{I} - \frac{3}{\sqrt{2}} 2j \cdot \underline{I} = 50 e^{j75^\circ}$$

$$\underline{I} \left(\frac{5}{\sqrt{2}} - \frac{10}{\sqrt{2}} j \right) = 50 e^{j75^\circ} \text{ (arctg 2)} \text{ As = (t+u)}$$

$$\underline{I} = \frac{50 e^{j75^\circ}}{\sqrt{\frac{125}{2}} e^{\arctg 2}} = \frac{10\sqrt{2}}{\sqrt{5}} e^{j(\frac{75^\circ}{2} + \arctg 2)}$$

$$\underline{I} = 5 e^{j120^\circ} \Rightarrow i(t) = 5\sqrt{2} \sin(2t + 120^\circ)$$

$$j20t + 120^\circ = j2t + 90^\circ - j$$

$$j2t + j2t - j(\frac{3}{2}) + 90^\circ - j = 0 \Rightarrow \omega = 50$$

$$[3.8] \quad 2\sqrt{2} \frac{d u(t)}{dt} + 5\sqrt{2} u(t) + 10\sqrt{2} \int u(t) dt = 50\sqrt{2} \sin(5t - 30^\circ)$$

$$2.5j \underline{U} + 5 \underline{U} + 10 \cdot \frac{1}{5j} \underline{U} = 50 e^{-j30^\circ}$$


$$\underline{U}(5+8j) = 50 e^{-j30^\circ}$$

$$\underline{U} = \frac{50 e^{-j30^\circ}}{\sqrt{89} \cdot e^{j \arctan \frac{8}{5}}} \Rightarrow u(t) = \frac{50\sqrt{2}}{\sqrt{89}} \sin(5t - 30^\circ + \arctan \frac{8}{5})$$

[3.9]

$$J(t) = ?$$

$$u_C(t) = ?$$

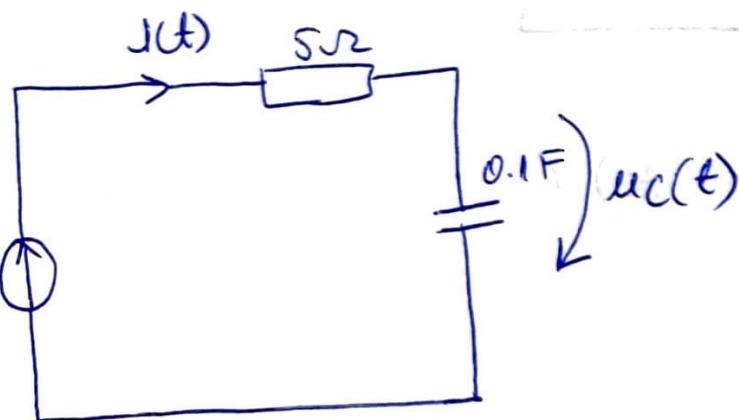

$$U_e(t) = 2 \cos 4t$$

$$U_e(t) = 2 \cos 4t \Rightarrow \omega = 4 \frac{\text{rad}}{\text{s}}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{4 \cdot 0.1} = 2.5 \Omega$$

$$Z = \sqrt{R^2 + (-X_C)^2} = \sqrt{5^2 + (-2.5)^2} = \frac{5\sqrt{5}}{2} \Omega = 5.6 \Omega$$


$$\tan \varphi = -\frac{X_C}{R} = -\frac{1}{2} \Rightarrow \varphi = \arctan(-\frac{1}{2})$$

$$i(t) = \frac{8\sqrt{5}}{5} \sin\left(4t + \arctg\left(-\frac{1}{2}\right)\right) A$$

$$U_{Cm} = i_m \cdot X_C = \frac{8\sqrt{5}}{5} \cdot \frac{5}{2} = 4\sqrt{5} \approx 9 V$$

$$u_C(t) = 4\sqrt{5} \sin\left(4t + \arctg\left(-\frac{1}{2}\right) - \frac{\pi}{2}\right)$$

3.10

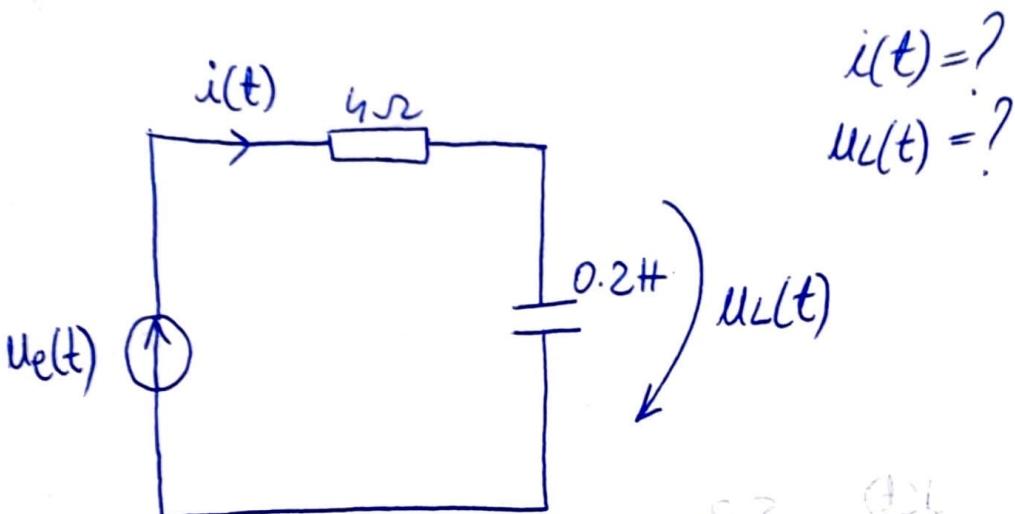

$$U_e(t) = 20 \cos(10t - 30^\circ) V$$

$$\omega = 10 \frac{\text{rad}}{\text{s}}$$

$$X_L = \omega L = 10 \cdot 0.2 \Rightarrow X_L = 2 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{4^2 + 2^2} = \sqrt{20} \Rightarrow Z = \sqrt{20} \Omega = 2\sqrt{5} \Omega$$

$$\tan \varphi = \frac{X_L}{R} = \frac{1}{2} \Rightarrow \varphi = \arctg\left(\frac{1}{2}\right)$$

$$I_m = Z \cdot i_m \Rightarrow I_m = \frac{20}{2\sqrt{5}} = \frac{10}{\sqrt{5}} = \frac{(10\sqrt{5})}{5} = 2\sqrt{5} A$$

$$i(t) = 2\sqrt{5} \sin\left(10t + \arctg\left(\frac{1}{2}\right) - 90^\circ\right) A$$

$$U_{Lm} = i_m \cdot X_L = 2\sqrt{5} \cdot 2 = 4\sqrt{5}$$

$$u_L(t) = 4\sqrt{3} \sin(10t + 123^\circ) V$$

3.11

sinusoidal current

at $t=0$, $I(0)=5 A$

$t_1=2.5 \text{ ms}$, peak value

$T=20 \text{ ms}$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{20} = \frac{\pi}{10}$$

a) $\varphi=?$

b) $I(t)=?$

• we will consider a sinusoidal current in the form:

$$I(t) = I_m \sin(\omega t + \varphi)$$

• peak value means $\sin(\omega t_1 + \varphi) = 1$ at $t_1 = 2.5 \text{ ms}$

$$\omega t_1 + \varphi = \frac{\pi}{2} \Rightarrow \varphi = \frac{\pi}{2} - \omega t_1 = \frac{\pi}{2} - \frac{\pi}{10} t_1 = \frac{\pi}{2} - \frac{2.5\pi}{10}$$

$$\Rightarrow \varphi = \frac{2.5\pi}{10} = \frac{\pi}{4} \Rightarrow \boxed{\varphi = 45^\circ}$$

• at $t=0$, $I(0)=5 A$

$$\Rightarrow 5 = I_m \sin \varphi \Rightarrow 5 = I_m \cdot \frac{\sqrt{2}}{2} \Rightarrow I_m = \frac{5 \cdot 2}{\sqrt{2}} = \frac{5 \cdot 2 \sqrt{2}}{2} = 5\sqrt{2} \text{ A}$$

$$\boxed{I(t) = 5\sqrt{2} \sin(314t + 45^\circ) \text{ A}}$$

3.12

$$f = 50 \text{ Hz}$$


$$i_m = 2,82 \text{ A}$$

$$R = 200 \Omega$$

$$C = 15,9 \mu\text{F}$$

$$\varphi_i = 0$$

a) $u(t) = ?$

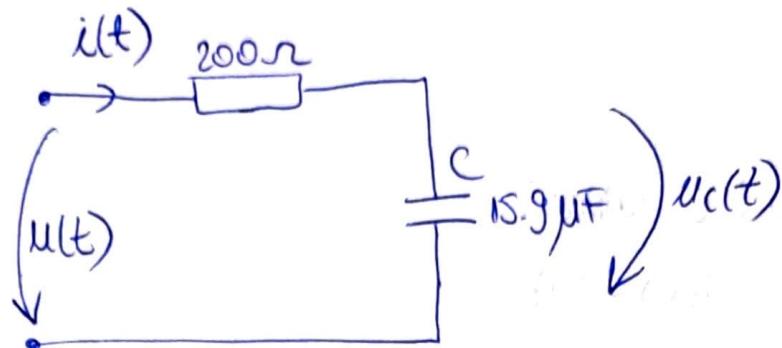

circuit impedance:

$$Z = \sqrt{R^2 + \left(-\frac{1}{\omega C}\right)^2}$$

b) $u_C(t) = ?$

$$\text{using } \omega = 2\pi f \Rightarrow \omega = 100\pi \frac{\text{rad}}{\text{s}}$$

$$Z = \sqrt{200^2 + \left(-\frac{1}{100\pi \cdot 15,9 \cdot 10^{-6}}\right)^2} = 283 \Omega$$

$$U_m = Z \cdot i_m \Rightarrow U_m = 283 \cdot 2,82 = 898 \text{ V}$$

$$\operatorname{tg} \varphi = -\frac{X_C}{R} = -\frac{200}{200} \Rightarrow \operatorname{tg} \varphi = -1 \Rightarrow \varphi = -45^\circ$$

$$u(t) = 898 \sin(100\pi t - \frac{\pi}{4}) \text{ V}$$

$$U_{Cm} = i_m \cdot \frac{1}{\omega C} = 2,82 \cdot 200 = 564 \text{ V}$$

$$u_C(t) = 564 \sin(100\pi t - \frac{\pi}{2})$$

3.13

$$R = 20 \Omega$$

$$L = 200 \text{ mH}$$

$$U_L(t) = 200 \sin(314t - 60^\circ)$$

a) $i(t) = ?$

b) $u(t) = ?$

$$U_{Lm} = 200 \text{ V}$$

$$\omega = 100\pi \frac{\text{rad}}{\text{s}} = 314 \frac{\text{rad}}{\text{s}}$$

$$U_{Lm} = Im \cdot XL$$

$$XL = \omega L = 100\pi \cdot 200 \cdot 10^{-3} \Rightarrow XL = 20\pi \Omega$$

$$Im = \frac{U_{Lm}}{XL} = \frac{200}{20\pi} = \frac{10}{\pi} = 3.2 \text{ A}$$

$$i(t) = 3.2 \sin(100\pi t - 60^\circ - 90^\circ) \text{ A}$$

$$= 3.2 \sin(100\pi t - 150^\circ) \text{ A}$$

$$Z = \sqrt{R^2 + (XL)^2} = \sqrt{R^2 + X_L^2} = \sqrt{20^2 + (20\pi)^2} = 66 \Omega$$

$$U_m = Z \cdot Im = 66 \cdot 3.2 = 211.2 \text{ V}$$

$$\tan \varphi = \frac{XL}{R} = \frac{20\pi}{20} \Rightarrow \tan \varphi = \pi \Rightarrow \varphi = \arctan(\pi) = 72^\circ$$

$$u(t) = 211.2 \sin(100\pi t - 60^\circ + 72^\circ)$$

$$= 211.2 \sin(100\pi t + 12^\circ)$$

3.14

$$R = 20 \Omega$$

$$L = 40 \text{ mH}$$

$$C = 50 \mu\text{F}$$

$$U(t) = 200 \sin(1000t - 30^\circ) \text{ V}$$


$$\text{a) } X_L, X_C, Z = ?$$

$$\text{b) } \mathcal{I} = ? \quad i(t) = ?$$

$$\text{c) } U_R = ? \quad u_R(t) = ?$$

$$\text{d) } U_L = ? \quad u_L(t) = ?$$

$$\text{e) } U_C = ? \quad u_C(t) = ?$$

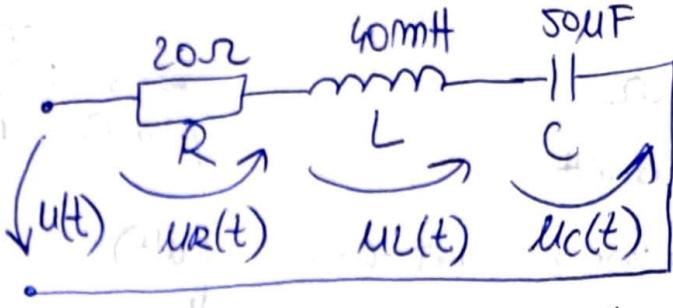

$$\text{a) } \omega = 1000 \frac{\text{rad}}{\text{s}}$$

$$X_L = \omega L = 1000 \cdot 40 \cdot 10^{-3} = 40 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000 \cdot 50 \cdot 10^{-6}} = 20 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{20^2 + 20^2} = 20\sqrt{2} \Omega = 28.3 \Omega$$

$$\text{b) } \mathcal{I} = \frac{U_m}{Z} = \frac{200}{20\sqrt{2}} = 5 \text{ A}$$

$$\tan \varphi = \frac{X_L - X_C}{R} = 1 \Rightarrow \varphi = \arctan(1) = \frac{\pi}{4}$$

because $X_L > X_C$ circ. behaves inductively, so

the current lags the voltage by $\varphi = \frac{\pi}{4}$

$$i(t) = 5\sqrt{2} \sin(1000t - 30^\circ - 45^\circ) = 5\sqrt{2} \sin(1000t - 75^\circ) \text{ A}$$

$$\text{c) } U_R = \mathcal{I} \cdot R = 100 \text{ V}$$

$$u_R(t) = 100\sqrt{2} \sin(1000t - 75^\circ) \text{ V}$$

$$\text{d) } U_L = X_L \cdot \mathcal{I} = 200 \text{ V}$$

$$u_L(t) = 200\sqrt{2} \sin(1000t - 75^\circ + 90^\circ) \text{ V}$$

$$= 200\sqrt{2} \sin(1000t + 15^\circ) \text{ V}$$

$$\text{e) } U_C = X_C \cdot \mathcal{I} = 100 \text{ V}$$

$$u_C(t) = 100\sqrt{2} \sin(1000t - 75^\circ - 90^\circ) = 100\sqrt{2} \sin(1000t - 165^\circ) \text{ V}$$


3.15

$$R = 30 \Omega$$

$$X_L = \omega L = 80 \Omega$$

$$X_C = \frac{1}{\omega C} = 40 \Omega$$
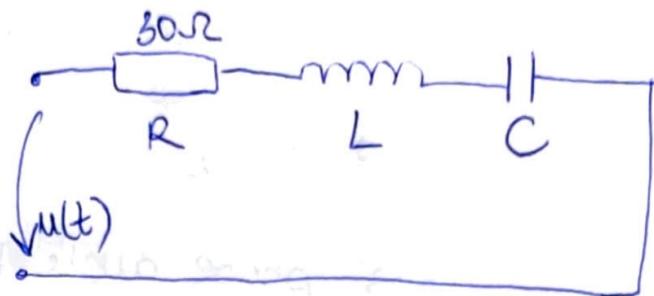
$$u(t) = 100\sqrt{2} \sin(100\pi t - 60^\circ) V$$



$$\omega = 100\pi \frac{\text{rad}}{\text{s}}$$


a) $Z = ?$ $I = ?$

b) $\underline{Y} = ?$ $i(t) = ?$

c) $P = ?$ $Q = ?$ $S = ?$

verify cons. of active, reactive, power


circuit in phasor form:

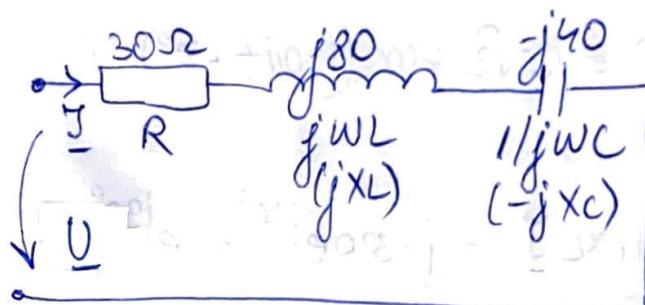

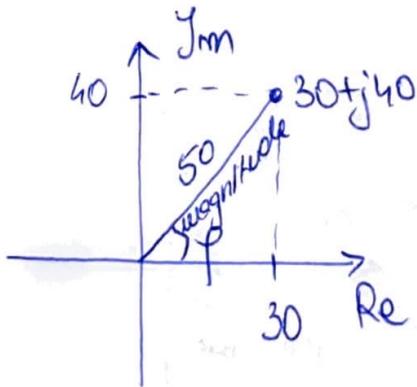d) $\underline{U} = 100 e^{j60^\circ}$

$$\underline{U} = \underline{YR} + j\underline{XL}\underline{Y} - j\underline{XC}\underline{Y} \Rightarrow \underline{Y} = \frac{\underline{U}}{R + j(X_L - X_C)} = \frac{100}{30 + j40} \Omega$$

$$\underline{Y} = \frac{100 e^{j60^\circ}}{30 + j40}$$



$$\operatorname{tg} \varphi = \frac{40}{30}$$

$$\varphi = \arctg\left(\frac{4}{3}\right) = 53^\circ$$

$$\text{so } 30 + j40 = 50 e^{j53^\circ}$$

$$\underline{Y} = \frac{100 e^{j60^\circ}}{50 e^{j53^\circ}} = 4 e^{j7^\circ} \Rightarrow \underline{Y} = 4 \Omega$$

$$i(t) = 4\sqrt{2} \sin(100\pi t + 7^\circ) A$$

$$a) \underline{Z} = R + j(X_L - X_C) = 30 + j40 = 50 e^{j53^\circ}$$

$$\Rightarrow Z = 50 \Omega$$

$\varphi = 53^\circ$ phase angle introduced by the impedance

$$c) U_R = I_R = 120 e^{j7^\circ} \Rightarrow U_R = 120 V$$

$$U_R(t) = 120\sqrt{2} \sin(100\pi t + 7^\circ) V$$

$$U_L = jX_L I = j \cdot 320 e^{j7^\circ} = e^{j90^\circ} \cdot 320 \cdot e^{j7^\circ} = 320 e^{j97^\circ}$$

$$j = e^{j90^\circ}$$

$$U_L = 320 V$$

$$U_L(t) = 320\sqrt{2} \sin(100\pi t + 97^\circ) V$$

$$U_C = -jX_C I = -j160 e^{j7^\circ} = e^{-j90^\circ} \cdot 160 \cdot e^{j7^\circ} = 160 e^{j83^\circ}$$

$$-j = e^{-j90^\circ}$$

$$U_C = 160 V$$

$$U_C(t) = 160\sqrt{2} \sin(100\pi t - 83^\circ) V$$

$$d) u(t) = 100\sqrt{2} \sin(100\pi t - 60^\circ) V$$

$$i(t) = 4\sqrt{2} \sin(100\pi t + 47^\circ) A$$

Active power:

$$P = U I \cos(\varphi_U - \varphi_I) = 100 \cdot 4^{\circ} (-60 - 7) = 400 \cos(-67^{\circ})$$

$$P = 156.3 \text{ W}$$

Reactive power:

$$Q = U I \sin(\varphi_U - \varphi_I) = 400 \sin(-67^{\circ})$$

$$Q = 368.2 \text{ VAR}$$

Apparent power:

$$S = U I = 400 \text{ VA}$$

3.16


$$R = 10 \Omega$$

$$X_L = \omega L = 5 \Omega$$

$$X_C = \frac{1}{\omega C} = 15 \Omega$$


$$U_1(t) = 100\sqrt{2} \sin(100\pi t) \text{ V}$$

$$U_2(t) = ?$$

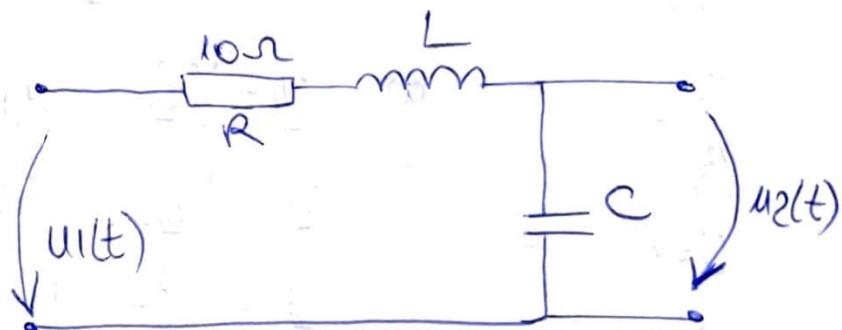

$$\underline{U}_1 = 100 e^{j \cdot 0^{\circ}} = 100 e^0$$
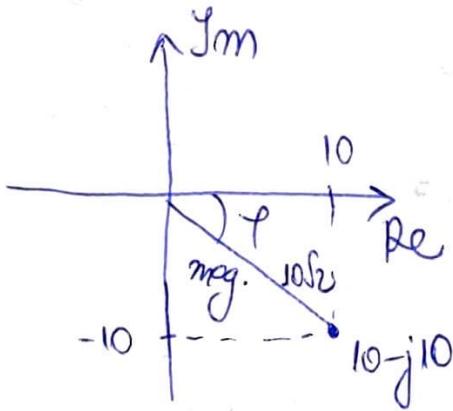
$$\underline{Z} = R + j(X_L - X_C) = 10 - j10$$



$$\operatorname{tg} \varphi = -1 \Rightarrow \varphi = -45^{\circ}$$

$$\underline{Z} = 10\sqrt{2} e^{-j45^{\circ}}$$

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} = \frac{100 e^0}{10\sqrt{2} e^{-j45^{\circ}}} \\ \underline{I} = 5\sqrt{2} e^{j45^{\circ}}$$

$$\underline{U}_2 = \underline{I} (-jX_C) = 75\sqrt{2} e^{-j45^\circ}$$

$$\Rightarrow U_2(t) = 75\sqrt{2}\sqrt{2} \sin(100\pi t - 45^\circ) V \\ = 150 \sin(100\pi t - 45^\circ) V$$

3.17

$$\underline{Z}_1 = 3+j4$$

$$\underline{Z}_2 = -j6$$

$$\underline{Z}_3 = 6+j8$$

$$I = 2A$$

$$a) \underline{U}_1 = ?$$

$$\underline{U}_2 = ?$$

$$\underline{U}_3 = ?$$


$$b) \underline{U} = ?$$

$$u(t) = ?$$

$$c) P = ?$$

$$Q = ?$$

$$S = ?$$

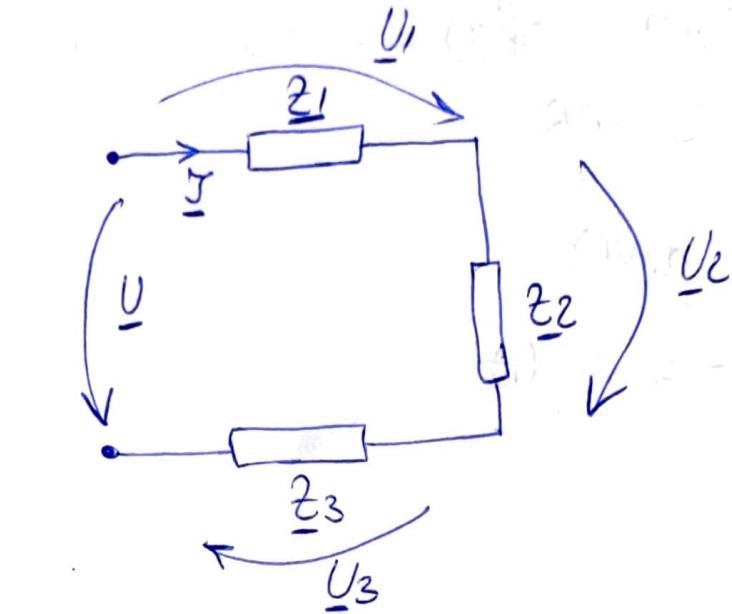


$$a) \underline{U}_1 = Y \underline{Z}_1 = 6 + j8 \Rightarrow U_1 = 10V$$

$$\underline{U}_2 = Y \underline{Z}_2 = -j12 \Rightarrow U_2 = 12V$$

$$\underline{U}_3 = Y \underline{Z}_3 = 12 + j16 \Rightarrow U_3 = 20V$$


$$b) \underline{U} = Y(\underline{Z}_1 + \underline{Z}_2 + \underline{Z}_3)$$
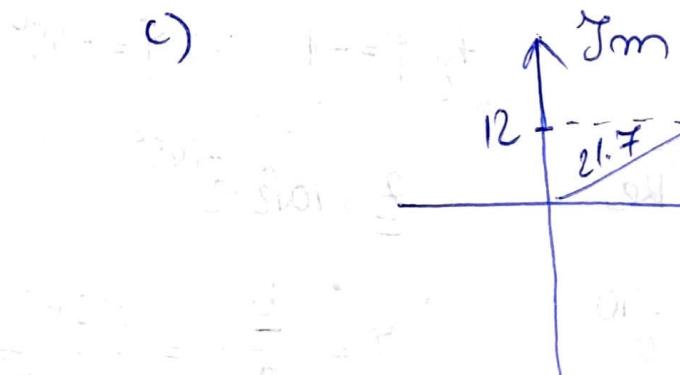
$$= 2(3 + j4 - j6 + 6 + j8) = 2(9 + j6) \\ = 18 + j12 \Rightarrow U = 21.7V \quad \checkmark$$



$$\operatorname{tg} \varphi = \frac{12}{18} = \frac{2}{3} \\ = 33^\circ$$

$$\underline{U} = 21.7 e^{j33^\circ}$$

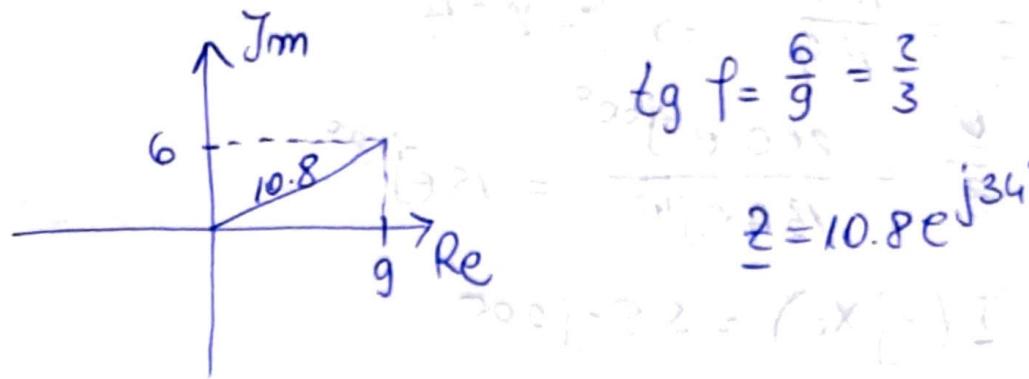

$$\operatorname{tg} \varphi = \frac{6}{9} = \frac{2}{3}$$

$$z = 10.8 e^{j34^\circ}$$

$$P = U_0 I \cos(\varphi_U - \varphi_I) = 43.4 \cos 34^\circ$$

$$Q = U_0 I \sin(\varphi_U - \varphi_I) = 43.4 \sin 34^\circ$$

$$S = U_0 I$$



B.18

$$R = 10 \Omega$$

$$L = \frac{3}{10\pi} H$$

$$C = \frac{1}{2.1\pi} mF$$

$$U_e(t) = 100\sqrt{2} \sin(100\pi t - 60^\circ) V$$

$$\omega = 100\pi \frac{\text{rad}}{\text{s}}$$

$$\text{a)} Z = ?$$

$$X_L = \omega L = 100\pi \cdot \frac{3}{10\pi} = 30 \Omega$$

$$\text{b)} Y = ?$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \cdot \frac{1}{2.1\pi}} = 21 \Omega$$


$$\text{c)} U_L(t) = ?$$

$$Z = R + j(X_L - X_C) = 10 + j \cdot 9 \Omega$$

$$\text{d)} P = ?$$

$$Q = ?$$

$$S = ?$$

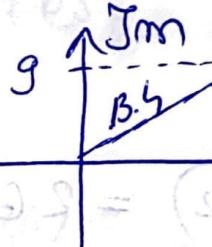

$$\operatorname{tg} \varphi = \frac{9}{10} \Rightarrow \varphi = 42^\circ$$

$$Z = 13.4 \Omega$$

$$b) \underline{I} = \frac{\underline{U}}{Z} = \frac{100}{13.4} \Rightarrow I = 7.5 A$$

$$c) \underline{I} = \frac{\underline{U}}{Z} = \frac{200 e^{-j60^\circ}}{13.4 e^{j42^\circ}} = 15 e^{-j18^\circ}$$

$$\underline{U}_C = \underline{I} (-jX_C) = 5.5 - j0.05$$

$$\underline{U}_L = \underline{U} - \underline{U}_C = 44.5 + j18$$

$$U_L(t) = 48\sqrt{2} \sin(100\pi t + 22^\circ) V$$

3.19

$$R = 8 \Omega$$

$$X_{L1} = \omega L_1 = 2 \Omega$$

$$X_{L2} = \omega L_2 = 1 \Omega$$

$$X_C = \frac{1}{\omega C} = 40 \Omega$$

$$U_e(t) = 100\sqrt{2} \sin(100\pi t - 60^\circ) V$$

$$a) Z = ? \quad \underline{Z} = ?$$

$$b) \underline{I} = ?$$

$$c) U_{L2}(t) = ? \quad \text{Ansatz: } U = j\omega X$$

$$d) P = ? = \frac{1}{R + j(X_L + X_C)} = \frac{1}{37.9} = jX \quad Z = 37.9 \Omega$$

$$Q = ?$$

$$S = ? \cdot j + 0 = (37.9 - jX) j + 0 = ?$$


$$e) \underline{I} = \frac{100 e^{-j60^\circ}}{37.9 e^{j78^\circ}}$$

$$\underline{I} = 2.6 e^{j18^\circ}$$

$$I = 2.6 A$$

$$f) \underline{U}_{L2} = \underline{I} (-jX_{L2}) = 2.6 e^{j18^\circ} - j \cdot 1 = 2.6 e^{j18^\circ} + e^{-j90^\circ}$$
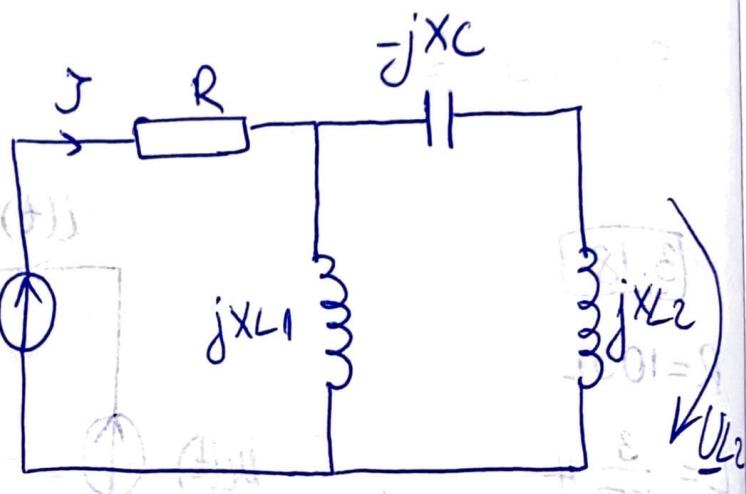
$$= 2.6 e^{j72^\circ} \Rightarrow U_{L2}(t) = 2.6\sqrt{2} \sin(100\pi t - 72^\circ) V$$



3.20

$$R = 15 \Omega$$

$$XL = \omega L = 30 \Omega$$

$$XM = \omega M = 20 \Omega$$


$$XC = \frac{1}{\omega C} = 50 \Omega$$

$$u(t) = 100\sqrt{2} \sin(100\pi t + 60^\circ) V$$

a) $\underline{Z} = ?$ $\underline{z} = ?$

b) $\underline{Y} = ?$ $i(t) = ?$

c) $U_L = ?$ $u_L(t) = ?$

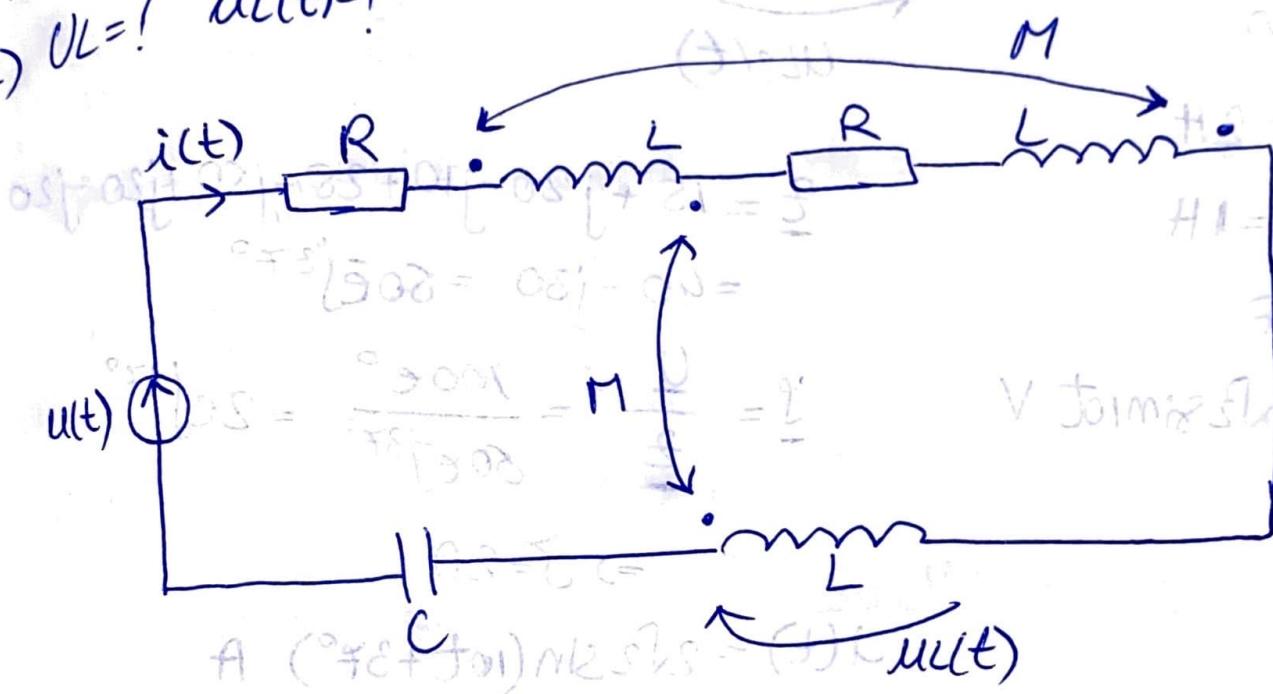

a) $\underline{Z} = 15 + j30 + j20 + (15 + j30 - j20 + j30 - j20)(j50) / 2 = 36 \Omega$

$$= 36 - j20$$

$$\underline{Z} = 36 \Omega$$

b) $\underline{Y} = \frac{1}{\underline{Z}} = \frac{100e^{j60^\circ}}{36e^{j34^\circ}} = 2.7e^{j26^\circ}$

$$y = 2.7 A$$

$$i(t) = 2.7\sqrt{2} \sin(100\pi t + 26^\circ) A$$

$$c) \underline{U_L} = \underline{I} (jX_L) = 2\sqrt{2} e^{j26^\circ} \cdot j30 = 83.2 e^{j116^\circ}$$

$$\Rightarrow U_{L2}(t) = 83.2 \sqrt{2} \sin(100\pi t + 116^\circ) V$$

3.21

$\underline{Y} = ?$

$U_{L2}(t) = ?$

$$R_1 = 15 \Omega$$


$$R_2 = 25 \Omega$$

$$L_1 = L_2 = 2 H$$

$$L_{12} = M = 1 H$$

$$C = 2 \mu F$$

$$U(t) = 100\sqrt{2} \sin(10t) V$$

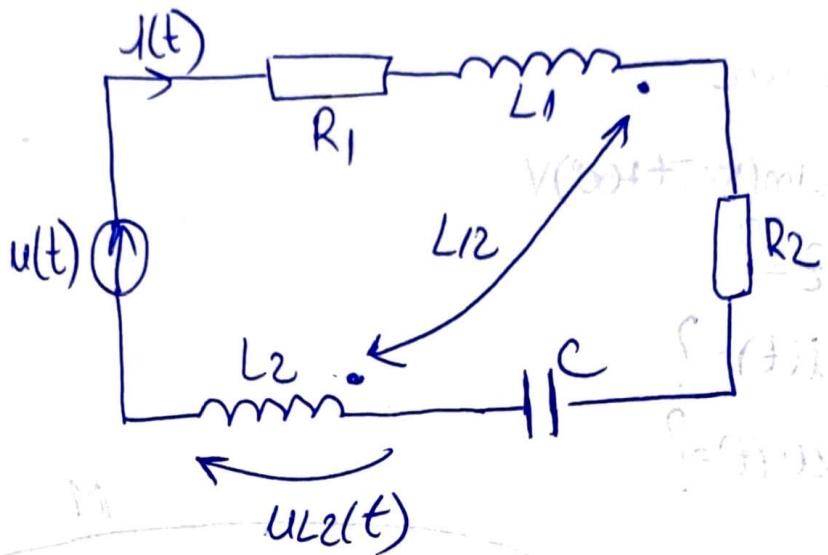

$$\underline{Z} = 15 + j20 - j10 + 25 - j50 + j20 - j20 \\ = 40 - j30 = 50 e^{-j37^\circ}$$

$$\underline{Y} = \frac{\underline{U}}{\underline{Z}} = \frac{100 e^{j0^\circ}}{50 e^{-j37^\circ}} = 2 e^{j37^\circ}$$

$$\Rightarrow J = 2 A$$

$$i(t) = 2\sqrt{2} \sin(10t + 37^\circ) A$$

$$U_{L2} = \underline{Y} (-jX_{L2} - j\omega M) = 2 e^{j37^\circ} (20 e^{j90^\circ} - 10 e^{-j90^\circ}) \\ = 20 e^{j127^\circ}$$

$$U_{L2}(t) = 20\sqrt{2} \sin(10t + 127^\circ) V$$

(B22)

$$i_1(t) = ?$$

$$U_2 = ?$$

$$R = 40 \Omega$$

$$X_{L1} = X_{L2} = 60 \Omega$$

$$X_M = 30 \Omega$$

$$X_C = 20 \Omega$$

$$U_1(t) = 400 \sin(50t - 30^\circ) V$$


$$\underline{U}_1 = 400\sqrt{2} e^{-j30^\circ}$$

$$\underline{Z} = 40 - j20 + j60 = 40 + j40 = 40\sqrt{2} e^{j45^\circ}$$

$$\underline{I}_1 = \frac{\underline{U}_1}{\underline{Z}} = \frac{400\sqrt{2} e^{-j30^\circ}}{40\sqrt{2} e^{j45^\circ}} = 10e^{-j75^\circ}$$

$$i_1(t) = 10\sqrt{2} \sin(50t - 75^\circ) A$$
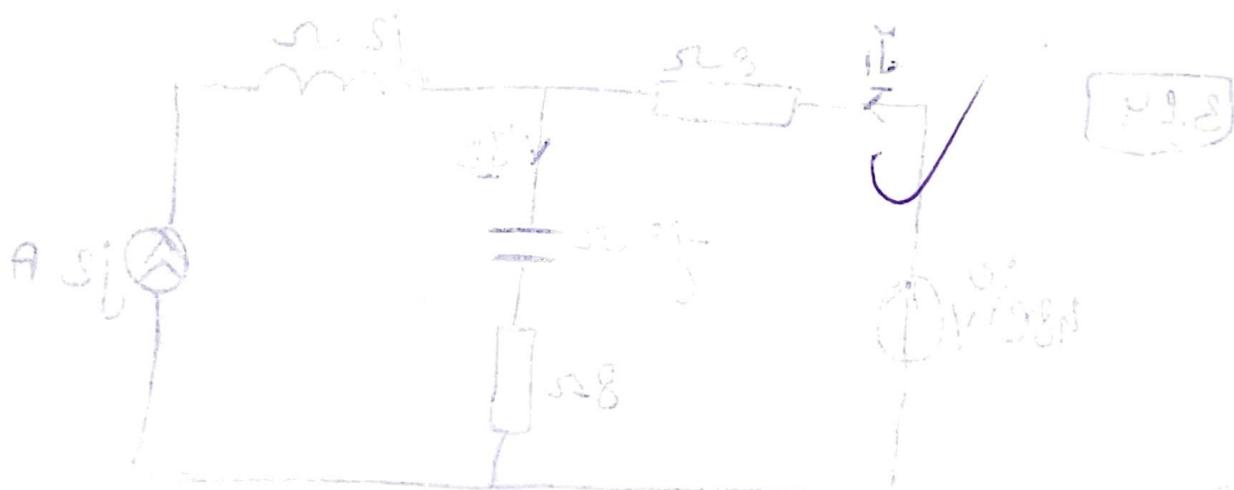
$$U_2 = \underline{U}_{L2} = 30 e^{j90^\circ} \cdot 10 e^{-j75^\circ} = 300 e^{j15^\circ} \Rightarrow U_2 = 300 V$$



$$S = 3$$

$$JS + S = J^2$$

$$J^2 + 16 = 36$$

$$J^2 = 20 \quad (J = \sqrt{20})$$

3.23

$$R_1 = R_2 = 50 \Omega$$


$$XL_1 = \omega L_1 = 10 \Omega$$

$$XL_2 = \omega L_2 = 40 \Omega$$

$$XM = \omega M = 20 \Omega$$

$$XC_1 = \frac{1}{\omega C} = 30 \Omega$$
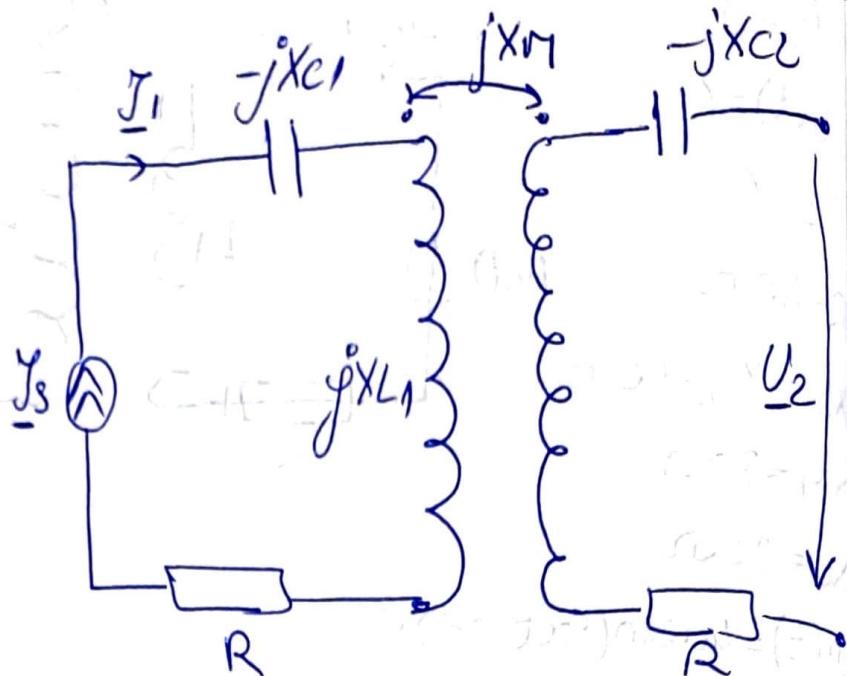
$$XC_2 = \frac{1}{\omega C} = 10 \Omega$$



$$i_s(t) = 3\sqrt{2} \sin(100\pi t + 30^\circ) V$$

$$\text{a)} \underline{U}_{L_1} = ?$$

$$\text{a)} \underline{I}_s = 3e^{j30^\circ}$$

$$\text{b)} \underline{U}_2(t) = ?$$


$$\underline{U}_{L_2} = 3e^{j30^\circ} \cdot 10e^{j90^\circ}$$

$$= 30e^{j120^\circ} \Rightarrow \underline{U}_{L_1} = \underline{I}_s$$

$$\text{c)} \underline{U}_{L_2} = \underline{U}_2 = \underline{I}_s - jXC_2 = 90e^{j120^\circ}$$

$$U_2(t) = 90\sqrt{2} \sin(100\pi t + 120^\circ)$$

3.24

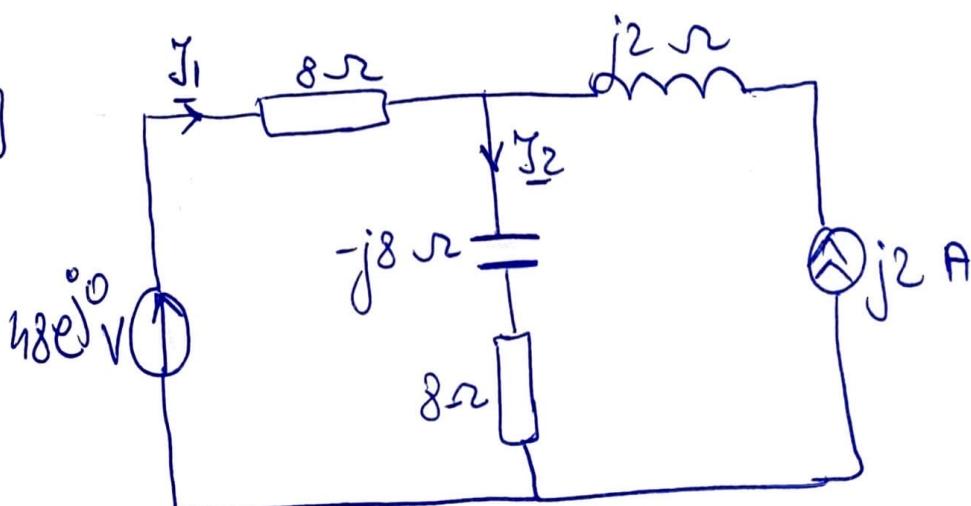

$$\left\{ \begin{array}{l} \underline{I}_2 = \underline{I}_1 + j2 \\ 8\underline{I}_1 + (-j8 + 8)\underline{I}_2 = 48 \end{array} \right.$$

$$\Rightarrow \begin{aligned} \underline{I}_1 &= 2 \\ \underline{I}_2 &= 2 + 2i \end{aligned}$$

B25

$$u(t) = 200\sqrt{2} \sin(500t - 30^\circ) V$$

$$i(t) = 5 \sin(500t + 60^\circ) A$$

$$\underline{U} = ? \quad \underline{I} = ?$$

$$\underline{Z} = ? \quad Z = ?$$

$$P = ? \quad Q = ?$$

$$\underline{U} = 200 e^{-j30^\circ} V$$

$$\underline{I} = \frac{5}{\sqrt{2}} e^{j60^\circ} A$$

$$\underline{Z} = \frac{\underline{U}}{\underline{I}} = \frac{200 e^{-j30^\circ}}{\frac{5}{\sqrt{2}} e^{j60^\circ}} = 40\sqrt{2} e^{-j90^\circ} \Rightarrow Z = 40\sqrt{2} \Omega$$


$$P = U \cdot I \cos(\phi_U - \phi_I) = 200 \cdot \frac{5}{\sqrt{2}} \cos(-30^\circ - 60^\circ)$$

$$= 200 \cdot \frac{5}{\sqrt{2}} \cdot 0 \Rightarrow P = 0 W$$

$$Q = U \cdot I \sin(\phi_U - \phi_I) = 200 \cdot \frac{5}{\sqrt{2}} \sin 90^\circ = -200 \cdot \frac{5}{\sqrt{2}}$$

$$= -500\sqrt{2} \text{ VAR}$$

$$\Delta V_{AC} = E \cdot n = 2$$

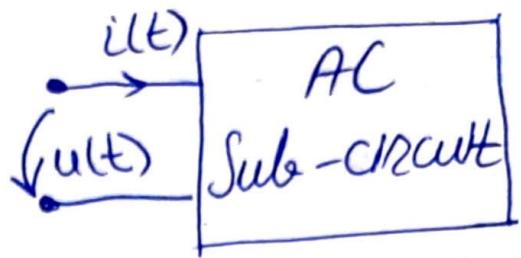

3.26


$$u(t) = 100 \sin(100\pi t + 30^\circ) V$$

$$i(t) = 2 \cos 100\pi t A$$

a) $\underline{U} = ? \quad \underline{J} = ?$

b) $\underline{Z} = ? \quad Z = ?$

c) $P = ? \quad Q = ? \quad S = ?$

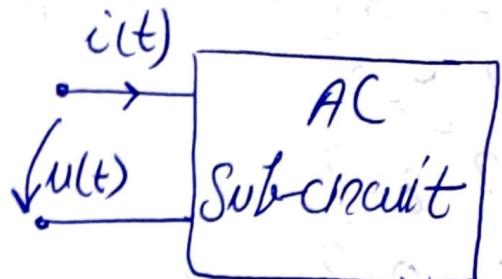

$$\underline{U} = 50\sqrt{2} e^{j30^\circ}$$

$$\underline{J} = \sqrt{2} e^{j0^\circ} \leftarrow \frac{50\sqrt{2} \cos 30^\circ}{50\sqrt{2} \sin 30^\circ} = \frac{\sqrt{3}}{1} = j\sqrt{3}$$

$$\underline{Z} = \frac{\underline{U}}{\underline{J}} = \frac{50\sqrt{2} e^{j30^\circ}}{\sqrt{2} e^{j0^\circ}} = 50 e^{j30^\circ} = 50 \cos 30^\circ + j50 \sin 30^\circ = 43.3 + j43.3 \Omega$$


$$\Rightarrow Z = 50 \Omega$$

$$P = U \cdot J \cos 30^\circ = 50\sqrt{2} \cdot \sqrt{2} \cdot \frac{\sqrt{3}}{2} = 50\sqrt{3} W$$

$$Q = U \cdot J \sin 30^\circ = 50\sqrt{2} \cdot \sqrt{2} \cdot \frac{1}{2} = 50 \text{ VAR}$$


$$S = U \cdot J = 100 \text{ VA}$$

3.27
 $N = 50 \frac{\text{rad}}{\Delta}$

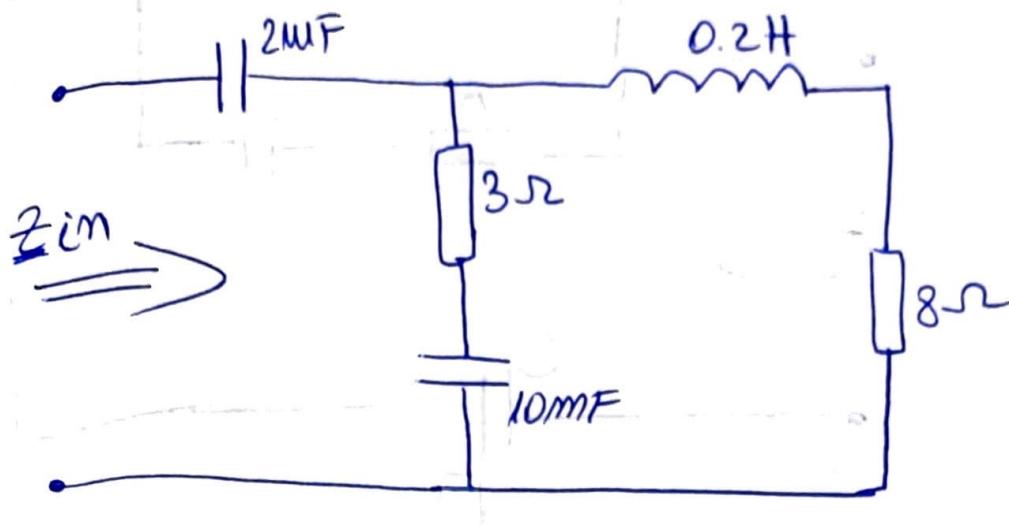

$$\underline{Z}_{in} = j20 + \frac{(3-j2)(8+j20)}{3-j2+8+j90} = 3.2 + j12$$

3.28

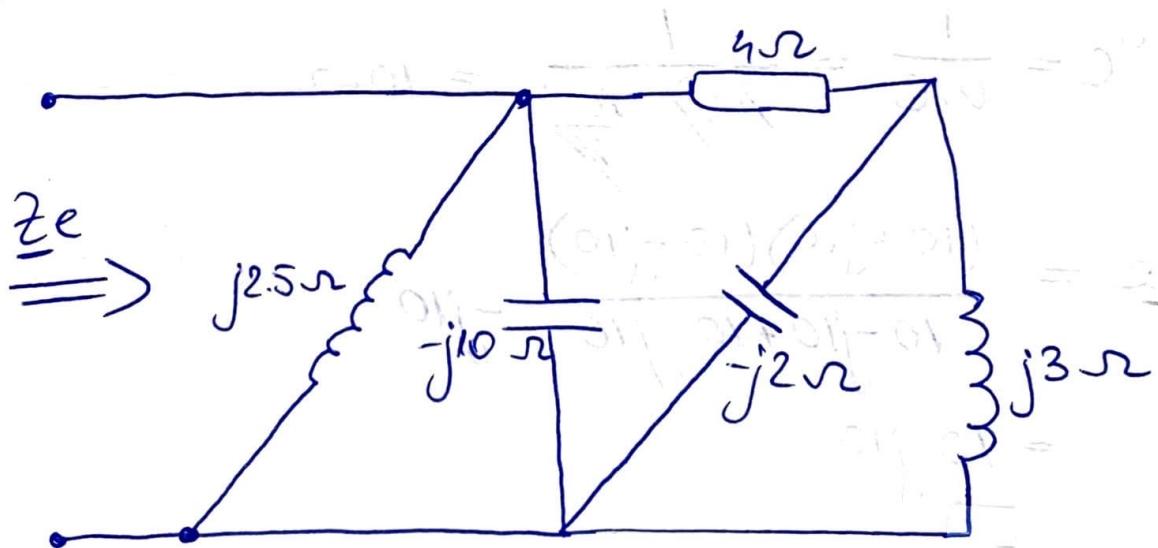

$$\frac{1}{\underline{Z}_e} = \frac{1}{j2.5} - \frac{1}{j20} + \frac{1}{4-j6}$$

$$\underline{Z}_e = 2 + j4.6$$

3.29


$$\underline{Z}_e = ?$$

$$R = 10 \Omega$$

$$L = \frac{100}{\pi} \text{ mH}$$

$$C = \frac{1}{\pi} \text{ mF}$$

$$f = 50 \text{ Hz}$$

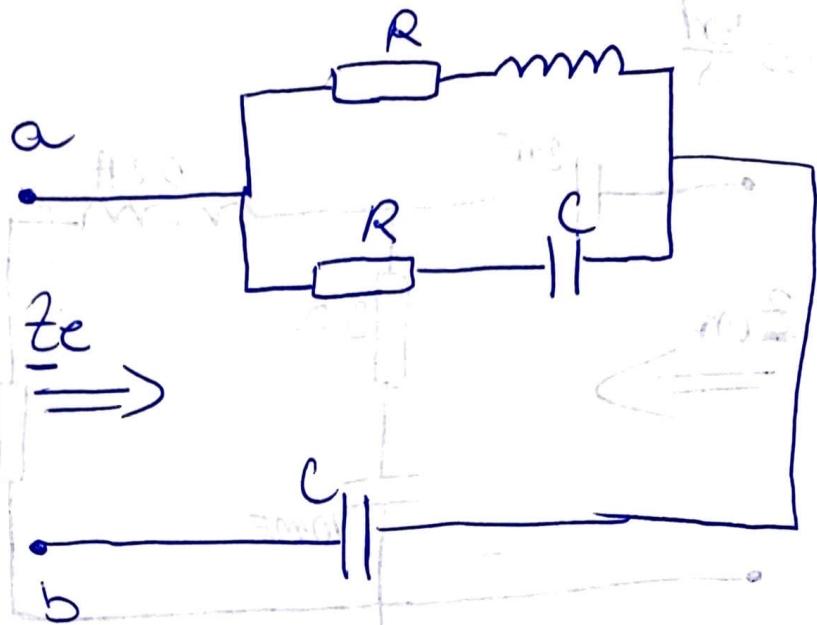

$$\omega = 2\pi f \Rightarrow \omega = 100\pi \frac{\text{rad}}{\text{s}}$$

$$X_L = \omega L = 100\pi \cdot \frac{100}{\pi} \cdot 10^{-3} = 10 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \cdot 10^{-3}} = 10 \Omega$$

$$\begin{aligned} \underline{Z}_e &= \frac{(10+j10)(10-j10)}{10-j10+10-j10} - j10 \\ &= 10-j10 \end{aligned}$$

$$\frac{1}{j(\omega - \omega_0)} + \frac{1}{j(\omega_0 + \omega)} = 0$$

$$3.14159^2 = 98$$


3.30

$$\underline{Z}_e = R_1 = R_2 = R_3 = 10 \Omega$$

$$L_3 = \frac{20}{\pi} \text{ mH}$$

$$C_2 = \frac{5}{\pi} \text{ mF}$$

$$f = 50 \text{ Hz}$$

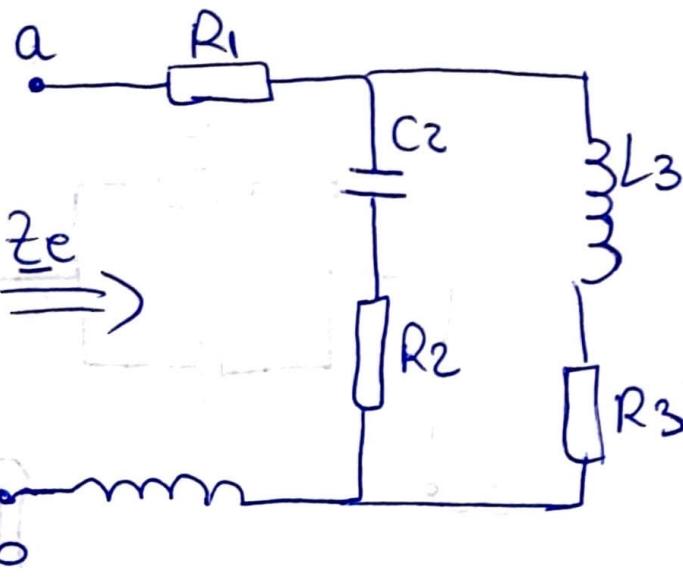

$$\omega = 2\pi f \Rightarrow \omega = 100\pi \frac{\text{rad}}{\text{s}}$$

$$X_L = \omega L_3 = 100\pi \cdot \frac{20}{\pi} \cdot 10^{-3} = 2 \Omega$$

$$X_C = \frac{1}{\omega C_2} = \frac{1}{100\pi \cdot \frac{5}{\pi} \cdot 10^{-3}} = 2 \Omega$$

$$\underline{Z}_e = 10 + \frac{(10+j2)(10-j2)}{10+j2+10-j2} + j2$$

$$\underline{Z}_e = 15.2 + j2$$

B.31


\underline{z}_e

$$R = 10 \Omega$$

$$L = \frac{100}{\pi} \text{ mH}$$

$$C = \frac{1}{\pi} \text{ mF}$$

$$f = 50 \text{ Hz}$$

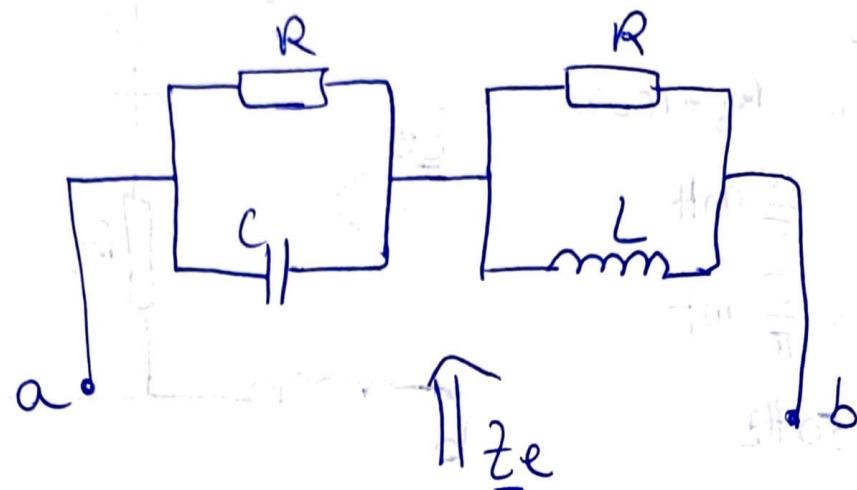

$$\omega = 2\pi f = 100\pi \frac{\text{rad}}{\text{s}} = 314 \frac{\text{rad}}{\text{s}} = 314 \text{ rad/s}$$

$$X_L = \omega L = 100\pi \cdot \frac{100}{\pi} \cdot 10^{-3} = 10 \Omega = \frac{1}{314 \text{ rad/s}} = 314 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \cdot \frac{1}{\pi} \cdot 10^{-3}} = 10 \Omega$$


$$\underline{z}_e = \frac{10 \cdot (-j20)}{10 - j10} + \frac{10 \cdot j10}{10 + j20}$$

$$Z = 10 \Omega$$

B.32

$$\begin{aligned}
 & \underline{Z_e} \\
 & R_1 = 5 \Omega \\
 & R_2 = R_3 = 10 \Omega \\
 & L_1 = \frac{150}{\pi} \text{ mH} \\
 & L_3 = \frac{100}{\pi} \text{ mH} \\
 & C_2 = \frac{10^3}{\pi} \mu F
 \end{aligned}$$

$$f = 50 \text{ Hz}$$

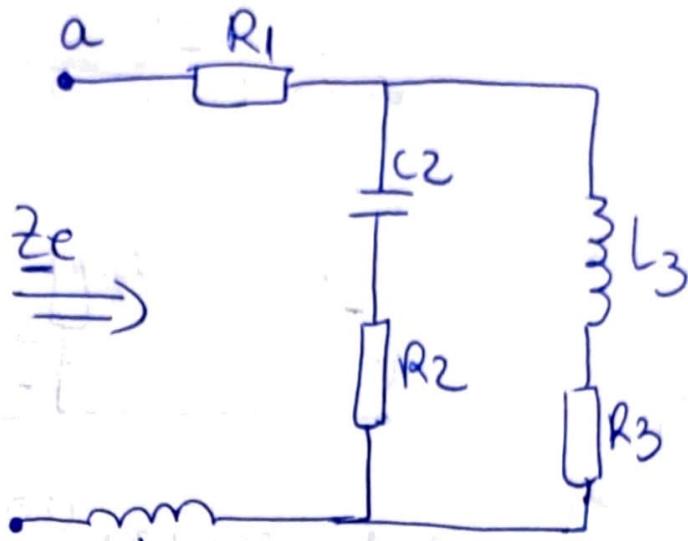

$$\omega = 2\pi f = 100\pi \frac{rad}{s}$$

$$X_{L1} = \omega L_1 = 100\pi \cdot \frac{150}{\pi} \cdot 10^{-3} = 15 \Omega$$

$$X_{L3} = \omega L_3 = 100\pi \cdot \frac{100}{\pi} \cdot 10^{-3} = 10 \Omega$$

$$X_{C2} = \frac{1}{\omega C_2} = \frac{1}{100\pi \cdot \frac{10^3}{\pi} \cdot 10^{-6}} = 10 \Omega$$

$$W_{33V} = (1 + j15) \cdot (1 + j15)$$

$$\underline{Z}_e = 5 + \frac{(10 + j10)(10 - j10)}{10 + j10 + 10 - j10} + j15 = 15 + j15$$



3.33

$$\underline{Z}_1 = 10 + j40$$

$$\underline{Z}_2 = 20 - j20$$

$$\underline{Z}_3 = 20 + j20$$

$$I = 4 \text{ A}$$

a) $\underline{Z}_e = ?$


b) $U_e = ?$

$$u_e(t) = ?$$

c) $P = ?$

$$Q = ?$$

$$S = ?$$

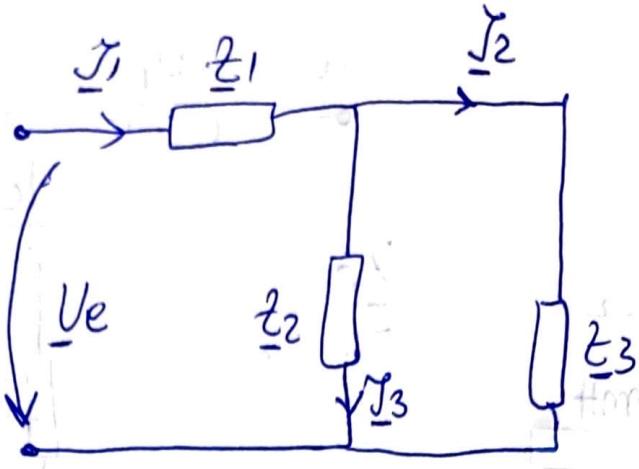

a) $\underline{Z}_e = 20 + j40 + \frac{(20 + j20)(20 - j20)}{20 + j20 + 20 - j20}$

$$= 30 + j40$$

b) $U_e = 4 e^{j\varphi_i} \cdot 50 e^{j53^\circ}$
 $= 200 e^{j(\varphi_i + 53^\circ)}$


$$U_e = 200 \text{ V}$$

$$u_e(t) = 200\sqrt{2} \sin(\omega t + \varphi_i + 53^\circ) \text{ V}$$

c) $P = U \cdot I \cos(\varphi_u - \varphi_I) = 482 \text{ W}$

$$Q = 639 \text{ VAR}$$

$$S = 800 \text{ VA}$$

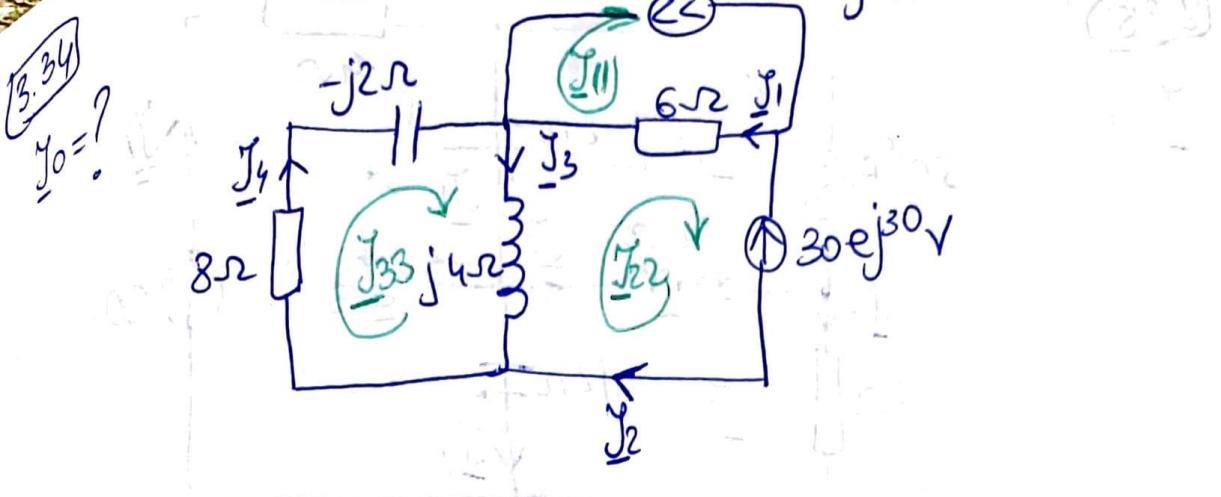

$$\left\{ \begin{array}{l} \underline{J}_{11} = -6 e^{j0^\circ} \\ \underline{J}_{22} (6 + j4) - \underline{J}_{11} 6 - \underline{J}_{33} j4 = -30 e^{j30^\circ} \\ \underline{J}_{33} (8 + j2) - \underline{J}_{22} j4 = 0 \end{array} \right.$$

$$y_{22} = -7.2 + j1.3 = \underline{J}_2 \text{ A}$$

$$\underline{J}_{33} = -1.4 - j3.2 = \underline{J}_4$$

$$\underline{J}_1 = \underline{J}_{11} - \underline{J}_{22} = 1.2 + j1.3 \text{ A}$$

$$y_3 = \underline{J}_{33} - \underline{J}_{22} = 5.4 - j4.5 \text{ A}$$

$$\underline{J}_2 = 31.23 = 33 \underline{J}$$

$$\underline{J}_4 = 8.14 \underline{J}$$


$$A \underline{J}_1 = 35 - \underline{J}_2 = \underline{J}_1$$

$$A \underline{J}_2 = 33 - 33 \underline{J} - \underline{J}_2 = 33 \underline{J}$$

$$A \underline{J}_3 = 33 - 53 \underline{J} - 53 \underline{J} = 33 \underline{J}$$

3.35

$$\underline{Y}_0 = ?$$

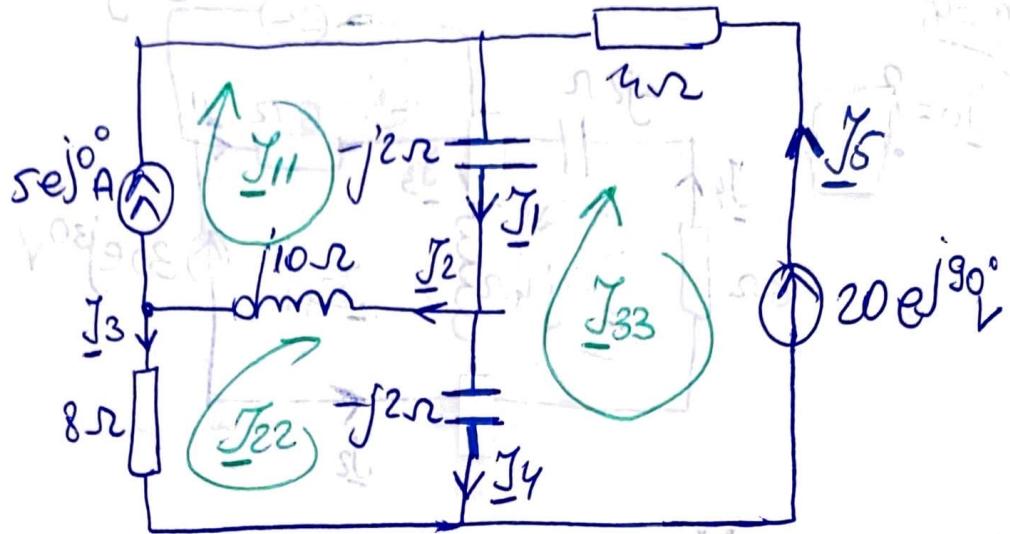

$$\left\{ \begin{array}{l} \underline{Y}_{11} = 5A \end{array} \right.$$

$$\underline{Y}_{22} (8-j2) - \underline{Y}_{11} j10 - \underline{Y}_{33} (-j2) = 0$$

$$\underline{Y}_{33} (4-j4) - j2 (\underline{Y}_{11} + \underline{Y}_{22}) = -j20$$

$$\underline{Y}_{22} = 29-18 = -\underline{Y}_3$$

$$\underline{Y}_{33} = -4+18 = \underline{Y}_2$$


$$\underline{Y}_1 = \underline{Y}_{11} - \underline{Y}_{33} = 5-j8 A$$

$$\underline{Y}_2 = \underline{Y}_{11} - \underline{Y}_{22} = -24+j8 A$$

$$\underline{Y}_3 = \underline{Y}_{22} - \underline{Y}_{33} = 33-j16 A$$

B.36
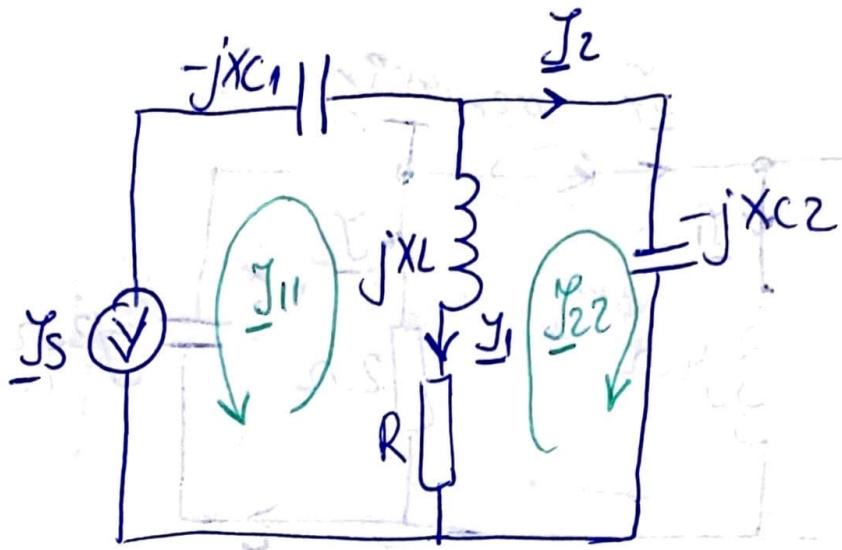
$$\begin{aligned}
 R &= 9.3 \Omega \\
 L &= 100 \mu H \\
 C_1 &= 1.2 nF \\
 C_2 &= 820 pF \\
 f &= 570 kHz \\
 \underline{y}_S &= 3e^{-j30^\circ} \\
 J_1 &=? \quad J_2 = ?
 \end{aligned}$$



$$\omega = 2\pi f = 2\pi \cdot 570 \cdot 10^3 = 114\pi \cdot 10^4 \text{ rad/s}$$

$$X_L = \omega L = 114\pi \cdot 10^4 \cdot 100 \cdot 10^{-6} = 114\pi \approx 359 \Omega$$

$$X_{C1} = \frac{1}{\omega C_1} = \frac{1}{114\pi \cdot 10^4 \cdot 1.2 \cdot 10^{-9}} = 233 \Omega$$


$$X_{C2} = \frac{1}{\omega C_2} = \frac{1}{114\pi \cdot 10^4 \cdot 820 \cdot 10^{-12}} = 341 \Omega$$

$$\begin{cases}
 Y_{11} = 3e^{-j30^\circ} \\
 Y_{22} (9.3 + j125.5) + J_{11}(9.3 + j358) = 0
 \end{cases}$$

$$Y_{22} = -9.3 + j3.9 = Y_2$$

$$Y_1 = -J_{11} - J_{22} = 5 - j2.4$$

3.3

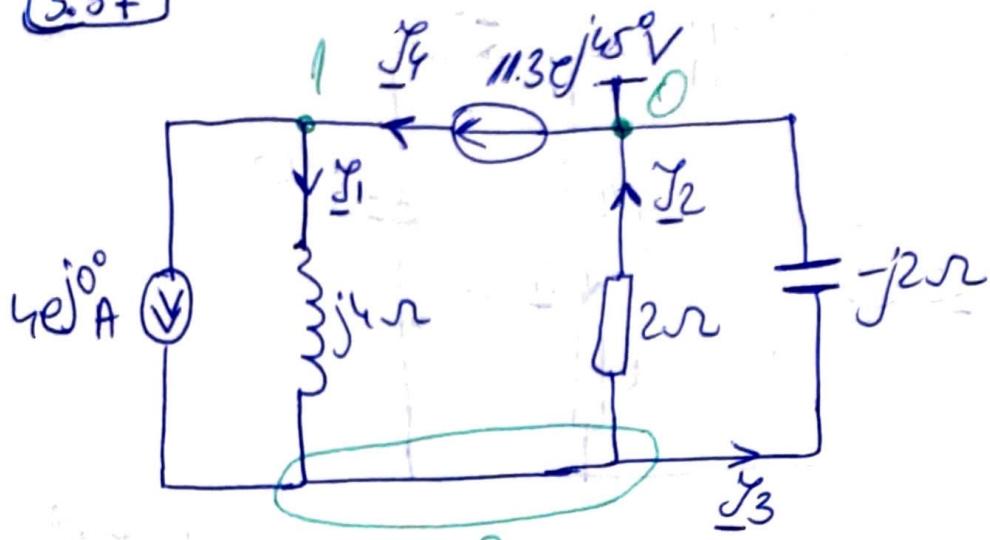

$$V_0 = 0V$$

$$\left\{ \begin{array}{l} V_1 = 8 + j4 \\ V_2 = ? \end{array} \right.$$

$$V_2 - \left(\frac{1}{2} + \frac{1}{j4} - \frac{1}{j2} \right) - V_1 \cdot \frac{1}{j4} = 4$$


$$V_2 = 8 - j8$$

$$I_1 = \frac{V_1 - V_2}{j4} = \frac{j26}{j4} = 4A \Rightarrow I_4 = 8A$$

$$I_2 = \frac{V_2}{2} = 4 - j4 A$$

$$I_3 = \frac{V_2}{j2} = 4 + j4 A$$

3.38

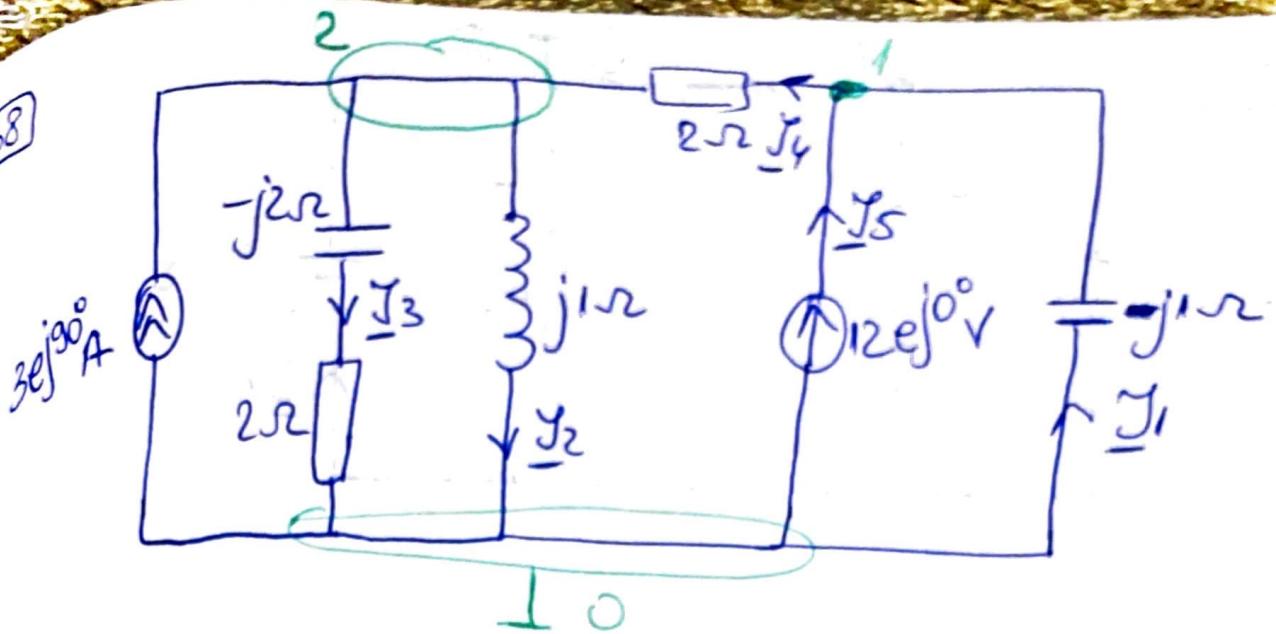

$$V_0 = 0$$

$$\begin{cases} V_1 = 12V \\ V_2 \left(\frac{1}{-j2+2} + \frac{1}{j} + \frac{1}{2} \right) - V_1 \cdot \frac{1}{2} = j3 \end{cases}$$

$$V_2 = 0.3 + j4.5$$


$$\underline{Y}_1 = \frac{-V_1}{j} = \frac{12}{j} = -j12 \text{ A}$$

$$\underline{Y}_2 = \frac{V_2}{j} = 4.5 - 0.3 \text{ A}$$

$$\underline{Y}_3 = \frac{V_2}{2-j2} = -1 + j1.2 \text{ A}$$

$$\underline{Y}_4 = \frac{V_1 - V_2}{2} = 5.8 - j2.2 \Rightarrow \underline{Y}_5 = 5.8 - j14.2$$

3.39

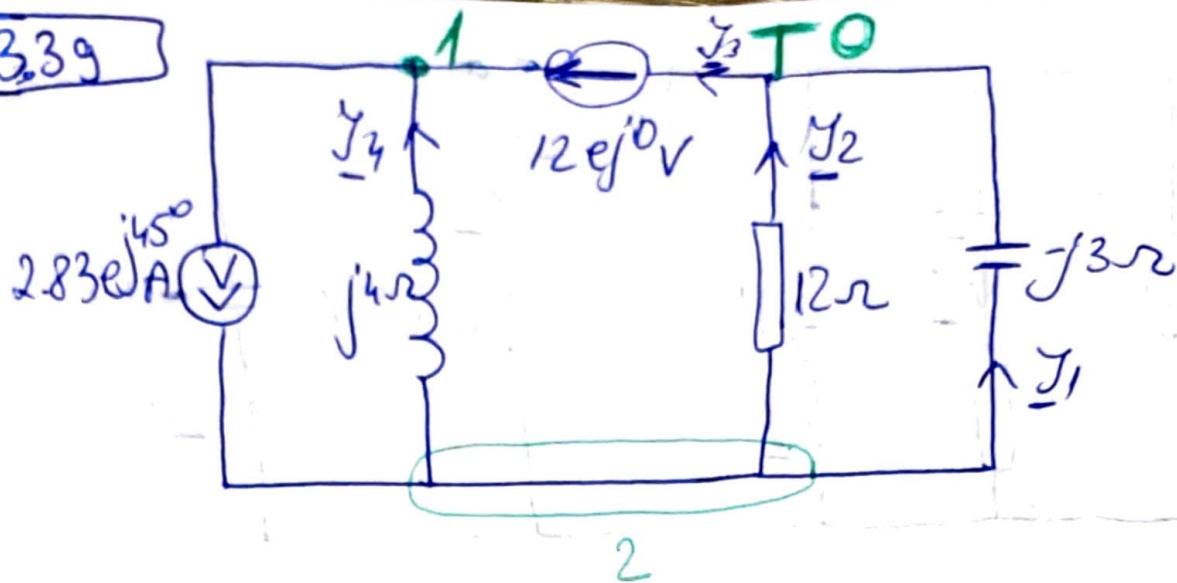

$$V_0 = 0$$

$$\left\{ \begin{array}{l} V_1 = 12V \\ V_2 = \end{array} \right.$$

$$V_2 \left(\frac{1}{j4} + \frac{1}{12} - \frac{1}{j3} \right) - V_1 \cdot \frac{1}{j4} = 2 + j2$$

$$V_2 = 6 - j18$$


$$I_1 = \frac{V_2}{j3} = 6 + j2 \text{ A}$$

$$I_2 = \frac{V_2}{12} = 0.5 - j1.5 \text{ A}$$

$$I_3 = 6.5 + j0.5 \text{ A}$$

$$I_4 = \frac{V_2 - V_1}{j4} = \frac{-6 - j18}{j4} = -8.5 + j25 \text{ A}$$

3.40

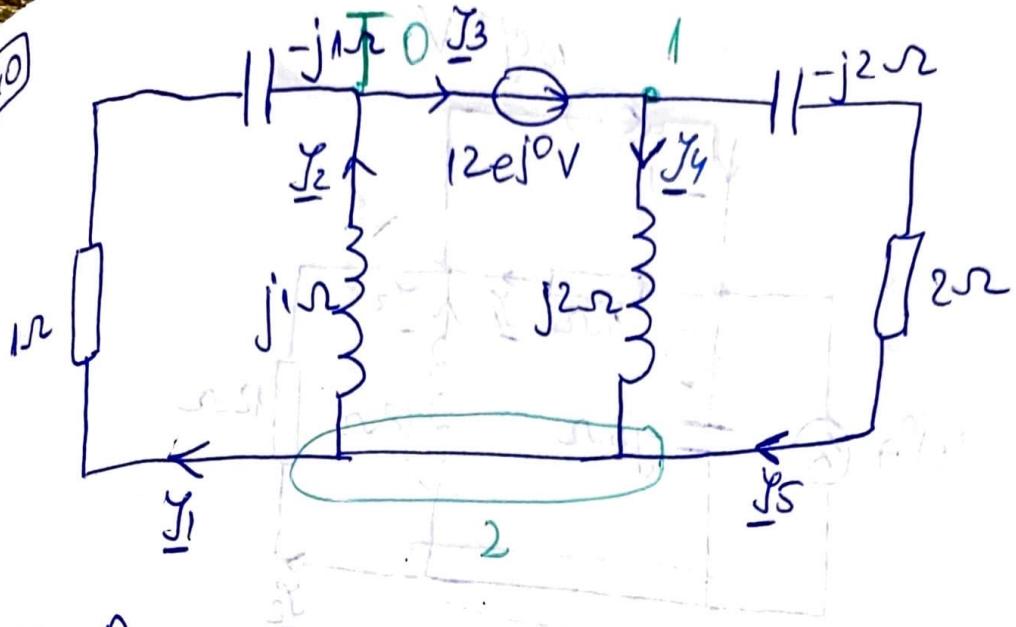

$$V_0 = 0$$

$$\begin{cases} V_1 = 12 \text{ V} \\ V_2 = 3 - j3 \\ V_3 = 1.5 - j4.5 \\ V_4 = -1.5 + j1.5 \end{cases}$$


$$V_2 = 3 - j3$$

$$I_1 = \frac{V_2}{2-j} = 3 \text{ A}$$

$$I_2 = -\frac{V_2}{j} = -3 - j3 \text{ A} \Rightarrow J_3 = -3\sqrt{3}$$

$$I_4 = \frac{V_1 - V_2}{j^2} = 1.5 - j4.5 \Rightarrow J_5 = -1.5 + j1.5$$

3.41

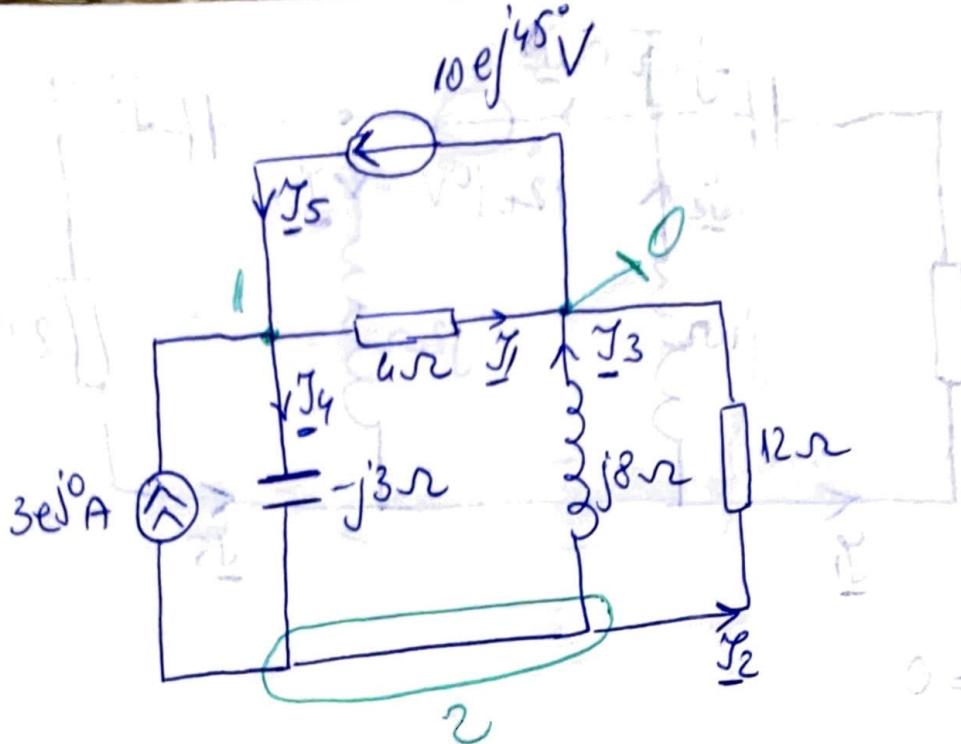

$$V_0 = 0 V$$

$$0 = \frac{1}{S_L} V - \left(\frac{1}{S_A} + \frac{1}{S_B} + \frac{1}{S_C} + \frac{1}{Z_L} \right) S_L V$$

$$\left\{ \begin{array}{l} V_1 = 5\sqrt{2} + j5\sqrt{2} \\ V_2 = \end{array} \right.$$

$$\left\{ \begin{array}{l} V_2 \left(\frac{1}{12} + \frac{1}{j8} + \frac{1}{j3} \right) + V_1 \cdot \frac{1}{j3} = 3 \end{array} \right.$$

$$S_L - \epsilon = 5V$$

$$A\epsilon = \frac{5V}{j-3} = 1.7$$

$$I_1 = \frac{1}{j5} = 1.25\sqrt{2} + j1.25\sqrt{2} = 1.7 + j1.7$$


$$I_2 = \frac{V_2}{12} = 0.074 + j2$$

$$I_3 = \frac{V_2}{j8} = 3.25 - j0.11$$

$$I_4 = \frac{V_1 - V_2}{-j3} = 6.3 + j2$$

$$I_5 = I_1 + I_2 + I_3 = 22.4 + j5.9$$

B.42

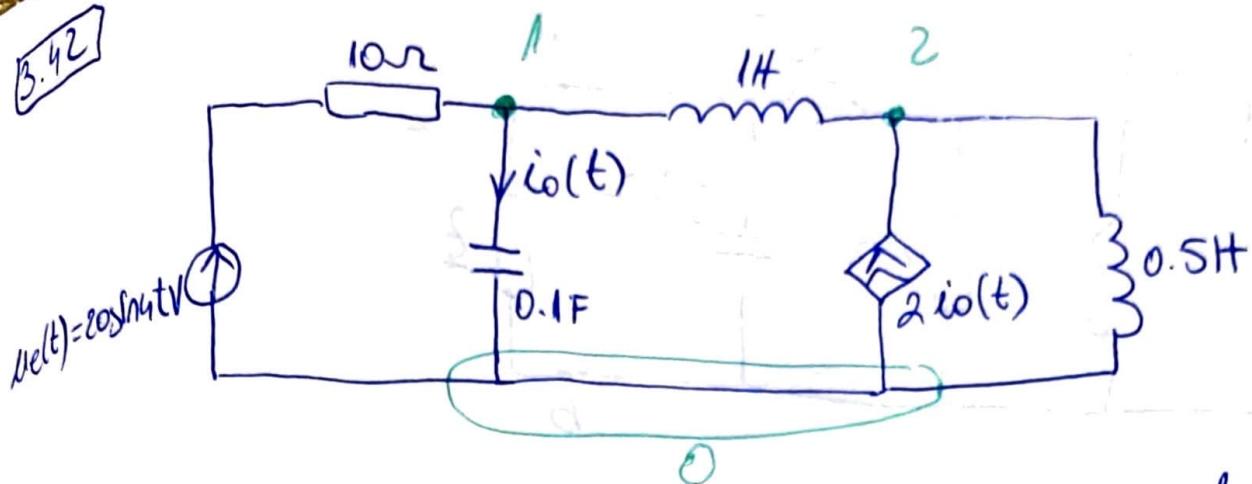

$$U_e = \frac{20}{\sqrt{2}} = \frac{20\sqrt{2}}{2} = 10\sqrt{2}$$

$$\omega = 4 \frac{\text{rad}}{\text{s}}$$

$$X_{L1} = \omega L_1 = 4\Omega$$

$$X_{L2} = \omega L_2 = 2\Omega$$

$$X_C = \frac{1}{\omega C} = 2.5\Omega$$

$$\begin{cases} V_1 \left(\frac{1}{10} - \frac{1}{j2.5} + \frac{1}{j4} \right) - V_2 \cdot \frac{1}{j4} = \sqrt{2} \\ V_2 \left(\frac{1}{j4} + \frac{1}{j2} \right) - V_1 \cdot \frac{1}{j4} = \frac{jV_1}{5} \end{cases}$$

$$V_1 = -2.8 - j4$$

$$Y_0 = -1.1 - j1.6 = 2e^{-j125^\circ}$$



$$J_0(t) = 2\sqrt{2} \sin(ut - 125^\circ) \text{ A}$$

NP.S

$$U + \underline{E} = \underline{ZI} = \frac{1}{10} + \frac{1}{j4} + \frac{1}{j4} \cdot \frac{(j4-j2)}{j4+j2} = -j2$$

$$-j2 = 2 \angle$$


3.43

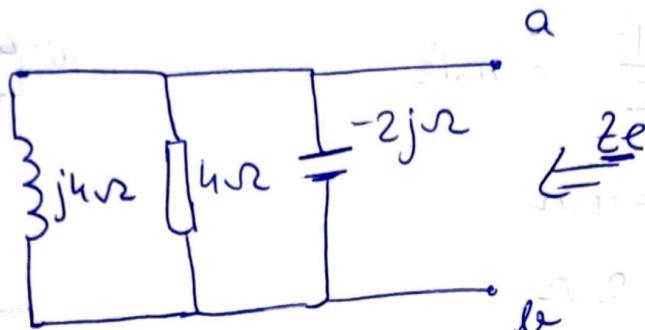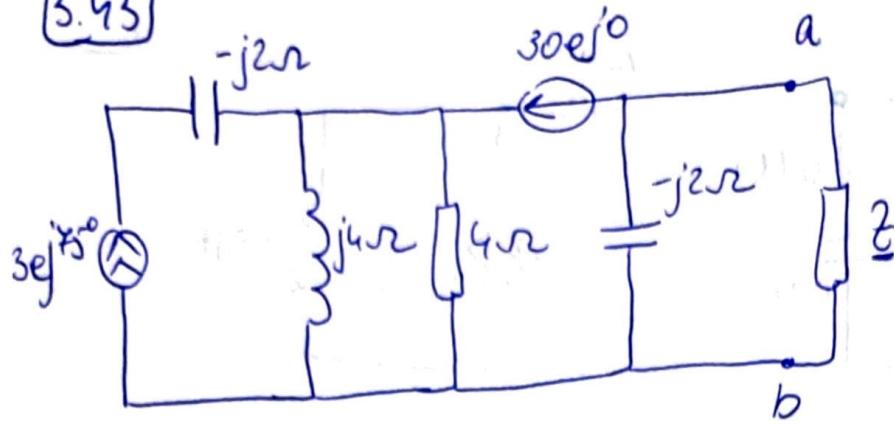

$$\frac{1}{Z_e} = \frac{1}{j4} + \frac{1}{4} + \frac{1}{-j2} \Rightarrow Z_e = 2 - j^2 \omega$$


$$Z_e = Z_e^* = 2 + j^2 \omega$$

3.44

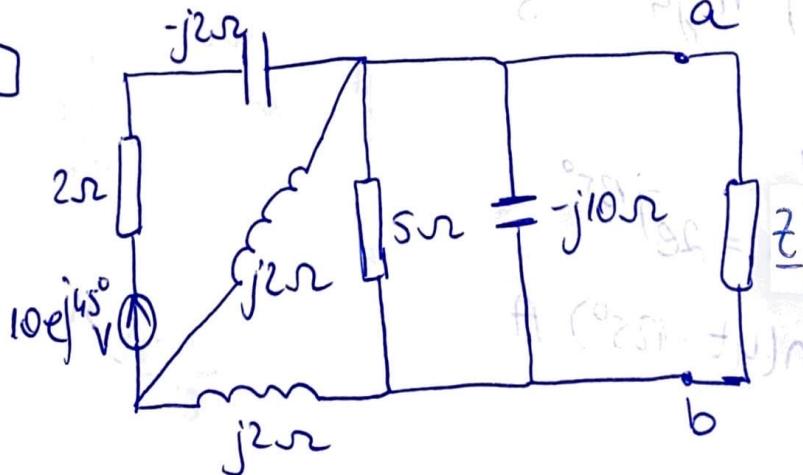


$$\frac{1}{Z_e} = \frac{1}{j2(2-j2)} + \frac{1}{j2+2-j2} + \frac{1}{5} + \frac{1}{-j10} \Rightarrow Z_e = 3 + j$$

$$\Rightarrow Z_e = 3 - j \omega$$

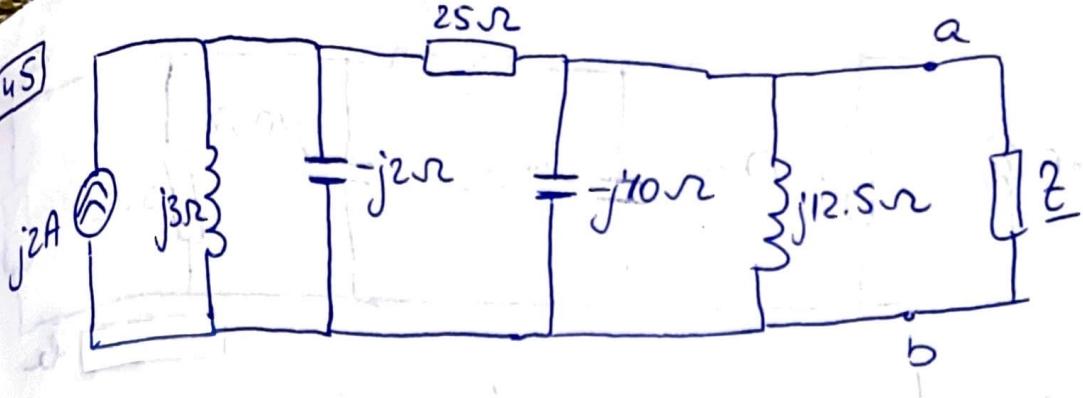


$$\frac{1}{Z_e} = \frac{1}{25 + \frac{6}{i}} + \frac{1}{-10i} + \frac{1}{125i} \Rightarrow Z_e = 2 - j5.5$$

$$\Rightarrow Z = 2 + j5.5\Omega$$

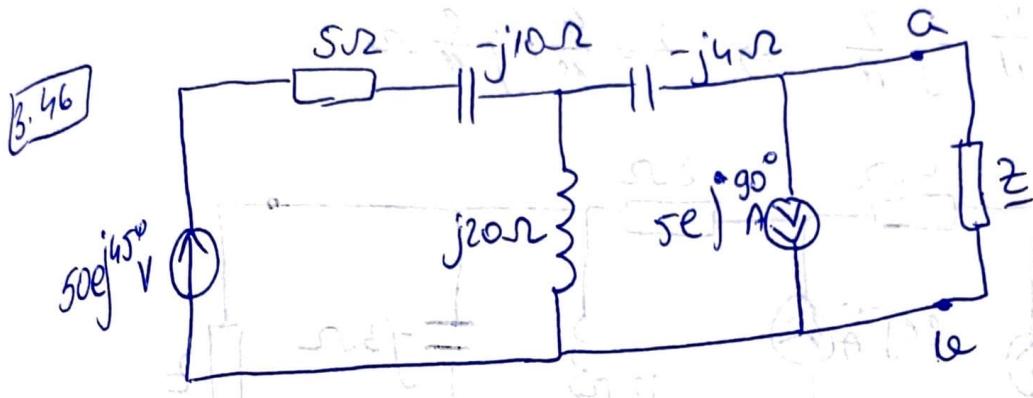

$$Z_e = \frac{j20(5 - j10)}{j20 + 5 - j10} + (-j4) = 16 - j16$$


$$\Rightarrow Z = 16 + j16\Omega$$

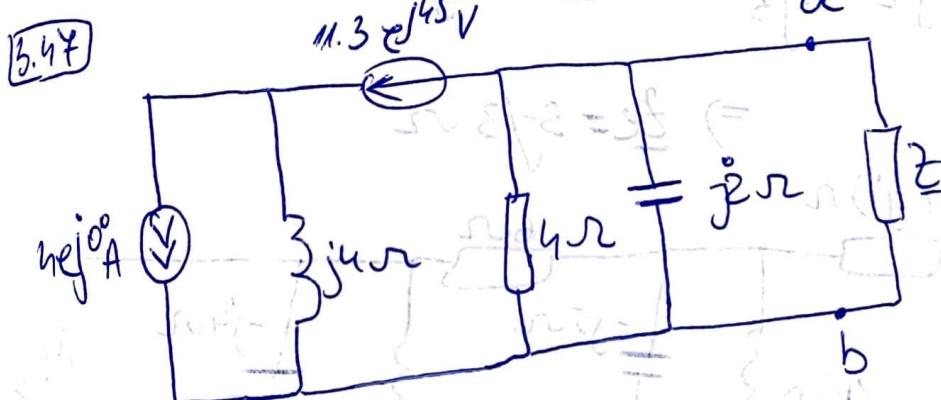

$$\frac{1}{Z_e} = \frac{1}{j4} + \frac{1}{4} + \frac{1}{j1} \Rightarrow Z_e = 2 - 2j$$

$$\Rightarrow Z = 2 + 2j\Omega$$


3.48

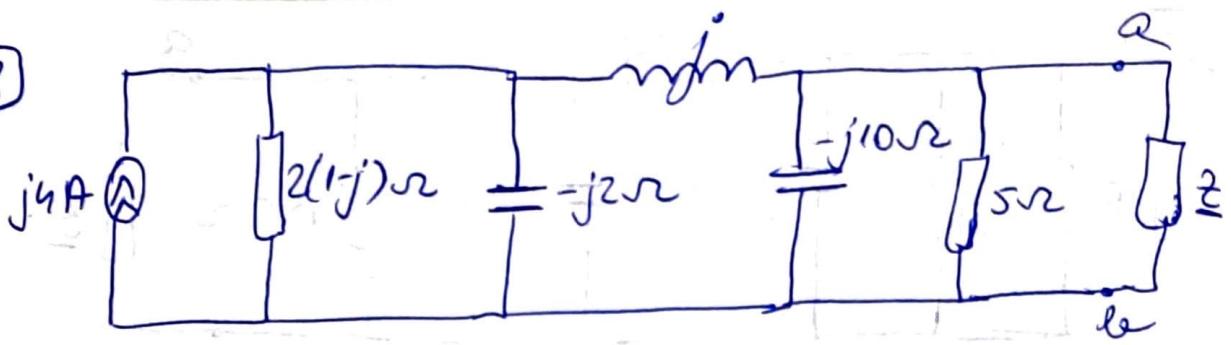

$$\frac{1}{\underline{Z}_e} = \frac{1}{2(j-j)(-j^2)} + \frac{1}{-j^2} + \frac{1}{-j^{10}} + \frac{1}{5}$$

$$\underline{Z}_e = \frac{4}{11} - j \frac{2}{11} \Rightarrow \underline{Z} = \frac{4}{11} + j \frac{2}{11} \Omega$$


3.49

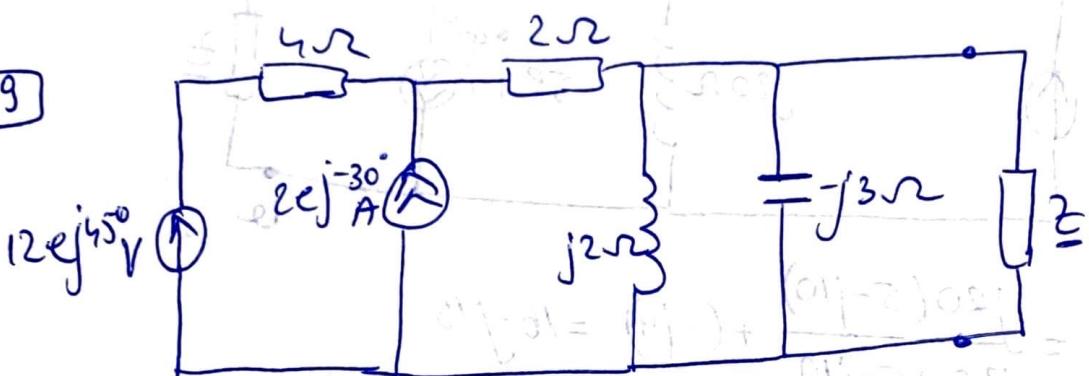

$$\frac{1}{\underline{Z}_e} = \frac{1}{4+2} + \frac{1}{j^2} + \frac{1}{-j^3} \Rightarrow \underline{Z}_e = 3 + j3$$


$$\Rightarrow \underline{Z} = 3\sqrt{3} \Omega$$

3.50

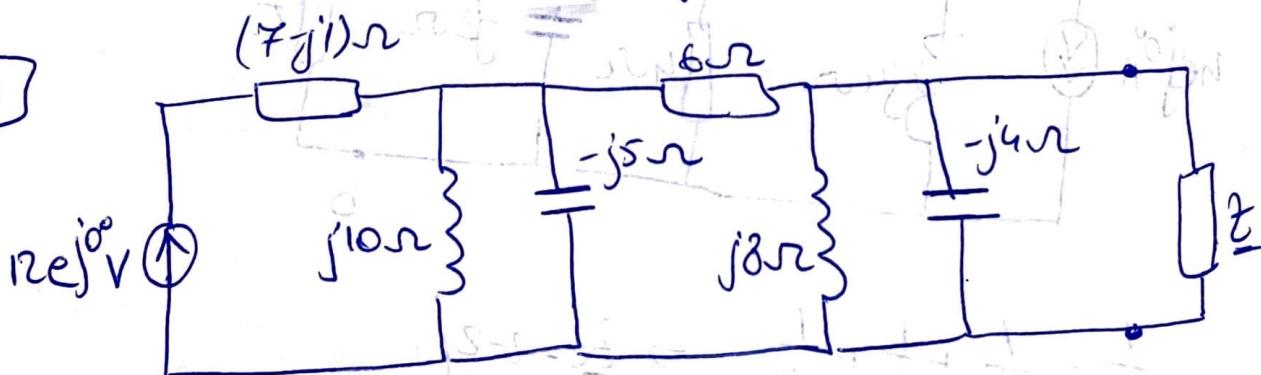

$$\begin{aligned} \frac{1}{\underline{Z}_e} &= \frac{1}{\frac{1}{7j1} + \frac{1}{j10} + \frac{1}{-j5} + \frac{1}{j8} + \frac{1}{-j4}} + 6 \Rightarrow \underline{Z}_e = 2.7 - j4.8 \\ &\Rightarrow \underline{Z} = 2.7 + j4.8 \Omega \end{aligned}$$

Transient problems

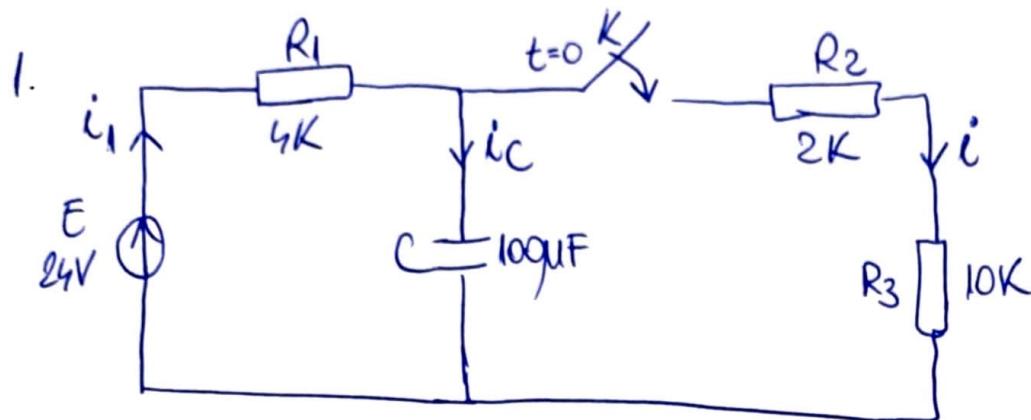


$$u_C(0-) = ?$$


$$u_C(t) = ?$$

$$i_C(t) = ?$$

$t \leq 0$

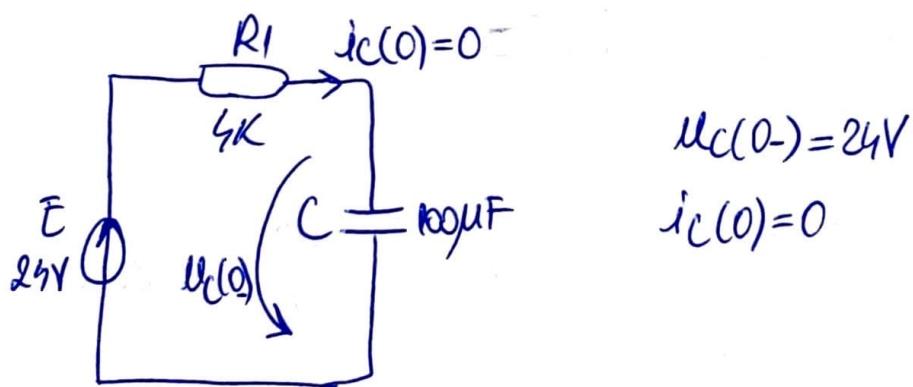

$t \rightarrow \infty$

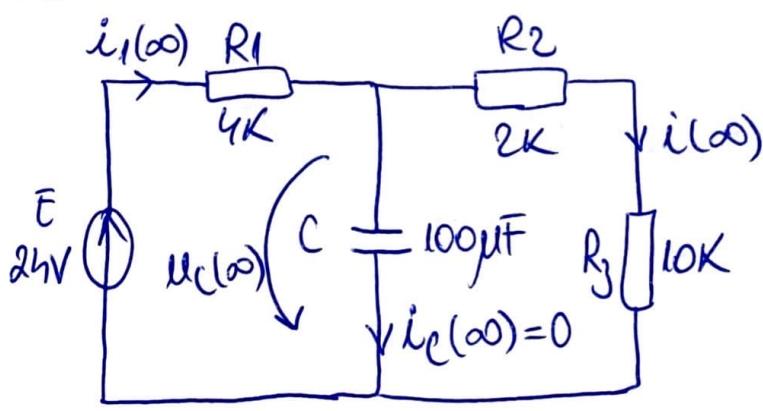


$$i_C(\infty) = 0$$

$$i_1(\infty) = i(\infty) = \frac{E}{R_1 + R_2 + R_3}$$


$$= \frac{24}{16} = 1.5 \text{ mA}$$

$$u_C(\infty) = i(\infty)(R_2 + R_3)$$

$$= 1.5(2 + 10) = 18V$$

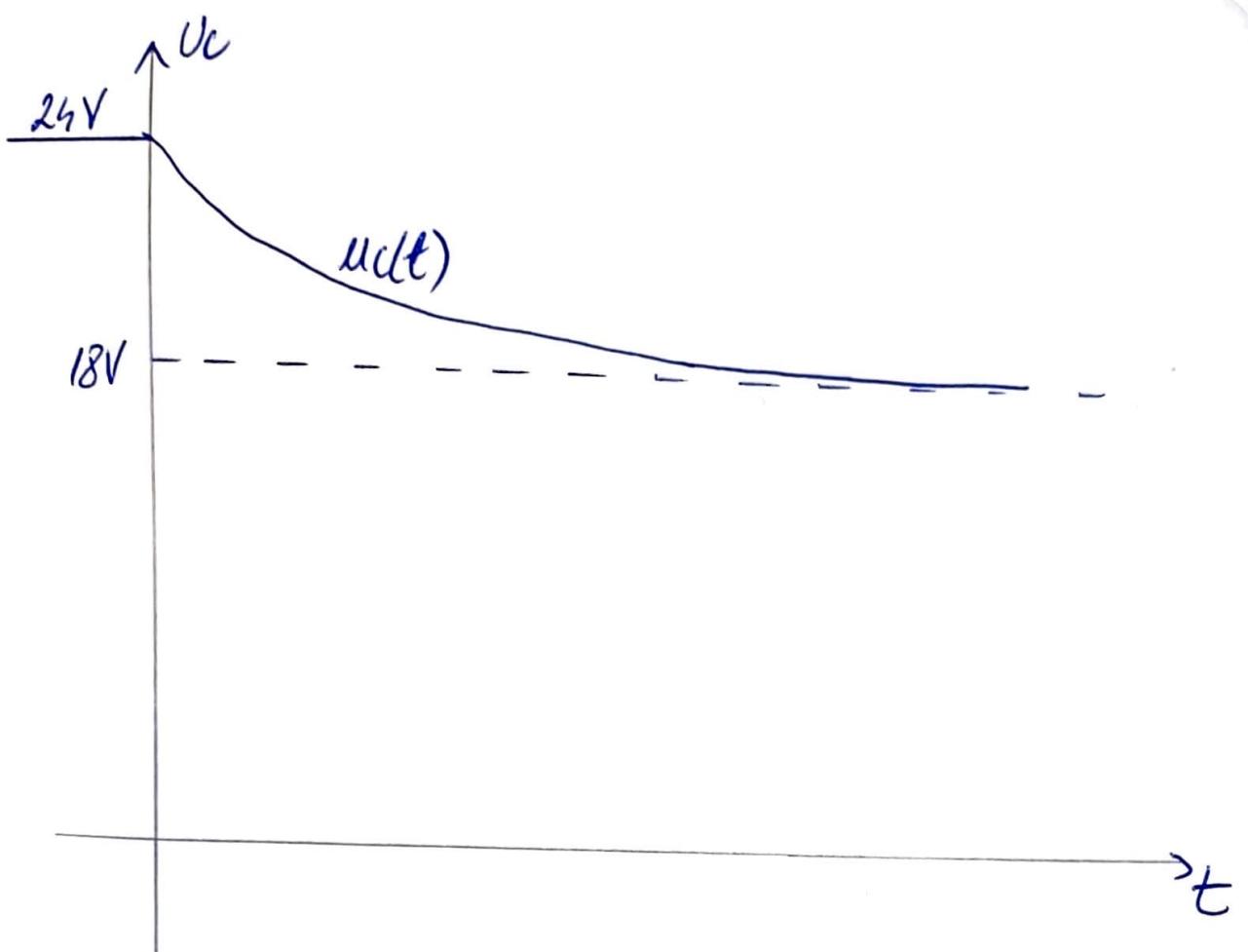
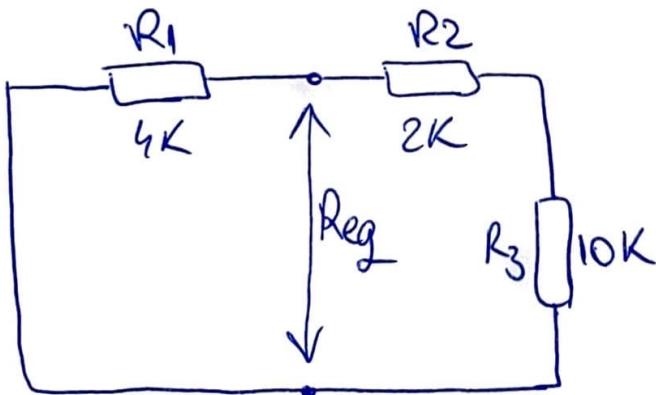
$$U_C(t) = U_C(\infty) - (U_C(\infty) - U_C(0)) e^{-\frac{t}{\tau}}$$




$$R_{\text{eq}} = \frac{4 \cdot 12}{4+12} = 3 \text{ k}\Omega$$

$$\tau = R_{\text{eq}} C = 3 \cdot 10^3 \cdot 0.1 \cdot 10^{-3} = 0.3 \text{ s}$$


$$U_C(t) = 18 - (18 - 24) e^{-\frac{t}{0.3}}$$

$$U_C(t) = 18 + 6 e^{-\frac{t}{0.3}}$$
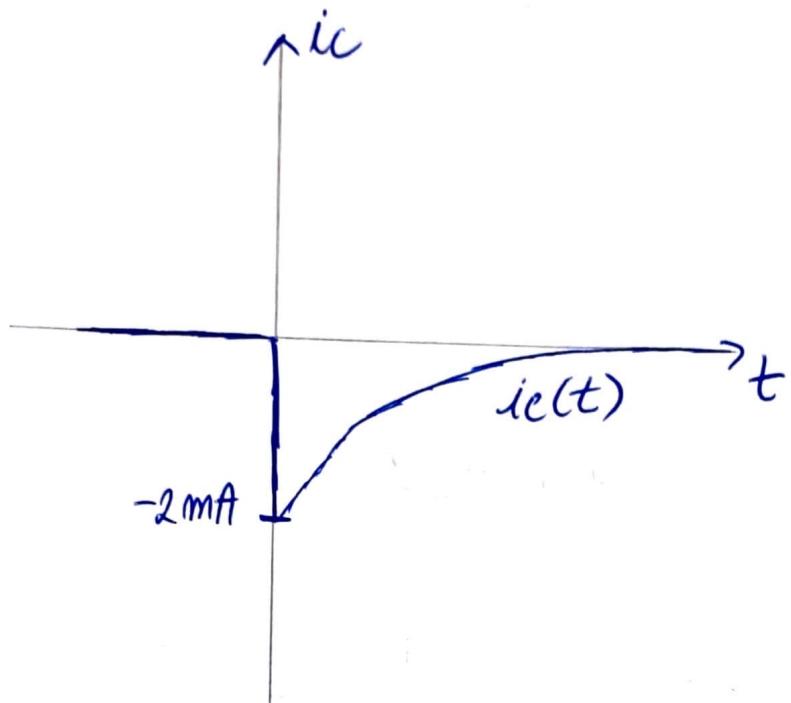
$$i_C(t) = C \frac{dU_C}{dt} = 0.1 \cdot 10^{-3} \cdot 6 \left(-\frac{1}{0.3} \right) e^{-\frac{t}{0.3}} \\ = -2 e^{-\frac{t}{0.3}} \text{ mA}$$




2.

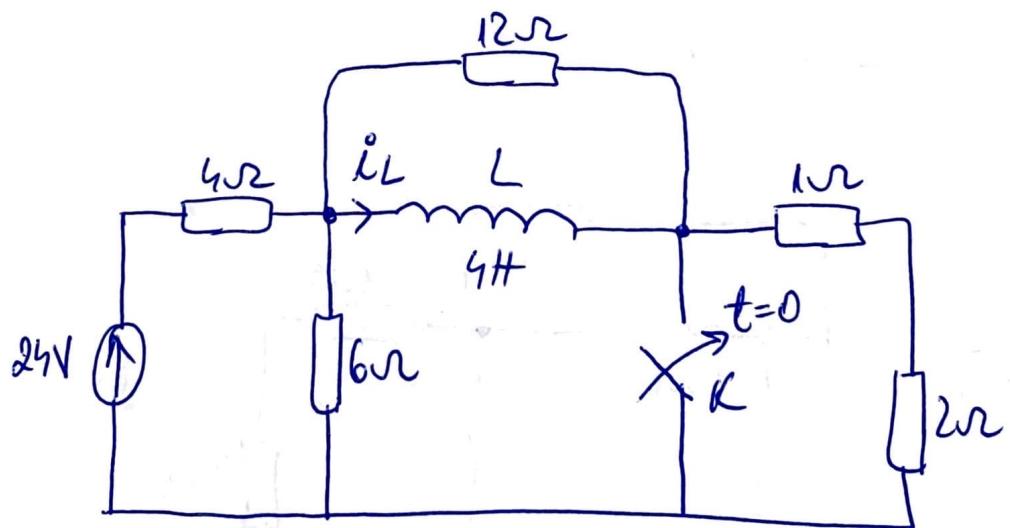


$$i_L(t) = i_L(\infty) - (i_L(\infty) - i_L(0)) e^{-\frac{t}{\tau}} \quad , \quad \tau = \frac{L}{R_{\text{eq}}}$$

$t < 0$

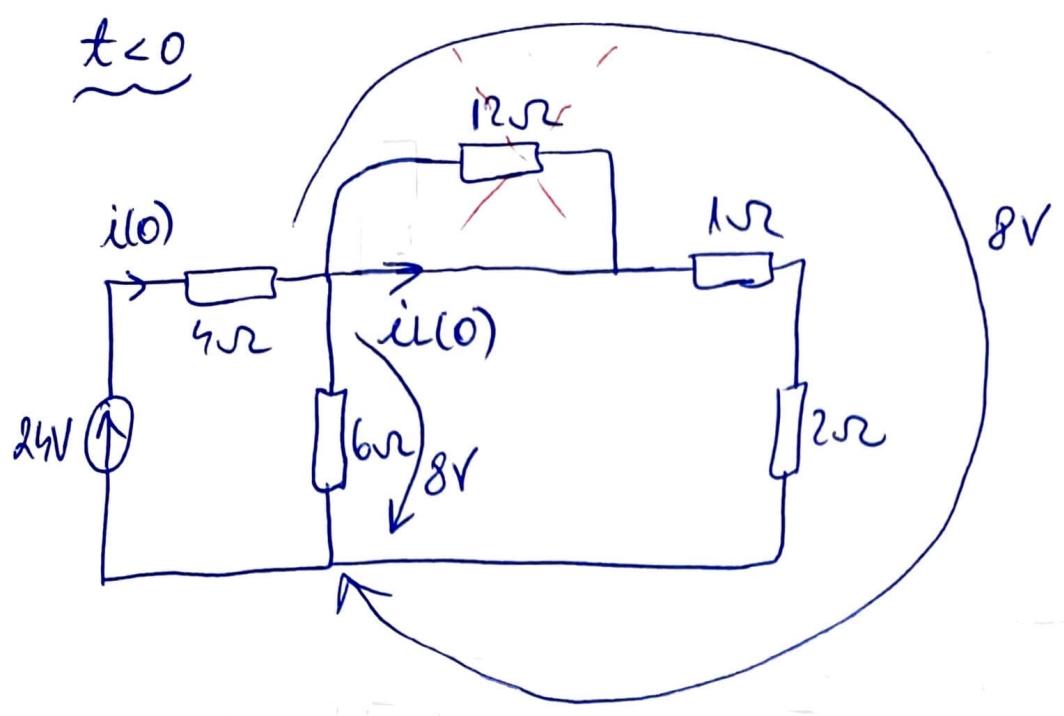


16V

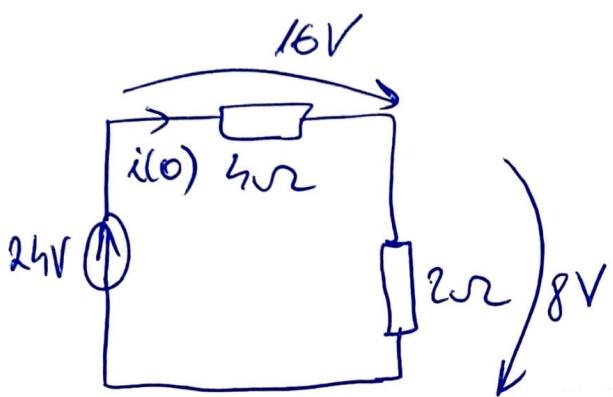


$$I(0) = \frac{24}{6} = 4 \text{ A}$$

$$i_L(0) = \frac{8}{3} \text{ A}$$

$t \rightarrow \infty$

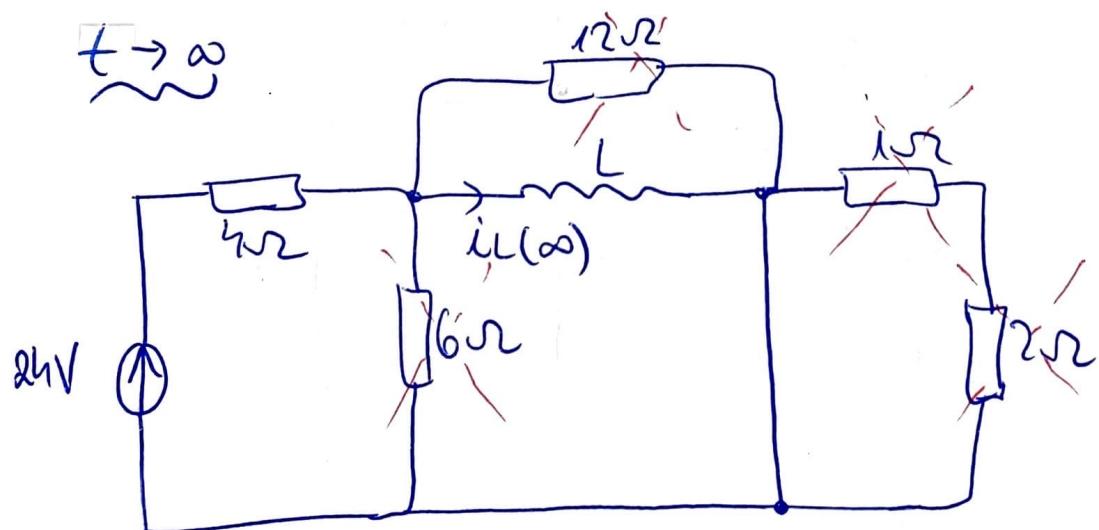
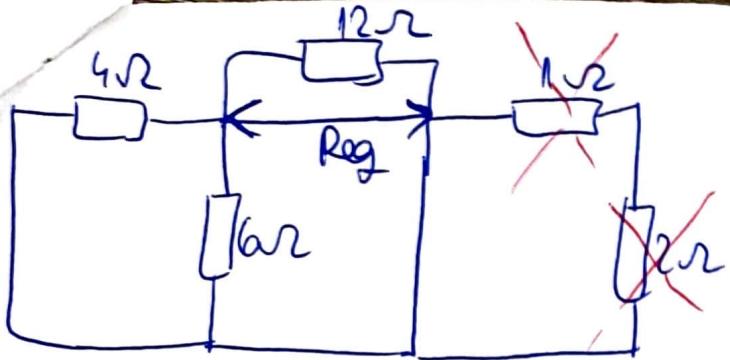
$$i_L(\infty) = \frac{12}{4} = 6 \text{ A}$$



$$\frac{1}{R_{\text{eq}}} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} = \frac{1}{2}$$


$$R_{\text{eq}} = 2 \Omega$$


$$T = \frac{L}{R_{\text{eq}}} = 2 \text{ s}$$

$$\begin{aligned} i_L(t) &= 6 - \left(6 - \frac{8}{3}\right) e^{-\frac{t}{2}} \\ &= 6 - \frac{10}{3} e^{-\frac{t}{2}} \text{ A} \end{aligned}$$


$$i_L(0) = \frac{8}{3} \text{ A}$$

$$i_L(\infty) = 6 \text{ A}$$

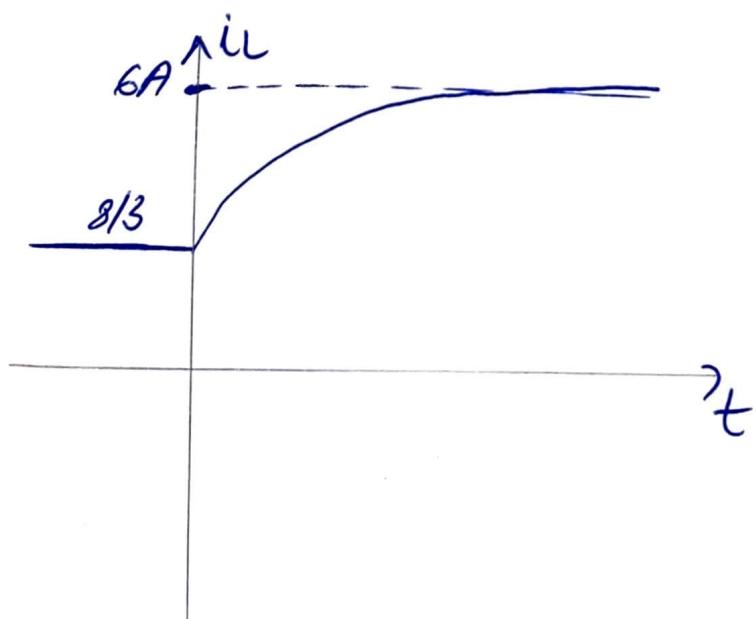


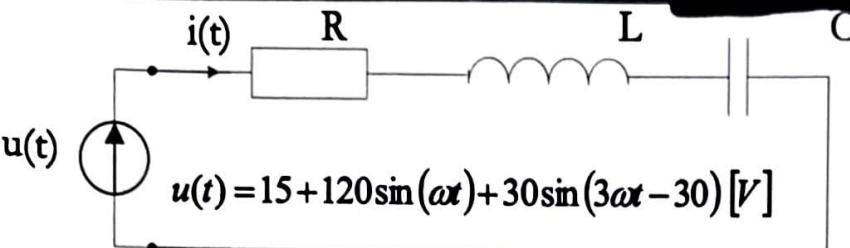
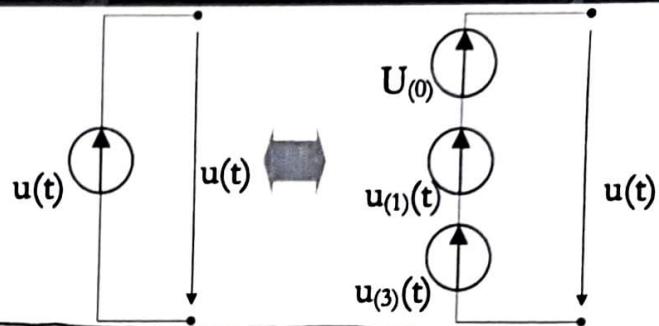
$$\begin{aligned}R &= 6\Omega \\ \omega L &= 1\Omega \\ 1/\omega C &= 9\Omega\end{aligned}$$



For the DC component:

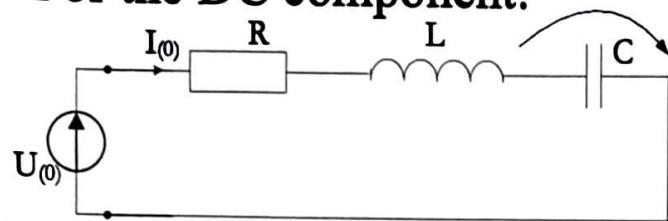

$$U_{(0)} = 15V, \quad I_{(0)} = 0A, \quad U_{C(0)} = U_{(0)} = 15V$$

$$u_1(t) = 120\sin(\omega t) \rightarrow \underline{U}_{(1)} = \frac{120}{\sqrt{2}}$$

$$I_{(1)} = \frac{\underline{U}_{(1)}}{\underline{Z}_{(1)}} = \frac{120}{\sqrt{2} \left[R + j \left(\omega L - \frac{1}{\omega C} \right) \right]} = \frac{120}{\sqrt{2} [6 + j(1 - 9)]} = 8.485e^{j53}$$

$$\underline{U}_{C(1)} = \frac{-j}{\omega C} I_{(1)} = -9j8.485e^{j53} = 76.365e^{-j37}$$

$$u_3(t) = 30\sin(\omega t - 30^\circ) \rightarrow \underline{U}_{(3)} = \frac{30}{\sqrt{2}}e^{-j30}$$

$$I_{(3)} = \frac{\underline{U}_{(3)}}{\underline{Z}_{(3)}} = \frac{30e^{-j30}}{\sqrt{2} \left[R + j \left(3\omega L - \frac{1}{3\omega C} \right) \right]} = \frac{30e^{-j30}}{\sqrt{2} [6 + j(3 - 3)]} = 3.536e^{-j30}$$

$$\underline{U}_{C(3)} = \frac{-j}{3\omega C} I_{(3)} = -3j3.536e^{-j30} = 10.608e^{-j120}$$


$$I = \sqrt{I_{(0)}^2 + I_{(1)}^2 + I_{(3)}^2} = \sqrt{0^2 + 8.485^2 + 3.536^2} = 9.192 (A)$$

$$u_C(t) = U_{(0)} + u_{C(1)}(t) + u_{C(3)}(t) = 15 + 76.365\sqrt{2}\sin(\omega t - 37^\circ) + 10.608\sqrt{2}\sin(3\omega t - 120^\circ) [V]$$

DC: - prim condensator nu
face curent

- bobina e considerata
nu fuz (nu are resist.)

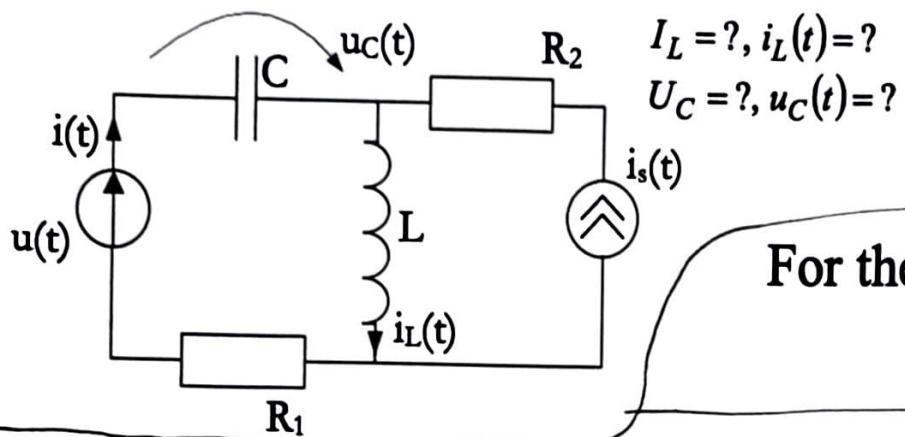$f_1 = f_{U_1} - f_{S_1}$ - for the fundamental
- same for 3rd, 5th, ...
harmonics.




$$R_1 = 5\Omega, R_2 = \omega L = 1/\omega C = 10\Omega$$

$$u(t) = 100 + 50 \sin(\omega t - 30^\circ) [V] \quad i_s(t) = 10 + 5 \sin(2\omega t) [A]$$

For the DC component: $U_{(0)} = 100V, I_{s(0)} = 10A$

$$U_{C(0)} = U_{(0)} = 100V, I_{L(0)} = I_{s(0)} = 10A$$

For the fundamental component:

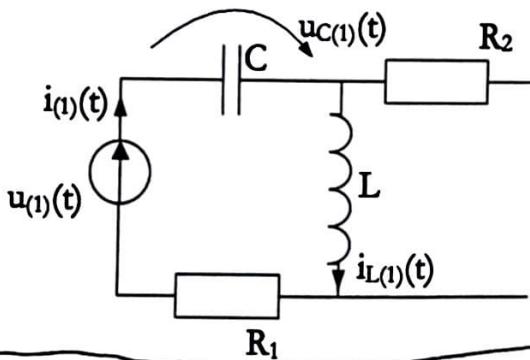


$$u_1(t) = 50 \sin(\omega t - 30^\circ) \rightarrow U_{(1)} = \frac{50 e^{-j30}}{\sqrt{2}}$$

$$I_{(1)} = I_{L(1)} = \frac{U_{(1)}}{Z_{(1)}} = \frac{50 e^{-j30}}{\sqrt{2} \left[R + j \left(\omega L - \frac{1}{\omega C} \right) \right]} = \frac{50 e^{-j30}}{\sqrt{2} [5 + j(10 - 10)]} = \frac{10}{\sqrt{2}} e^{-j30}$$

$$U_{C(1)} = -j \frac{1}{\omega C} I_{(1)} = -10j \frac{10}{\sqrt{2}} e^{-j30} = \frac{100}{\sqrt{2}} e^{-j120}$$

For the 2th order harmonic:

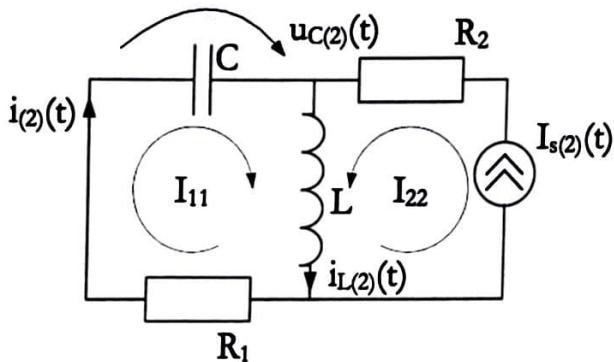

$$i_{s(2)}(t) = 5 \sin(2\omega t) \rightarrow I_{s(2)} = \frac{5}{\sqrt{2}}$$

$$I_{22} = I_{s(2)} = \frac{5}{\sqrt{2}}$$

$$I_{11} \left[R_1 + j2\omega L - \frac{j}{2\omega C} \right] + j2\omega L I_{22} = 0$$

$$I_{(2)} = I_{11} = -4.243 - j1.414 = 4.472 e^{-j162}$$

$$I_{L(2)} = I_{11} + I_{22} = -0.707 - j1.414 = 1.581 e^{-j117}$$


$$U_{C(2)} = -j \frac{1}{2\omega C} I_{(2)} = -7.071 + j21.213 = 108.435 e^{j108}$$

$$I = \sqrt{I_{(0)}^2 + I_{(1)}^2 + I_{(2)}^2} = \sqrt{10^2 + \left(\frac{10}{\sqrt{2}}\right)^2 + 1.581^2} = 12.349 [A]$$

$$i_L(t) = I_{L(0)} + i_{L(1)}(t) + i_{L(2)}(t) = 10 + 10 \sin(\omega t - 30^\circ) + 1.581\sqrt{2} \sin(2\omega t - 117^\circ) [A]$$

$$U_C = \sqrt{U_{C(0)}^2 + U_{C(1)}^2 + U_{C(2)}^2} = \sqrt{100^2 + \left(\frac{100}{\sqrt{2}}\right)^2 + 108.435^2} = 163.579 (V)$$
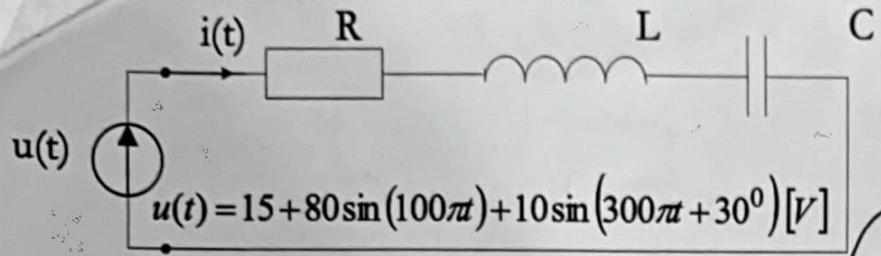
$$u_C(t) = U_{C(0)} + u_{C(1)}(t) + u_{C(2)}(t) = 100 + 100 \sin(\omega t - 120^\circ) + 108.435\sqrt{2} \sin(2\omega t - 108^\circ) [V]$$



$$R = 6\Omega$$

$$L = 100\text{mH}$$

$$C = 200\mu\text{F}$$

$$U = ?$$

$$u_C(t) = ?$$

$$P = ?, Q = ?, D = ?$$

$$U = \sqrt{U_{(0)}^2 + U_{(1)}^2 + U_{(3)}^2} = \sqrt{15^2 + \left(\frac{80}{\sqrt{2}}\right)^2 + \left(\frac{10}{\sqrt{2}}\right)^2} = 59 (\text{V})$$

For the DC component: $U_{(0)} = 15 \text{V}$, $I_{(0)} = 0 \text{A}$, $U_{C(0)} = U_{(0)} = 15 \text{V}$

For the fundamental component: $u_1(t) = 80 \sin(100\pi t) \rightarrow U_{(1)} = \frac{80}{\sqrt{2}}$

$$X_{L(1)} = \omega L = 100\pi \cdot 0.1 = 31.42 (\Omega)$$

$$X_{C(1)} = \frac{1}{\omega C} = \frac{1}{100\pi \cdot 200 \cdot 10^{-6}} = 15.92 (\Omega)$$

$$I_{(1)} = \frac{U_{(1)}}{Z_{(1)}} = \frac{U_{(1)}}{R + j(X_{L(1)} - X_{C(1)})} = 3.07 e^{-j57}$$

$$U_{C(1)} = -jX_{C(1)} I_{(1)} = 48.81 e^{-j147}$$

For the 3th order harmonic: $u_3(t) = 10 \sin(300\pi t + 30^\circ) \rightarrow U_{(3)} = \frac{10}{\sqrt{2}} e^{j30}$

$$X_{L(3)} = 3\omega L = 3 \cdot 100\pi \cdot 0.1 = 94.25 (\Omega)$$

$$X_{C(3)} = \frac{1}{3\omega C} = \frac{1}{3 \cdot 100\pi \cdot 200 \cdot 10^{-6}} = 5.31 (\Omega)$$

$$I_{(3)} = \frac{U_{(3)}}{Z_{(3)}} = \frac{U_{(3)}}{R + j(X_{L(3)} - X_{C(3)})} = 0.08 e^{-j53}$$

$$U_{C(3)} = -jX_{C(3)} I_{(3)} = 0.42 e^{-j143}$$

$$u_C(t) = U_{(0)} + u_{C(1)}(t) + u_{C(3)}(t) = 15 + 48.81\sqrt{2} \sin(100\pi t - 147^\circ) + 0.42\sqrt{2} \sin(300\pi t - 143^\circ) [\text{V}]$$

$$I = \sqrt{I_{(0)}^2 + I_{(1)}^2 + I_{(3)}^2} = \sqrt{0^2 + 3.07^2 + 0.08^2} \cong 3.07 (\text{A})$$


$$S = UI = 59 \cdot 3.07 = 180.83 [\text{VA}]$$

$$P = U_{(0)} I_{(0)} + U_{(1)} I_{(1)} \cos \varphi_1 + U_{(3)} I_{(3)} \cos \varphi_3 = \frac{80}{\sqrt{2}} 3.07 \cos(0 - (-57)) + \frac{10}{\sqrt{2}} 0.08 \cos(30 - (-53)) = 94.11 [\text{W}]$$

$$P = I^2 R = 94.11 [\text{W}]$$

$$Q = U_{(1)} I_{(1)} \sin \varphi_1 + U_{(3)} I_{(3)} \sin \varphi_3 = \frac{80}{\sqrt{2}} 3.07 \sin(0 - (-57)) + \frac{10}{\sqrt{2}} 0.08 \sin(30 - (-53)) = 146.33 [\text{VAR}]$$
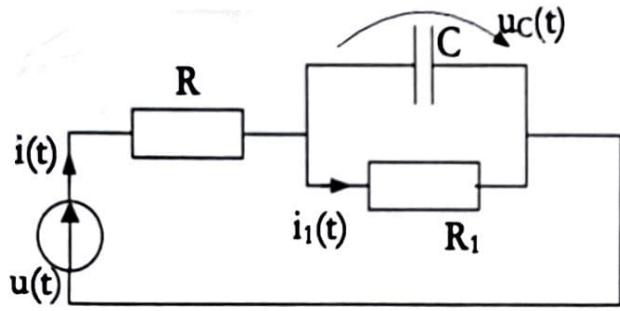
$$D = \sqrt{S^2 - P^2 - Q^2} = 49.34 [\text{VAD}]$$



$$u(t) = 50 + 100 \sin\left(400t + \frac{\pi}{6}\right) + 50 \sin\left(1200t - \frac{\pi}{4}\right) [V]$$

$$R = 30\Omega, R_1 = 50\Omega, C = 50\mu F$$

$U = ?$
 $I = ?, I_1 = ?$
 $u_C(t) = ?$
 $P = ?, Q = ?, D = ?$

For the DC component:

$$U_{(0)} = 50V, \quad I_{(0)} = I_{1(0)} = \frac{U_{(0)}}{R + R_1} = 0.625A \quad U_{C(0)} = I_{1(0)}R_1 = 31.25V$$

For the fundamental component:

$$u_1(t) = 100 \sin\left(400t + \frac{\pi}{6}\right) \rightarrow \underline{U}_{(1)} = \frac{100}{\sqrt{2}} e^{j\frac{\pi}{6}}$$

$$X_{C(1)} = \frac{1}{\omega C} = \frac{1}{400 \cdot 50 \cdot 10^{-6}} = 50(\Omega)$$

$$\underline{Z}_{p(1)} = \frac{R_1(-jX_{C(1)})}{R_1 - jX_{C(1)}} = 25 - 25j (\Omega), \quad \underline{Z}_{e(1)} = R + \underline{Z}_{p(1)} = 55 - 25j (\Omega)$$

$$\underline{I}_{(1)} = \frac{\underline{U}_{(1)}}{\underline{Z}_{e(1)}} = 0.681 + j0.952 = 1.17 e^{j54^\circ} \quad \underline{U}_{C(1)} = \underline{I}_{(1)} \underline{Z}_{p(1)} = 40.819 + j6.79 = 41.38 e^{j9^\circ} \quad \underline{I}_{1(1)} = \frac{\underline{U}_{C(1)}}{R_1} = 0.816 + j0.136 = 0.828 e^{j9^\circ}$$

For the 3th order harmonic:

$$u_3(t) = 50 \sin\left(1200t - \frac{\pi}{4}\right) \rightarrow \underline{U}_{(3)} = \frac{50}{\sqrt{2}} e^{-j\frac{\pi}{4}}$$

$$X_{C(3)} = \frac{1}{3\omega C} = \frac{1}{1200 \cdot 50 \cdot 10^{-6}} = 16.667(\Omega)$$

$$\underline{Z}_{p(3)} = \frac{R_1(-jX_{C(3)})}{R_1 - jX_{C(3)}} = 5 - 15j (\Omega), \quad \underline{Z}_{e(1)} = R + \underline{Z}_{p(1)} = 35 - 15j (\Omega)$$

$$\underline{I}_{(3)} = \frac{\underline{U}_{(3)}}{\underline{Z}_{e(3)}} = 0.862 - j0.345 = 0.928 e^{-j22^\circ} \quad \underline{U}_{C(3)} = \underline{I}_{(3)} \underline{Z}_{p(3)} = -0.862 - j14.655 = 14.68 e^{-j93^\circ} \quad \underline{I}_{1(3)} = \frac{\underline{U}_{C(3)}}{R_1} = -0.017 - j0.293 = 0.294 e^{-j93^\circ}$$

$$I = \sqrt{I_{(0)}^2 + I_{(1)}^2 + I_{(3)}^2} = \sqrt{0.625^2 + 1.17^2 + 0.928^2} \approx 1.619 (A) \quad I_1 = \sqrt{I_{1(0)}^2 + I_{1(1)}^2 + I_{1(3)}^2} = \sqrt{0.625^2 + 0.828^2 + 0.294^2} \approx 1.078 (A)$$

$$u_C(t) = U_{(0)} + u_{C(1)}(t) + u_{C(3)}(t) = 31.25 + 41.38\sqrt{2} \sin(400t + 9^\circ) + 14.68\sqrt{2} \sin(300\pi t - 93^\circ) [V]$$

$$P = U_{(0)}I_{(0)} + U_{(1)}I_{(1)} \cos \varphi_1 + U_{(3)}I_{(3)} \cos \varphi_3 = 50 \cdot 0.625 + \frac{100}{\sqrt{2}} 1.17 \cos(-24^\circ) + \frac{50}{\sqrt{2}} 0.928 \cos(-23^\circ) = 136.765 [W]$$

$$P = I^2 R + I_1^2 R_1 = 136.765 W$$

$$Q = U_{(1)}I_{(1)} \sin \varphi_1 + U_{(3)}I_{(3)} \sin \varphi_3 = \frac{100}{\sqrt{2}} 1.17 \sin(-24^\circ) + \frac{50}{\sqrt{2}} 0.928 \sin(-23^\circ) = -47.178 [VAR]$$

$$U = \sqrt{U_{(0)}^2 + U_{(1)}^2 + U_{(3)}^2} = \sqrt{50^2 + \left(\frac{100}{\sqrt{2}}\right)^2 + \left(\frac{50}{\sqrt{2}}\right)^2} = 93.541 (V)$$

$$S = UI = 93.541 \cdot 1.619 = 151.484 [VA]$$

$$D = \sqrt{S^2 - P^2 - Q^2} = 45 [VAD]$$