

One Hot encoding for FSMs


Proposed problems

Oprițoiu Flavius
flavius.opritoiu@cs.upt.ro

September 28, 2026

 
Problem 1

Construct the frequency divider *fdivby5* depicted bellow:




Problem 1 (contd.)

Test the unit with a testbench that generates the inputs as in the diagram bellow:

 

 Problem 2

Prepare the implementation of a One Hot encoded, divide-by-3 frequency divider, called *fdivby3*, whose transition diagram is depicted bellow:




Problem 2 (contd.)

The module will have the following interface:

```
1 module fdivby3 (  
2     input  clk , rst_b , clr , c_up ,  
3     output fdclk  
4 );
```

Test the unit with a testbench that generates the inputs as in the diagram bellow:

 

Problem 3

Using the One Hot encoding, implement a divide-by-6 frequency divider that activates its output for 4 consecutive clock cycles (whichever 4 consecutive states).

Test the unit with a testbench that generates the inputs as in the diagram bellow:

