

Hardware design of a Sign-Magnitude sequential multiplier

Oprițoiu Flavius
flavius.opritoiu@cs.upt.ro

September 28, 2026

Introduction


Objectives:

- ▶ Construct a sequential architecture for Sign-Magnitude multiplication

Architecture's characteristics:

- Operate fractional numbers on 8 bits
- Design and customize multiplier's components
- Design the control path of the architecture

 Sign-Magnitude sequential multiplier architecture



Note: Except rst_b, all other signals are *synchronous*.

Register M (solved)

Stores the multiplicand, having the following interface:

- ▶ ld_ibus: loads multiplicand's value from INBUS
 - ▶ ibus: the INBUS lines
- ▶ q: register's content

```
1 module reg_m(  
2     input clk , rst_b , ld_ibus , [7:0] ibus ,  
3     output reg [7:0] q  
4 );  
5     always @ (posedge clk , negedge rst_b)  
6         if (!rst_b) q <= 0;  
7         else if (ld_ibus) q <= ibus;  
8 endmodule
```

Register Q

Stores the multiplier, having the following interface:

- ▶ `clr_lsb`: clear register's LSB
- ▶ `ld_ibus`: loads multiplier's value from INBUS
 - ▶ `ibus`: the INBUS lines
- ▶ `sh_r`: right shifts the register's content
 - ▶ `sh_i`: bit to be loaded into MSB during right shift
- ▶ `ld_obus`: deliver accumulator's content onto OUTBUS
 - ▶ `obus`: the OUTBUS lines
- ▶ `q`: register's content

```
1 module reg_q(  
2     input clk, rst_b, clr_lsb, ld_ibus, ld_obus, sh_r,  
3     input sh_i, [7:0] ibus,  
4     output reg [7:0] obus, [7:0] q  
5 );  
6     always @ (posedge clk, negedge rst_b)  
7         //treat inputs rst_b, clr_lsb, ld_ibus, sh_r here  
  
9     always @ (*) //write content to obus when ld_obus==1  
10         obus = (ld_obus) ? q : 8'bz;  
11 endmodule
```

Register A

Multiplier's accumulator, it has the following interface:

- ▶ `clr`: synchronous, active high reset
- ▶ `ld_sum`: loads adder's result into accumulator
 - ▶ `sum`: adder's result to be loaded into accumulator
- ▶ `ld_sgn`: loads accumulator's sign
 - ▶ `sgn`: accumulator's sign
- ▶ `ld_obus`: unload accumulator's content onto OUTBUS
 - ▶ `obus`: the OUTBUS lines
- ▶ `sh_r`: right shift register's content
 - ▶ `sh_i`: bit to be loaded into MSB during right shift
- ▶ `q`: accumulator's content

```
1 module reg_a(  
2     input  clk, rst_b, clr, sh_r, ld_sgn, ld_obus, ld_sum,  
3     input  sh_i, sgn, [7:0] sum,  
4     output reg [7:0] obus, [7:0] q  
5 );  
6     //implementation here  
  
8     //write content to obus  
9 endmodule
```


Control Unit

The control unit has the following interface:

- ▶ `bgn`: starts the multiplication
- ▶ `q_0`: register Q's LSB
- ▶ `cnt_is_7`: active if COUNTER's value is 7
- ▶ `c0`: clears registers A and COUNTER, loads M from INBUS
- ▶ `c1`: loads Q from INBUS
- ▶ `c2`: loads adder's result back into A
- ▶ `c3`: right-shifts A concatenated with Q (introduce a bit of 0 in register A's MSB), increments COUNTER
- ▶ `c4`: sets sign of register A, clear register Q's LSB
- ▶ `c5/c6`: deliver register A/Q to OUTBUS
- ▶ `fin`: marks multiplication completion, activated along c5, c6

```
1 module ctrl_u(  
2     input  clk, rst_b, bgn, q_0, cnt_is_7,  
3     output c0, c1, c2, c3, c4, c5, c6, fin  
4 );  
5     //implementation here  
6 endmodule
```

Control Unit (contd.)

 

Important: Control unit must be triggered by the opposite edge of the clock, compared to all the other sequential elements in the architecture!

Putting together all the components

The Sign-Magnitude sequential multiplier's architecture:

```
1 module sm_unit (  
2     input clk, rst_b, bgn, [7:0] ibus,  
3     output fin, [7:0] obus  
4 );  
5     //implementation here  
6 endmodule  
  
8 module sm_unit_tb;  
9     reg clk, rst_b, bgn; reg [7:0] ibus; wire fin; wire [7:0] obus;  
  
11    sm_unit test (.clk(clk), .rst_b(rst_b), .bgn(bgn), .ibus(ibus),  
12        .fin(fin), .obus(obus));  
13    localparam CLK_PERIOD=100, CLK_CYCLES=17, RST_PULSE=25;  
14    localparam X=8'b10010111/*=-23*2-7*/, Y=8'b10000011;/*=-3*2-7*/  
15    initial begin clk=1'd0; repeat (CLK_CYCLES*2) #(CLK_PERIOD/2) clk=~clk; end  
16    initial begin rst_b=1'd0; #(RST_PULSE); rst_b=1'd1; end  
17    initial begin bgn=1'd1; #200; bgn=1'd0; end  
18    initial begin ibus=0; #100 ibus=X; #100 ibus=Y; end  
19 endmodule
```

Testbench keeps OUTBUS in high impedance until 1300 time units, when, for 1 clock cycle OUTBUS becomes 8'b00000000, than, for another clock cycle, OUTBUS becomes 8'b10001010 only to remain in high impedance afterwards.