

Writing parameterized modules

Oprițoiu Flavius
flavius.opritoiu@cs.upt.ro

September 28, 2026

Introduction

Objectives:

- ▶ Datapath and control path separation
- ▶ Understand how to write parameterized modules

Datapath

- Consists of elements processing the data: no decisions are taken
- Typical components: multiplexers, registers, Arithmetic and Logic Units (ALUs), counters
- Construct shared buses using three-state drivers

Control path

- Concerned with decision making
- Described in terms of state machines

Note: State-enabled components (such as registers, counters) can be part of the datapath, as well.

Reusable modules

Reusable modules are defined in terms of *parameters*, which can be redefined. In Verilog 2001 the module's parameters are specified in a dedicated section, marked by #(and) symbols.

The code bellow describes a parallel load register with parameterized width (no. of bits) and initialization value (register content after reset or clear).

```
1  module rgst #(
2      parameter w = 8,           //register's width parameter; default of 8
3      parameter iv = {w{1'b0}} //initialization value parameter
4  )(
5      input clk ,
6      input rst_b ,               //asynchronous reset; active low
7      input [w-1:0] d,           //input data, on w bits
8      input ld ,                 //synchronous load; active high
9      input clr ,               //synchronous clear; active high
10     output reg [w-1:0] q       //register's content, on w bits
11 );
12
13     always @ (posedge clk , negedge rst_b)
14         if (!rst_b)
15             q <= iv; //set content to initialization value
16         else if (clr)
17             q <= iv; //set content to initialization value
18         else if (ld)
19             q <= d;
20 endmodule
```

Reusable modules (contd.)

In-line, explicit redefinition of module's parameters, in Verilog 2001, uses the following format:

```
module-name #(.parameter-name(value), ...)  
    instance_name (.port-name(signal), ...)
```

Code bellow instantiate a 16-bit register, with an initialization value of 0

```
1  rgst #(  
2      .w(16)  
3  ) registru1 (  
4      .clk(clk), ...  
5  );
```

Code bellow instantiate a 4-bit register, initialized 15

```
1  rgst #(  
2      .w(4),  
3      .iv(4'd15)  
4  ) registru2 (  
5      .clk(clk), ...  
6  );
```

Solved problem

Constructing a register file using discrete registers

Exercise: Construct a 4×8 register file.

Solution: An $M \times N$ *register file* is a storage element organized as an array of **M** registers, each register having **N** bits. It permits simultaneous reading one internal register and writing one internal register (possibly the same).

A register file's interface includes the following connections:


- an N -bit data input, for writing internal registers (wr_data)
- an N -bit data output, for reading internal registers (rd_data)
- an input address, selecting the register to be written (wr_addr)
- an output address, selecting the register to be read (rd_addr)
- data write enable signal (wr_e)
- data read enable signal (rd_e)

The enable lines of the writing/reading port are optional. **M** is, typically, of form 2^k : the input/output addresses use k bits.

Solved problem (contd.)

Constructing a register file using discrete registers

 The interface of a $4 \times n$ register file is depicted bellow




For this case, the interface is made up of:

- the writing port (*wr_data*, *wr_addr*, *wr_e*)
- the reading port (*rd_data*, *rd_addr*, *rd_e*)
- clock signal (*clk*)
- reset signal (*rst_b*)

Solved problem (contd.)

Constructing a register file using discrete registers

 
An 4x8 register file with no output enable line:



Note: The clock and reset lines were omitted for brevity.

Three-state driver

 Used for connecting several components on a shared line or bus.



Output *o* is set to *i* when enable line, *e*, is active, and to *high impedance* otherwise. An output set to high impedance (symbolized by *z*, in Verilog) allows other component to drive the logic level of the shared line or bus it connects to.

The code fragment bellow demonstrates commanding a signal into high impedance by a control line, *e*:


```
1  wire [15:0] data , data_hiz ;  
2  assign data_hiz = (e) ? data : 16'bz ;
```

Because the high impedance symbol, *z*, is the most significant bit of the constant in line 2, it is extended to 16 high impedance bits.

Solved problem

Constructing a multiplexer using three-state drivers

 An n -bit 4-to-1 multiplexer, implemented with three-state drivers:



Multiplexer's select input, s , drives a 1-out-of-4 decoder. The final stage connects all three-state drivers' outputs together.