

Handshake signaling for data transfer

Proposed problems

Oprițoiu Flavius
flavius.opritoiu@cs.upt.ro


September 28, 2026

Problem 1

Build a module called *prod* (producer) having inputs *clk* (1-bit) and *rst_b* (1-bit) and outputs *val* (1-bit) and *data* (8-bits). The module produces random values between 0 and 5. Output *val* (*valid* handshaking signal) announces when the unit cannot produce new data (*val* == 0).

The module will generate data for at least 3 and at most 5 clock cycles after which it will wait at least 1 and at most 4 clock cycles without producing new data. Build:

1. the Verilog code
2. the script file, "run_prod.txt"
3. a testbench generating inputs as in the timing diagram bellow

 


Problem 2

Construct a consumer module called *cons* (consumer) having inputs *clk* (1-bit), *rst_b* (1-bit), *val* (1-bit) and *data* (8-bits) and having one output *sum* (8-bit). The module consumes data generated by the producer. At the output *sum*, the consumer provides the sum of all valid data received. The testbench will instantiate the producer module from Exercise 1 and connects the 2 modules together.

Build:

1. the Verilog code
2. the script file, "run_cons.txt"
3. a testbench generating inputs as in the timing diagram bellow

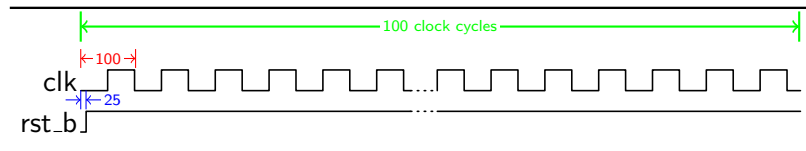

Problem 3

Modify the consumer module from Problem 2 so that at any moment, at its output it provides the sum of the latest monotonically increasing sequences of valid data.

A valid data is part of a monotonically increasing sequence if it is greater or equal than the previous valid data. Example: the sequence 0, 1, 1, 3, 3, 3, 5 is monotonically increasing and corresponding to this sequence, the consumer's output is expected to be 0, 1, 2, 5, 8, 11, 16. The sequence 0, 1, 4, 3, 2, 3, 5 is made up of 3 monotonically increasing sub-sequences and the consumer's output is expected to be 0, 1, 5, 3, 2, 5, 10.

Problem 4

Build the control unit described in the Solved problem of this week's material, called *sha2inctrl*. The testbench will instantiate the *sha2indpath* module constructed last week, which will be controlled by this control unit and connects the two modules together.

Build:

1. the Verilog code
2. the script file, "run_sha2inctrl.txt"
3. a testbench generating inputs as in the timing diagram bellow

